

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Z \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\text{ref } i_3 = 0 \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} CR & 0 & g - CR \\ 0 & G & -G \\ -g - CR & -G & G + CR \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} \Rightarrow \begin{bmatrix} C & 0 & -C \\ 0 & 0 & 0 \\ -C & 0 & C \end{bmatrix} v = \begin{bmatrix} 0 & 0 & -g \\ 0 & -G & G \\ g & G & -G \end{bmatrix} v + \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$y = \text{output}$
 $u = \text{input}$

$$A E x = D v + B u, \quad x = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}, \quad u = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$y = C x$$

$$y = Cx, \quad (AE - a)Y = Bu; \quad x = (AE - a)^{-1}Bu$$

$$= C(AE - a)^{-1}Bu \quad \text{hence } Z = C(AE - a)^{-1}B$$

output \uparrow \downarrow input

$$Z(a) = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}^{-1} \begin{bmatrix} ac & b & ga + c \\ 0 & c & -c \\ -g - ac & -c & ac + c \end{bmatrix}^{-1} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}$$

to get the inverse: $\det = acg(ac+c) + 0 + 0 - [-(g+ac)(g-ac)g + g^2ac]$
 $= a^3c^2g + acg^2 + g^2g - a^2cg - g^2ac = g^2g = \det$

$$\Delta_{11} = g(ac+c) - g^2 = acg \quad \Delta_{21} = (-1)(cg - acg)$$

$$\Delta_{12} = (-1)^3(-g(ac+c)) \quad \Delta_{22} = ac(ac+c) + (cg^2 - (ac)^2)$$

$$\Delta_{13} = gac + acg \quad \Delta_{23} = (-1)(-gac) \quad \Delta_{33} = acg$$


$$Z(s) = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \frac{1}{s^2 G} \begin{bmatrix} RCG & -Gs + RCG & -G(s-Rc) \\ G(s+Rc) & s^2 + RCG & G-Rc \\ G(s+Rc) & RCG & RCG \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}$$

$$= \frac{1}{s^2 G} \begin{bmatrix} RCG & -Gs + RCG & -G(s-Rc) \\ G(s+Rc) & s^2 + RCG & G-Rc \\ G(s+Rc) & RCG & RCG \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}$$

$$= \frac{1}{s^2 G} \begin{bmatrix} RCG & -Gs + RCG \\ G(s+Rc) & s^2 + RCG \end{bmatrix} = \frac{1}{s} \begin{bmatrix} c/g^2 & c/g^2 \\ c/g^2 & c/g^2 \end{bmatrix} + \frac{1}{s} \begin{bmatrix} 0 & -1/g \\ 1/g & 0 \end{bmatrix} + \frac{1}{s} \begin{bmatrix} 0 & 0 \\ 0 & 1/g \end{bmatrix}$$

Z_R Z_{gg} Z_R

$$L = c/g^2$$

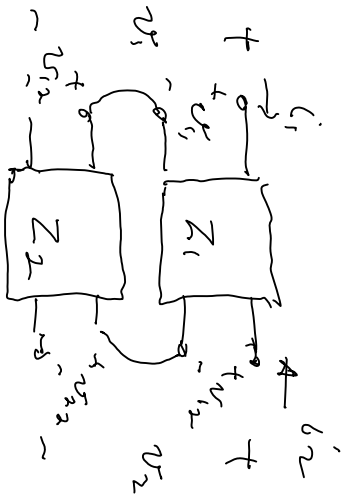

for our case

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} v_1' \\ v_2' \end{bmatrix} + \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Z_1 i + Z_2 i = \underset{\text{matrix}}{Z} \cdot i$$

$$R = 1/G$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$i_2 = 0$


$$Z_{12} = Z_{21} = \frac{v_2}{i_1} \Big|_{i_2=0}$$

$$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$i_2 = 0$

$$v_2 = Z_{21} i_1 \Big|_{i_2=0}$$

an equivalent circuit

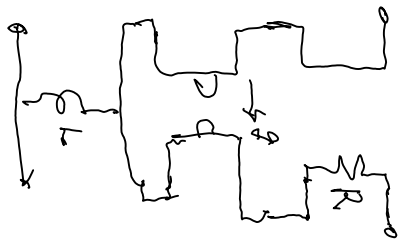

$$Z_L \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$I_{z_2} v = z_2 c'$$

$$y v = I_{z_2} c'$$

$$A_{(z_2)} v = B_{(z_2)} c'$$

now v & c' are root variables



$$\Rightarrow \begin{matrix} v_1 = 0 \\ v_2 = 0 \end{matrix} \quad \begin{matrix} c_1 = 0 \\ c_2 = 0 \end{matrix}$$

v_2, c_2 don't

$$\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} c_1 \\ c_2 \end{bmatrix}$$

$$\begin{matrix} z v = v + R c \\ z v = v - R c \end{matrix} \quad \begin{matrix} v = \text{incident} \\ v = \text{reflected} \end{matrix}$$

$$v = S v', \quad S = \text{scattering matrix}$$

$$I(t) = \begin{cases} 1 & \text{if } t > 0 \\ 0 & \text{if } t < 0 \end{cases}$$

= unit step function



$$\begin{matrix} Z = A^{-1} \\ Y = B^{-1} A \end{matrix}$$

$$I_m = m \times m \text{ identity} = \begin{bmatrix} 1 & 0 & 0 & \dots & 0 \\ 0 & 1 & 0 & \dots & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ 0 & \dots & 0 & \dots & 1 \end{bmatrix}$$

$$Zv = Z(v' + v^n)$$

$$2Rv' = Z(v' - v^n)$$

$$\Rightarrow A(v' + v^n) = B \cdot R^{-1}(v' - v^n)$$

$$(A - BR^{-1})v' = (BR^{-1} + A)(-v^n)$$

$$v^n = (BR^{-1} + A)^{-1}(BR^{-1} - A) \cdot v'$$

if $R = I_m$, A & B $m \times n$

$$S = (B + A)^{-1}(B - A) \quad \text{if } Z \text{ then } (A(A^{-1}B + I_m))^{-1}(A(A^{-1}B - I_m))$$

$$S = (Z + I_m)^{-1}A^{-1}A(Z - I_m)$$

$$= (Z + I_m)^{-1}(Z - I_m)$$

$$\text{if } Y \text{ exists } = (I_m + B^{-1}A)^{-1}(I_m - B^{-1}A) = (I_m + Y)^{-1}(I_m - Y)$$