



$$E(\infty) = \int_{-\infty}^{\infty} \frac{1}{2\pi} \frac{e^{i\tau t}}{i\tau} [1_m - S(j\omega)]^T S(j\omega) \frac{d\omega}{2\pi} e^{i\omega t}$$

$2 v^o = v + v^i$
 $2 v^o = v - v^i$
 $S v^i = v^o$

Rational BR

- 1) $S(\omega)$ has real coefficients
- 2) $S(\omega)$ has poles in $\sigma < 0$
(analytic in closed RHP)
- 3) $1_m - S(j\omega) S(j\omega)^T \geq 0$ Positive semidefinite

$\omega = \sigma + j\omega$


for all v^i
 if ≤ 0 for some v^i (if ≤ 0 for some v^i \Rightarrow active)
 if $= 0$ N is lossless \Rightarrow active

$\frac{1}{a-a}$

$f(t) = e^{-at}$




unstable

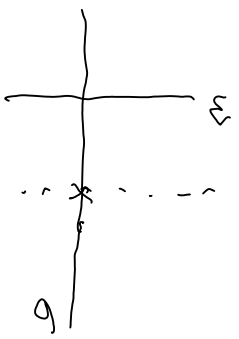

Let $\delta \omega \rightarrow a$ $\Gamma_{\text{cap}} S(-a) S(a) = \mathbf{0}_m$ of lossless $S(-a)^T = S(a)^{-1} \Rightarrow S(a) = S(-a)^T$

Ex: $S(a) = \frac{1-c a}{1+c a} = \frac{1-y}{1+y}$ $S(-a) = \frac{1-c(-a)}{1+c(-a)} = \frac{1+ca}{1-ca} = \frac{1}{S(a)}$

circulator:

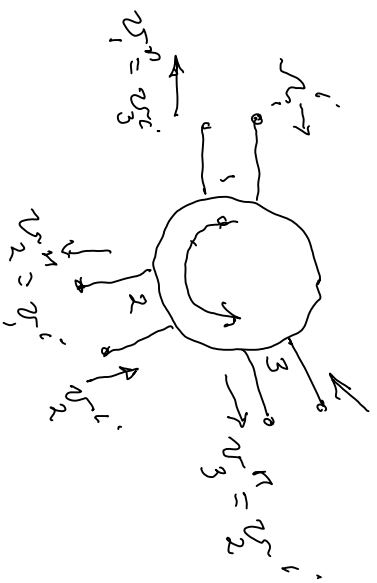

$v_1^r = S v_1^i$

$$\begin{bmatrix} v_1^r \\ v_2^r \\ v_3^r \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1^i \\ v_2^i \\ v_3^i \end{bmatrix}$$

(check lossless)

$$S_{\text{ris}} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix} \Rightarrow I_3 - S_{\text{ris}}^T S_{\text{ris}} = I_3 - \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix} = I_3 - S_{\text{ris}}^T S_{\text{ris}}$$

$$I_3 - \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = Q_3 = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

Need to look PR = positive real (rational)

- def: $Y(s)$
- 1) $Y(s)$ is real for $\sigma > \sigma_0$
 - 2) $Y(s)$ is analytic in $\sigma > \sigma_0$
 - 3) $Y(s) + Y(s)^T > 0$ in $\sigma > \sigma_0$

$$\begin{aligned} \mathcal{E}(r) &= \int_{-\infty}^t p(r) dr = \int_{-\infty}^t v(r) v'(r) dr = \int_{-\infty}^t i(r) v(r) dr \\ &= \int_{-\infty}^t \frac{(v(r) v'(r) + i(r) v(r))}{2} dr \end{aligned}$$

$$\int_{-\infty}^{\infty} f(t) g(t) dt = \int_{-\infty}^{\infty} f^*(\omega) G(\omega) \frac{d\omega}{2\pi} \Rightarrow \text{Plancherel's theorem}$$

if f & g are square integrable

$$I_{g(\omega)} = Y(\omega) V(\omega)$$

$$\mathcal{E}(\infty) = \int_{-\infty}^{\infty} \frac{(V^* \cdot I + I^* V)}{2} \frac{d\omega}{2\pi} \geq 0 \text{ if positive}$$

$$\mathcal{E}(\infty) = \int_{-\infty}^{\infty} V^* (Y(\omega) + Y^*(\omega)) V(\omega) \frac{d\omega}{2\pi} \Rightarrow \frac{Y(\omega) + Y^*(\omega)}{2} \geq 0$$

$$\frac{Y(\omega) + Y(-j\omega)^T}{2} \geq 0, \text{ real } j\omega = \alpha \Rightarrow \text{analytically continues to all } \alpha \text{ (except poles)}$$

$$Y(\alpha) + Y(-j\alpha)^T \geq 0 \text{ in } \sigma > 0$$

\Rightarrow leads to positive real; real $Y(\alpha) + Y(-j\alpha)^T = 2 \operatorname{Re} Y(\alpha)$

also $Y(\alpha) + Y(-\alpha)^T \Rightarrow 2 \operatorname{Re} Y(\alpha) = Y(\alpha) + Y(-\alpha)$

if lossless $Y(j\omega) + Y(-j\omega)^T = 0$ for almost $\omega \Rightarrow$ real $Y(\alpha) + Y(-\alpha) = 0$ if lossless

$$Y(\alpha) + Y(-\alpha)^T \geq 0 \text{ in } \sigma > 0 \quad (\text{from max } |e^{-s} Y(s)| = |e^{-\operatorname{Re} Y(j\omega)}|)$$

$$e^{-j\omega} = e^{-\operatorname{Re} Y(j\omega)} \cdot e^{j \operatorname{Im} Y(j\omega)} \Rightarrow |e^{-s}| = |e^{-\operatorname{Re} Y(j\omega)}|$$

$$Y \& e^{-s} \text{ are analytic in } \sigma > 0 \quad \Downarrow$$

$$\operatorname{Re} Y(\alpha) \geq 0 \text{ in } \sigma > 0$$

$$n=1, \quad y(a) + y(-a) = 0 \text{ if } \text{zeros} \\ \text{or } y(a)$$

$$\Rightarrow y(a) = \text{odd in } a = \frac{N_1 N_1'}{D_1} \text{ with } N_1 \& D_1 \text{ even}$$

$$\text{or } = \frac{1}{a} \frac{N_2'}{D_2} \text{ with } N_2 \& D_2 \text{ even}$$

polynomial

$$\therefore \text{there is a pole @ } a=0 \text{ or } 0$$

zeros $y(a) = \text{see later}$

function



$$y(-a) = -y(a)$$

$$\text{Ex: } y(a) = \frac{a^5 k 3a^3 + 2a}{a^4 + 5a^2 + 6} = a \left(\frac{a^4 + 3a^2 + 2}{a^4 + 5a^2 + 6} \right)$$

$$x = a^2: \quad x^2 + 3x + 2 \Rightarrow x_{1,2} = \frac{-3 \pm 1}{2} \sqrt{9 - 8} = -1, -2$$

$$x^2 + 5x + 6 \Rightarrow x_{1,2} = \frac{-5 \pm 1}{2} \sqrt{25 - 24} = -2, -3$$
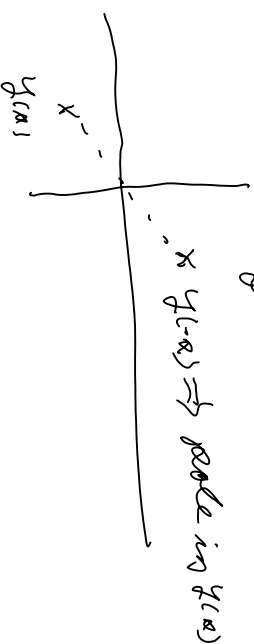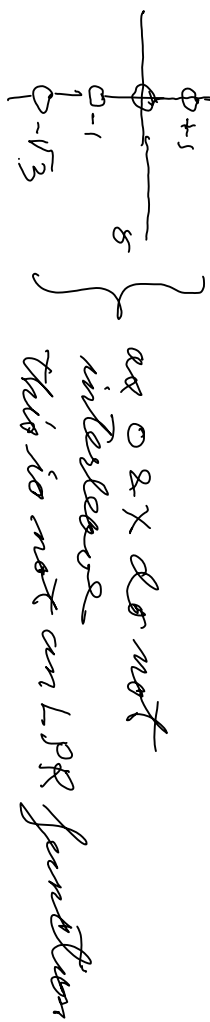
$$y(a) = \frac{a(a^2+1)(a^2+2)}{(a^2+2)(a^2+3)} = \frac{a(a^2+1)}{a^2+3}$$



no poles in $5 < 0$ or $5 > 0$
 \Rightarrow all poles are on $j\omega$ axis
 \Rightarrow as $y(a)$ is PR with $y(a)$
 \Rightarrow no zeros in $5 < 0, 5 > 0$

\therefore all poles & zeroes for a LPR are on the $j\omega$ axis (all poles & zeroes are simple zeros)

Comments on Spice for scattering matrices: The setup in the Cadence pdf file s-Parameter_Data_appnote.pdf (on the course web page) shows how to plot the scattering matrix entries for the sinusoidal steady state for any S_{ij} . Their setup is for 50 Ohm reference resistors so all ports should have 50 Ohm loading. This is already in the excitation port shown in their R2 of Fig. 4 where SFE is the terminal to measure the voltage as the reflection coefficient (diagonal entry ii of S), E2 and E1 (of Fig 1) are voltage controlled voltage sources of gain=2. Figure 1 gives the load circuit to attach to the transmission port (I when $j \neq i$) except a 50 Ohm load is needed from the CKT lead to ground. STR is the terminal at which to measure the voltage which is the transmission entry ij , $i \neq j$, of S . Their Figure 6 gives a nice example of use for obtaining all four entries of S for a 2-port. Note that their incident and reflected voltages have a square root of $Z_0=R$ factor included in Eq. (1) where the denominator Z is a misprint for Z_0 .