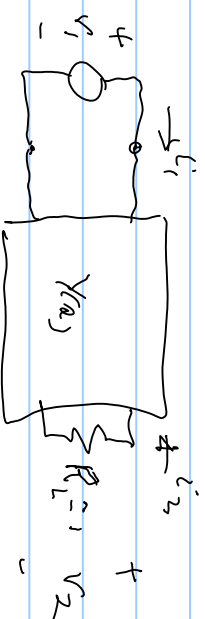


$$\frac{V_2(A)}{V_1} =$$



$$I_1 = g_{11} V_1 + g_{12} V_2,$$

$$I_2 = g_{21} V_1 + g_{22} V_2 = -g_{12} V_2$$

$$g_{21} V_1 = -(g_{12} + g_{22}) V_2$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{-g_{21}}{g_{12} + g_{22}} = \frac{-g_{21}/g_{12}}{1 + g_{22}/g_{12}}$$

$$\text{Let } g_{12} = 1 \Rightarrow \frac{V_2(A)}{V_1} = \frac{-g_{21}}{1 + g_{22}} = \frac{N(A)}{D(A)}$$

If \$D(A)\$ is strictly \$O\$ unity (true for \$B\_n(A)\$) then


$$D(A) = \sum D(A) + \text{adj } D(A) = \sum D(A) \left[ 1 + \frac{\text{adj } D(A)}{\sum D(A)} \right] = \text{adj } D(A) \left[ 1 + \frac{\sum D(A)}{\text{adj } D(A)} \right]$$

$$\frac{V_2}{V_1}(a) = \frac{-Y_{21}}{1+Y_{22}} = \frac{R(a)/\epsilon_r D(a)}{1 + \frac{\partial D(a)}{\partial V(a)}/\epsilon_r (V(a))} \Rightarrow \text{choose } Y_{22} = \frac{\partial D(a)}{\epsilon_r (V(a))}$$

$$\begin{aligned} \text{Eg: } \frac{V_2}{V_1}(a) &= \frac{-R}{[R+1]^3} = \frac{-R}{R^3 + 3R^2 + 3R + 1} = \frac{-R}{(3R^2+1) + (R^3+3R)} = \frac{-R/(3R^2+1)}{1 + \frac{(R^3+3R)}{3R^2+1}} \\ \therefore Y_{22} &= \frac{R(R^2+3)}{3R^2+1} = \frac{R(R^2+3)}{3(R^2+1/3)} \end{aligned}$$

$\uparrow$   
 3 ports of transmission @  $\infty$


Look at ladder circuits

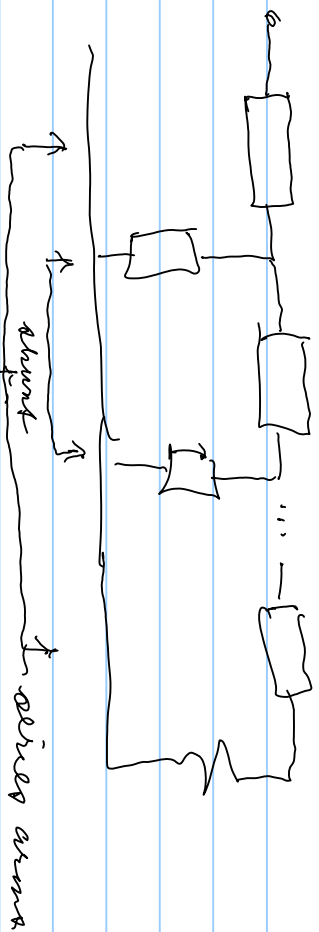

where resistors are open  $\Rightarrow$  a series of transmission  
 admittances " " short " " " "

if all resistors are at  $\infty$ , resistors have  $z(\infty) = \infty \Rightarrow z(\omega) = R_L$   
 admittance " " " "  $y(\infty) = \infty \Rightarrow y(\omega) = 1/R_C$

for our  $S_x$ : 3 poles

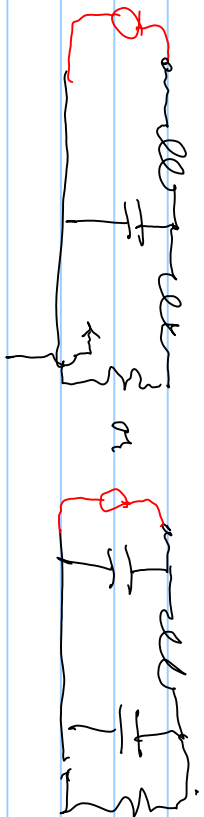

synthesizing  $y_{22}$  by 1st corner

know a pole @  $\infty$  of  $z \approx 1/y_{22}$

$\therefore$  need the possible  $y_{22}$  as our choice above has  $y_{22} \approx \frac{R_2^2}{3R_2}$  is a pole @  $\infty$   
 $\infty$


$$\therefore \text{choose for } \frac{1}{x^2} = \frac{1x/D(x)}{1 + \frac{8x^2+1}{3x^2+1}} \Rightarrow y = \frac{8x^2+1}{3x^2+1} = \frac{3x^2+1}{x^2+3x}$$

synthesizing  $y_{22}$  by lot cover:  $y_{22} =$

$$\frac{1}{3x^2+1} = \frac{1}{\frac{1}{3}x + \frac{1}{8}x + \frac{1}{3}}$$

$$\begin{array}{ccccccc} 2 & & 2 & & 2 & & 2 \\ & & \nearrow & & \nearrow & & \nearrow \\ & & \frac{1}{3}x & + & \frac{1}{8}x & + & \frac{1}{3} \\ & & & & & & + 0 \\ & & & & & & \end{array}$$

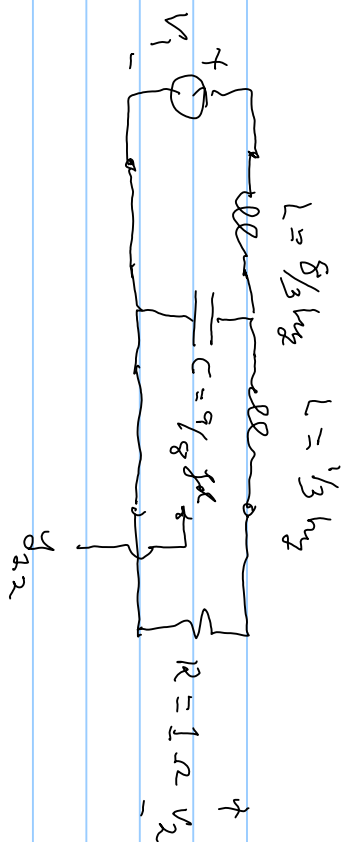
$$\begin{array}{ccccccc} 2 & \rightarrow & \frac{1}{3}x & & & & \\ & & \underbrace{\frac{3x^2+1}{x^2+3x}} & & \underbrace{\frac{9x}{3x^2+1}} & & \underbrace{\frac{8}{3}x} \\ & & \underbrace{\frac{8}{3}x} & & \underbrace{\frac{1}{3}} & & \end{array}$$



$$\frac{V_2}{V_1} = \frac{R}{(R+1)^3}$$

to get  $R$ : choose  $R = 0$
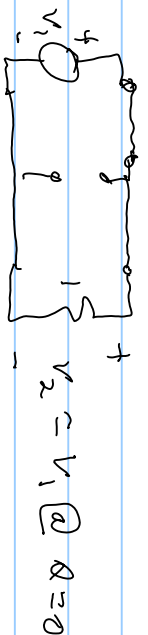
$$\frac{V_2}{V_1}(R) = \frac{R}{1^3} = R = 1 \text{ so } V_2 = V_1 \text{ in the circuit } V_1$$



as a check: let  $R = 1$



$$i_1 = 1 + 3/2 = 5/2 \text{ amp}$$

$$i_2 = 1 + 1/3 = 4/3, \quad i_C = \frac{9}{8} \cdot \frac{4}{3} = 3/2$$

$$V_1 = \frac{8}{3} \cdot i_1 + 2V_2 = \frac{8}{3} \cdot \frac{5}{2} + 4/3 = \frac{48}{6} = 8. \quad \text{But } \frac{2V_2}{V_1}(1) = \frac{R}{8} = 1/8 \Rightarrow R = 1$$

---