


ENEE 610 Fall H.W. 1 Due Tu 09/10/1

Chaybam Ghabech #1


Solution:

#1

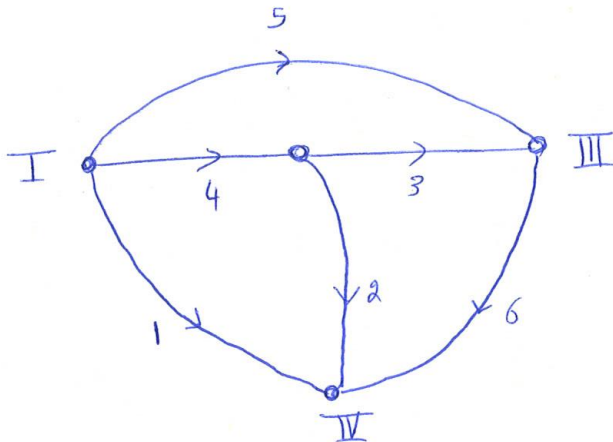a) The corresponding graph for the given circuit is:



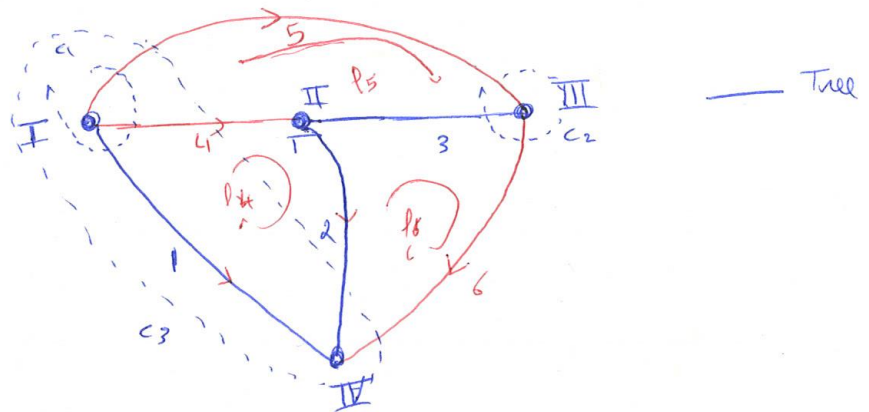b) For the cutset and tie set matrices we use the following KCL and KVLs:



KCL at cut set (1):

$$i_1 + 0i_2 + 0i_3 + i_4 + i_5 + 0i_6 = 0$$

KCL at cut set (2):

$$0i_1 + i_2 + 0i_3 - i_4 - i_5 + 0i_6 = 0$$

KCL at cut set (3):

$$0i_1 + 0i_2 + i_3 + 0i_4 + i_5 - i_6 = 0$$

Putting these in matrix format we get:

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & -1 & -1 & 1 \\ 0 & 0 & 1 & 0 & 1 & -1 \end{bmatrix} \times \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

C : cut set matrix.

Using KVLs we can obtain \uparrow set matrix:

KVL in loop 4:

$$-V_1 + V_2 + 0V_3 + V_4 + 0V_5 + 0V_6 = 0$$

$$-V_1 + V_2 + V_3 + 0V_4 + V_5 + 0V_6 = 0$$

$$0V_1 - V_2 + V_3 + 0V_4 + 0V_5 + V_6 = 0$$

Arranging the equations in matrix format we obtain;

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}$$

↑
Tree matrix

c) For the augmented incidence matrix we have:

$$A_a = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} \text{I} \\ \text{II} \\ \text{III} \\ \text{IV} \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 \\ -1 & -1 & 0 & 0 & 0 & -1 \end{bmatrix} \end{matrix}$$

If we delete last row:

$$A = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 \end{bmatrix}$$

To determine how many trees we need to calculate $\det(AA^T)$,

$$(A \times A^T) = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & -1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 \end{bmatrix} \times \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$\det(A\bar{A}) = 3(9-1) + 1(-3-1) - 1(1+3)$$
$$= 24 - 4 - 4 = 16$$

of trees this graph has is $\boxed{16}$.

Question 02

a) $e = \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$ $j = \underline{0}_6$ $G_3 = \frac{1}{R_3}$, $G_4 = \frac{1}{R_4}$, $G_6 = \frac{1}{R_6}$

Equations:
 $v = Ls i$
 $i = C s v$

Now to find $A(s)$ and $B(s)$ such that $A(s)v = B(s)i$

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & sL_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & G_3 - 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & G_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & G_6 \end{bmatrix}}_{A(s)} v = \underbrace{\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & sL_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}}_{B(s)} i$$

$$\begin{aligned} v_b &= v + e \\ v &= v_b - e \\ v &= C^T v_b - e \end{aligned}$$

$$\begin{aligned} i_b &= i + j \\ i &= i_b - j \\ i &= J^T i_b - j \end{aligned}$$

b) $A(s)v = B(s)i \rightarrow A(s)[C^T v_b - e] = B(s)[J^T i_b - j]$
 $\Rightarrow [A C^T \quad -B J^T] \begin{bmatrix} v_b \\ i_b \end{bmatrix} = A e - B j$

$$A e = \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad B j = \underline{0}_6 \Rightarrow A e - B j = \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \rightarrow \textcircled{A}$$

Now we need to find Ae^T and Bj^T

$$Ae^T = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & sL_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & G_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & G_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & G_6 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \\ 1 & -1 & 1 \\ 0 & 1 & -1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & sL_2 & 0 \\ 0 & 0 & G_3 \\ G_4 & -G_4 & 0 \\ 1 & -1 & 1 \\ 0 & G_6 & -G_6 \end{bmatrix} \rightarrow \textcircled{B}$$

$$Bj^T = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & sL_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} -1 & -1 & 0 \\ 1 & 1 & -1 \\ 0 & -1 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 1 & 1 & -1 \\ 0 & -1 & 1 \\ 1 & 0 & 0 \\ 0 & sL_5 & 0 \\ 0 & 0 & 1 \end{bmatrix} \rightarrow \textcircled{C}$$

Circuit equations are then obtained using \textcircled{A} , \textcircled{B} and \textcircled{C}

$$\begin{bmatrix} Ae^T & -Bj^T \end{bmatrix} \begin{bmatrix} v_t \\ i_t \end{bmatrix} = Ae - Bj$$

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & sL_2 & 0 & -1 & -1 & 1 \\ 0 & 0 & G_3 & 0 & 1 & -1 \\ G_4 & -G_4 & 0 & -1 & 0 & 0 \\ 1 & -1 & 1 & 0 & -sL_5 & 0 \\ 0 & G_6 & -G_6 & 0 & 0 & -1 \end{bmatrix}}_{Ae^T} \underbrace{\begin{bmatrix} v_{1t} \\ v_{2t} \\ v_{3t} \\ i_{4t} \\ i_{5t} \\ i_{6t} \end{bmatrix}}_{-Bj^T} = \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$