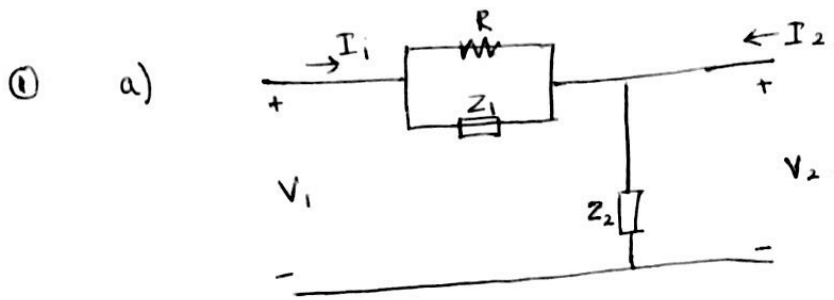


Imiya karunathilake.



$$V_1 = i_1 \left(\frac{RZ_1}{R+Z_1} \right) + (i_1 + i_2)Z_2 \quad - (1)$$

$$V_2 = (i_1 + i_2)Z_2 \quad - (2)$$

$$\therefore \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{RZ_1}{R+Z_1} + Z_2 & Z_2 \\ Z_2 & Z_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\therefore Z_{2 \text{ port}} = \begin{bmatrix} \frac{RZ_1}{R+Z_1} + Z_2 & Z_2 \\ Z_2 & Z_2 \end{bmatrix}$$

b) $R_{\text{load}} = R$

$\therefore -V_2 = i_2 R$

② \Rightarrow $V_2 = (i_1 + i_2)Z_2$
 $\therefore -i_2 R = (i_1 + i_2)Z_2$
 $\therefore Z_2 i_1 = -i_2 (R + Z_2)$

$$Z_{\text{in}} = \frac{V_1}{i_1} = \frac{-\frac{i_2}{Z_2} \left(\frac{RZ_1}{R+Z_1} \right) (R+Z_2) - i_2 R}{-i_2 \frac{(R+Z_2)}{Z_2}}$$

$$= \frac{R^2 Z_1 + RZ_1 Z_2 + R^2 Z_2 + RZ_1 Z_2}{(R+Z_2)(R+Z_1)} = \frac{RZ_1}{R+Z_1} + \frac{RZ_2}{R+Z_2}$$

c). $Z_{in} = R$ when $\frac{Z_1}{R} = \frac{R}{Z_2}$.

$$Z_{in} = \frac{RZ_1}{R+Z_1} + \frac{RZ_2}{R+Z_2} = R.$$

$$RZ_1 + Z_1Z_2 + RZ_2 + Z_1Z_2 = R^2 + RZ_2 + RZ_1 + Z_1Z_2.$$

$$R^2 = Z_1Z_2.$$

d) $\frac{V_2}{V_1} = \frac{-i_2 R}{-\frac{i_2}{Z_2} \left(\frac{RZ_1}{R+Z_1} \right) (R+Z_2) - i_2 R} = \frac{1}{\frac{Z_1}{Z_2} \left(\frac{R+Z_2}{R+Z_1} \right) + 1}$


$$= \frac{RZ_2 + Z_1Z_2}{RZ_1 + Z_1Z_2 + RZ_2 + Z_1Z_2} = \frac{RZ_2 + R^2}{RZ_1 + 2R^2 + RZ_2} = \frac{R+Z_2}{Z_1+Z_2+2R}.$$

$$\left[Z_1 = \frac{R^2}{Z_2} \right] \therefore \frac{V_2}{V_1} = \frac{R + Z_2}{\frac{R^2}{Z_2} + Z_2 + 2R} = \frac{Z_2(R+Z_2)}{R^2 + Z_2^2 + 2RZ_2}$$

$$= \frac{Z_2}{R+Z_2}$$

when $Z_2 = LS$ $\frac{V_2}{V_1} = \frac{LS}{R+LS} = \frac{S}{S + R/L}$.

b circuit

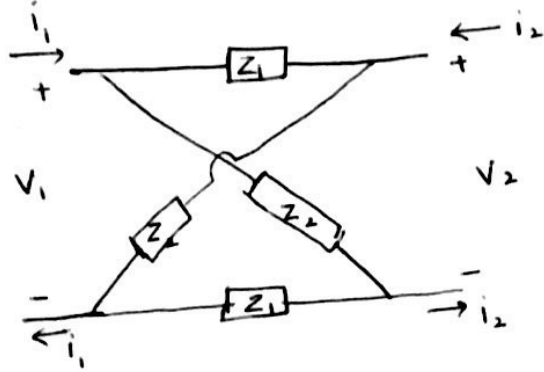

$$Z_{11} = \frac{V_1}{I_1} \Big|_{i_2=0} = \frac{Z_1 + Z_2}{2} = Z_{22}$$

$$Z_{12} = Z_{21} = \frac{V_1}{I_2} \Big|_{i_1=0} = \frac{Z_2 - Z_1}{2}$$

$$\therefore \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{Z_1 + Z_2}{2} & \frac{Z_2 - Z_1}{2} \\ \frac{Z_2 - Z_1}{2} & \frac{Z_1 + Z_2}{2} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\therefore Z_{2 \text{ port}} = \begin{bmatrix} \frac{Z_1 + Z_2}{2} & \frac{Z_2 - Z_1}{2} \\ \frac{Z_2 - Z_1}{2} & \frac{Z_1 + Z_2}{2} \end{bmatrix}$$

$$V_2 = \left(\frac{Z_2 - Z_1}{2}\right) i_1 + \left(\frac{Z_1 + Z_2}{2}\right) i_2 = -i_2 R$$

$$(Z_2 - Z_1) i_1 = -i_2 (Z_1 + Z_2 + 2R)$$

(b) $R_{\text{load}} = R$
 $\Rightarrow V_2 = -i_2 R$

$$Z_{\text{in}} = \frac{V_1}{i_1} = \frac{i_1 \left(\frac{Z_1 + Z_2}{2}\right) + \left(\frac{Z_2 - Z_1}{2}\right) \left[\frac{-(Z_2 - Z_1)}{Z_1 + Z_2 + 2R}\right] i_1}{i_1}$$

$$= \frac{Z_1 + Z_2}{2} - \frac{(Z_2 - Z_1)^2}{(Z_1 + Z_2 + 2R)^2} = \frac{(Z_1 + Z_2)^2 + 2RZ_1 + 2RZ_2 - (Z_2 - Z_1)^2}{(Z_1 + Z_2 + 2R)^2}$$

$$= \frac{4Z_1Z_2 + 2R(Z_1 + Z_2)}{(Z_1 + Z_2 + 2R)^2} = \frac{R(Z_1 + Z_2) + 2Z_1Z_2}{Z_1 + Z_2 + 2R}$$

$$(c) \quad Z_{in} = R \quad \text{when} \quad \frac{Z_1}{R} = \frac{R}{Z_2} .$$

$$Z_{in} = \frac{R(Z_1 + Z_2) + 2Z_1 Z_2}{Z_1 + Z_2 + 2R} = R \quad \Rightarrow \quad Z_1 Z_2 = R^2 .$$

$$(d) \quad \frac{V_2}{V_1} = \frac{-i_2 R}{\left(\frac{Z_1 + Z_2}{2}\right)} \left\{ \frac{-i}{\left(-i_2 \frac{(Z_1 + Z_2 + 2R)}{Z_2 - Z_1}\right)} + i_2 \left(\frac{Z_2 - Z_1}{2}\right) \right\}$$

$$= \frac{2R(Z_2 - Z_1)}{(Z_1 + Z_2)^2 + (Z_1 + Z_2)2R - (Z_2 - Z_1)^2} = \frac{2R(Z_2 - Z_1)}{4Z_1 Z_2 + 2R(Z_1 + Z_2)}$$

$$= \frac{R\left(Z_2 - \frac{R^2}{Z_2}\right)}{2R^2 + 2R\left(Z_2 + \frac{R^2}{Z_2}\right)} = \frac{Z_2^2 - R^2}{Z_2^2 + R^2 + 2RZ_2} = \frac{Z_2 - R}{Z_2 + R} .$$

$$\left[Z_1 = \frac{R^2}{Z_2} \right]$$

$$Z_2 = LS \quad \Rightarrow \quad \frac{V_2}{V_1} = \frac{LS - R}{LS + R} = \frac{s - R/L}{s + R/L} .$$