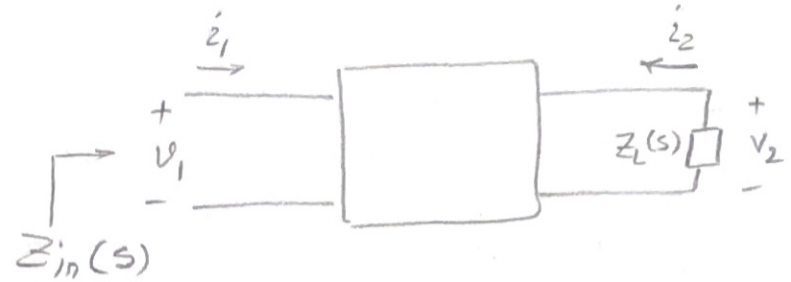


Negative Impedance Converters

a) $i_2 = k_i i_1$, $v_2 = k_v v_1$, k_i and k_v : non-zero current and voltage gain constants, load with $Z_L(s)$ and give $Z_{in}(s) = ?$

$$\begin{cases} v_1 = Z_{11} i_1 + Z_{12} i_2 \\ v_2 = Z_{21} i_1 + Z_{22} i_2 \end{cases}$$



$$Z_{in}(s) = \frac{v_1}{i_1} = ?$$


$$v_2 = -Z_L i_2 \quad (1), \quad i_2 = k_i i_1 \quad (2), \quad v_2 = k_v v_1 \quad (3)$$

Plugging (2) and (3) in (1):

$$k_v v_1 = -Z_L k_i i_1 \rightarrow \frac{v_1}{i_1} = - \frac{k_i Z_L}{k_v}$$

Negative impedance converter

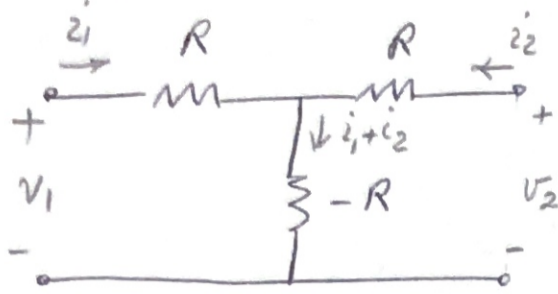b) R : positive #, Find Y, Z, S, Z_{in} when loaded with Z_L .



Finding Z :

$$\begin{cases} v_1 = Z_{11} i_1 + Z_{12} i_2 \\ v_2 = Z_{21} i_1 + Z_{22} i_2 \end{cases}, Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

KVL equations: $\begin{cases} -v_1 + R i_1 - R(i_1 + i_2) = 0 \rightarrow v_1 = -R i_2 \\ -v_2 + R i_2 - R(i_1 + i_2) = 0 \rightarrow v_2 = -R i_1 \end{cases} \rightarrow Z = \begin{bmatrix} 0 & -R \\ -R & 0 \end{bmatrix}$

Finding Y : (method 1)

$$Y = Z^{-1} \quad \det(Z) = 0 - (R^2) = -R^2 \rightarrow Y = \frac{1}{\det(Z)} \begin{bmatrix} 0 & R \\ R & 0 \end{bmatrix}$$

$$\rightarrow Y = \begin{bmatrix} 0 & -1/R \\ -1/R & 0 \end{bmatrix}$$

(Method 1)

From above KVL equations:

$$\begin{cases} i_2 = -\frac{1}{R} v_1 \\ i_1 = -\frac{1}{R} v_2 \end{cases}, \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \rightarrow Y = \begin{bmatrix} 0 & -1/R \\ -1/R & 0 \end{bmatrix}$$

Finding S:

$$\begin{cases} 2V^i = V + Ri \\ 2V^r = V - Ri \end{cases}, \quad V^r = S V^i, \quad S: \text{Scattering Matrix}$$

$$S = (BR^{-1} + A)^{-1} (BR^{-1} - A), \quad A(S)V = B(S)i$$


$$\text{For } R = 1_n: \quad S = \textcircled{1} (Z + 1_n)^{-1} (Z - 1_n) \quad \text{or } S = \textcircled{2} (1_n + \gamma)^{-1} (1_n - \gamma)$$

$$\text{Using } \textcircled{1} \text{ and } Z = \begin{bmatrix} 0 & -R \\ -R & 0 \end{bmatrix}:$$

$$\begin{aligned} S &= \left(\begin{bmatrix} 0 & -R \\ -R & 0 \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \right)^{-1} \left(\begin{bmatrix} 0 & -R \\ -R & 0 \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \right) \\ &= \begin{bmatrix} 1 & -R \\ -R & 1 \end{bmatrix}^{-1} \begin{bmatrix} -1 & -R \\ -R & -1 \end{bmatrix} = \frac{1}{1-R^2} \begin{bmatrix} 1 & R \\ R & 1 \end{bmatrix} \begin{bmatrix} -1 & -R \\ -R & -1 \end{bmatrix} = \frac{1}{R^2-1} \begin{bmatrix} 1+R^2 & 2R^2 \\ 2R^2 & 1+R^2 \end{bmatrix} \end{aligned}$$

Finding Z_{in} when loaded with Z_L :

$$Z_{in} = \frac{V_1}{i_1}$$

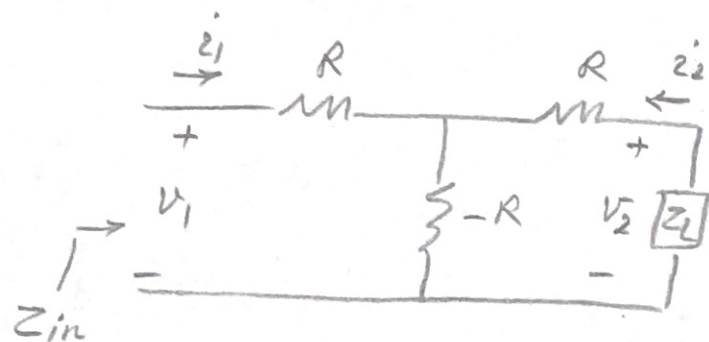

$$\text{KVL: } \begin{cases} -V_1 + Ri_1 - R(i_1 + i_2) = 0 & \textcircled{1} \\ -V_2 + Ri_2 - R(i_1 + i_2) = 0 & \textcircled{2} \end{cases} \quad \text{and } V_2 = -Z_L i_2 \quad \textcircled{3}$$

$$\textcircled{2}, \textcircled{3} \rightarrow Z_L i_2 + Ri_2 - R(i_1 + i_2) = 0 \rightarrow Z_L i_2 = Ri_1 \rightarrow i_2 = \frac{R}{Z_L} i_1 \quad \textcircled{4}$$

$$\textcircled{1}, \textcircled{4} \rightarrow -V_1 - Ri_2 = 0 \rightarrow -V_1 - R \left(\frac{R}{Z_L} \right) i_1 = 0 \rightarrow$$

$$Z_{in} = \frac{V_1}{i_1} = - \frac{R^2}{Z_L}$$

c) Loaded with Z_L and $R=1$ ($K_i = K_v$), find S for Z_{in} and compare with that of Z_L ($n=1$).


From part a)

$$Z_{in} = -\frac{K_i}{K_v} Z_L \xrightarrow{K_i = K_v} \boxed{Z_{in} = -Z_L}$$

From part b)

$$Z_{in} = -\frac{R^2}{Z_L} \xrightarrow{R=1} \boxed{Z_{in} = -\frac{1}{Z_L}}$$

1-port circuit:

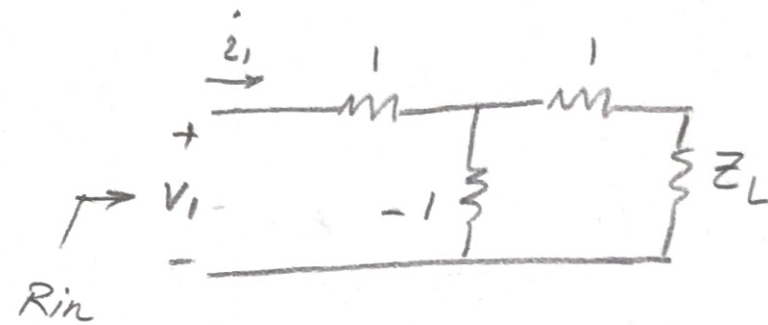

$$R_{in} = 1 + (-1 \parallel (1 + Z_L))$$

$$\rightarrow R_{in} = 1 + \frac{-(1 + Z_L)}{Z_L} = \frac{Z_L - 1 - Z_L}{Z_L} = \frac{-1}{Z_L} = Z$$

$$S = (Z + 1)^{-1} (Z - 1) = \left(\frac{-1}{Z_L} + 1\right)^{-1} \left(\frac{-1}{Z_L} - 1\right) = \left(\frac{Z_L - 1}{Z_L}\right)^{-1} \left(\frac{-1 - Z_L}{Z_L}\right)$$

$$= \left(\frac{Z_L}{Z_L - 1}\right) \left(\frac{-1 - Z_L}{Z_L}\right) = \frac{1 + Z_L}{1 - Z_L}$$