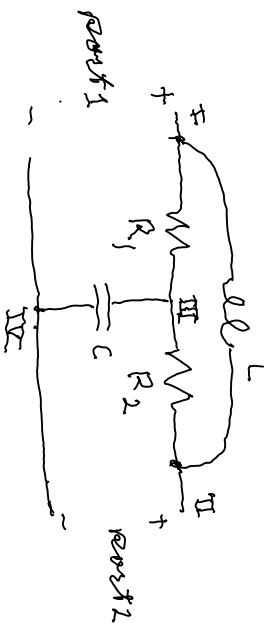


ENEE 610 Fall 2019 Homework 2 Due Tu 09/17/19

#1 (50 points; indefinite admittance matrix )

For the following circuit

- a) Give the indefinite admittance.
- b) Ground node IV to get the nodal admittance matrix.
- c) Eliminate the internal node III to get the 2-port admittance matrix.



#2 (50 points, gyrator L-C equivalents)

For the following circuits

- By adding admittance matrices on the left circuit and inverting the sum of impedance matrices on the right circuit find the 2-port admittance descriptions of each of the two 2-ports shown below.
- These two admittance matrices will be equal if L and  $g_2$  are chosen in terms of C and  $g_1$ . Give those choices.
- Load the left hand circuit's 2nd port in a resistor of conductance G and calculate the input admittance,  $y_{in}(s)$ , looking into its first port. Give the poles and zeroes of  $y_{in}(s)$ .

