
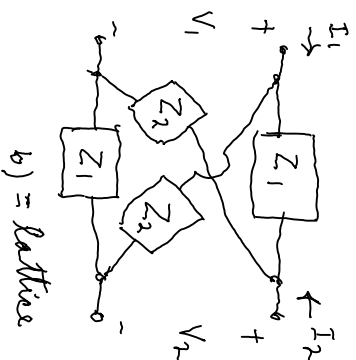


ENEE 610 Fall 2019 Homework 3 Due Tu 09/24/19

#1 (50 points; constant R circuits)

For the following circuits

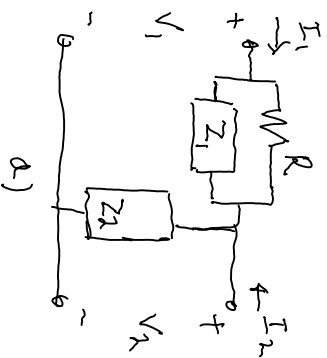- a) Give the 2-port impedance matrices.
- b) Load port 2 in a resistor of resistance $R_{load} = R$ and find the input impedance Z_{in} .
- c) Calculate the element values such that $Z_{in} = R$ when $Z_1/R = R/Z_2$
- d) With those element values give V_2/V_1 for each R-loaded 2-port and evaluate for an inductive $Z_2 = Ls$




#2 (50 points, bridge T circuit).


Choose $C_1=1/(2a)$, $C_2=2a/b$, $L_1=a/b$ and $L_2=(1/2)[(1/a)-(a/b)]$ with $a=2$ and $b=1$, in which case the mutual $L_2 < 0$

Also the coupled coils equivalent of circuit a) is used for the bridge T of circuit b).


- Give $L_{11}=L_{22}$ and $L_{21}=L_{12}=M$ in terms of L_1 and L_2 .
- By finding the impedance matrix for the non- C_1 portion and then adding admittance matrices obtain the 2-port admittance of the bridge T.
- Load in a resistor of G Mho conductance and calculate $V_2/V_1(s)$: give its zeroes and poles under open circuit load conditions ($G=0$).
- When loaded in the G Mho resistor calculate the input admittance, $Y_{in}(s)$, looking into its first port.

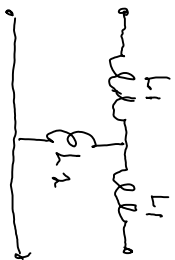

a)

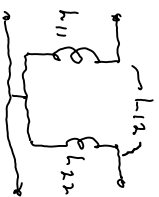
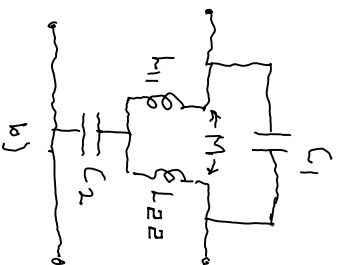
$$Z_{CE}(s) = \mathcal{L} \begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix}$$



b)