
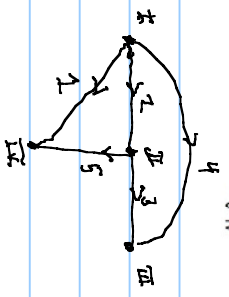


The final report is a term paper based upon the study of your base paper topic. The electronic journal is a collection of than required things you have done for the course, such as computer runs, notes on reading of non-assigned papers, etc., to show me what you have done in the course beyond the required homework and term paper.

network = connection of circuits  
 electronic devices = R, L, C, controlled sources (E, F, G, H), gyrators, op-amps, transistors, switches, transformers, coupled coils, diodes, vacuum tubes, transmission lines, motors, etc.  
 Graph: points (=nodes=vertices=>n)  
 lines (=branches=edges=>b)  
 trees=>t, cotrees=links=>l forest=>f  
 Limit to finite circuits; project on a plane  
 =>graphs in the plane = 2-simplex

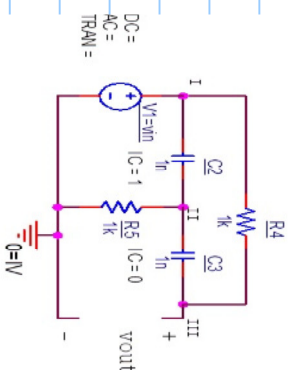

$$\text{Incident} = \begin{pmatrix} 1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & -1 & -1 & 0 \\ -1 & 0 & 0 & 0 & -1 \end{pmatrix}$$


$$\text{Ircdcd} = \begin{pmatrix} 1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & -1 & -1 & 0 \end{pmatrix}$$



$$\text{Ircdcd}^T = \begin{pmatrix} 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & -1 \\ 0 & 1 & 0 \end{pmatrix}$$

$$D = \text{Ircdcd} \cdot \text{Ircdcd}^T$$

$$D = \begin{pmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 2 \end{pmatrix}$$

$$|D| = 8$$

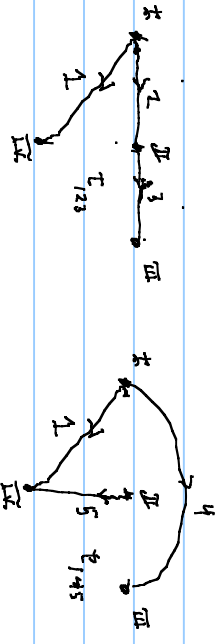

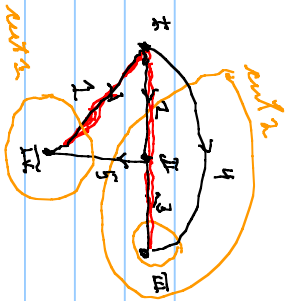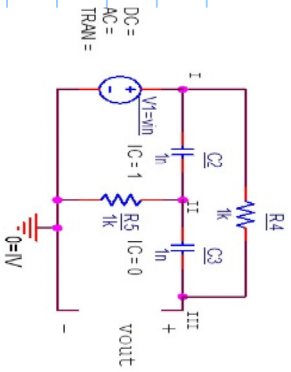


KCI

- 1  $0 = i_1 + 0 \cdot i_2 + 0 \cdot i_3 + 0 \cdot i_4 + i_5$
- 2  $0 = 0 \cdot i_1 + 1 \cdot i_2 + 0 \cdot i_3 + 1 \cdot i_4 - i_5$
- 3  $0 = 0 \cdot i_1 + 0 \cdot i_2 + 1 \cdot i_3 + 1 \cdot i_4 + 0 \cdot i_5$

cut 2 eqn,  $i_4 = i_3$
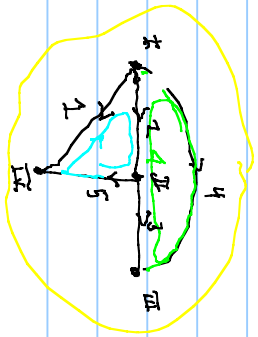
$$Q_b = E \cdot i_b, \quad E = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & -1 \\ 0 & 0 & 1 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} \quad t \times b$$



KVL

$$4 \quad 0 = 0 \cdot v_1 - 1 \cdot v_2 + 1 \cdot v_3 + 1 \cdot v_4 + 0 \cdot v_5$$

$$5 \quad 0 = -v_1 + v_2 + v_3 + 0 \cdot v_4 + 1 \cdot v_5$$

cut 2 eqn.  $i_4 = i_3$

$$Q_R = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 \end{bmatrix} v_b = -k^T i_b + 1 \cdot i_5 \quad t \times b$$

$$= Q_R^T \cdot v_b = [-k^T i_b + 1 \cdot i_5]$$

$v_b \cdot i_b = \text{power in a branch}$   
 $v_b^T \cdot i_b = 0 = [v_1 \ v_2 \ v_3 \ v_4 \ v_5] \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \text{total power in the circuit from outside.}$

$$b = t + \rho$$

$$v_b = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}, \quad i_b = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

$$0 = [1 \ 1 \ 1 \ 1 \ 1] \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} \Rightarrow -i_2 = k i_3 \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = i_b = \begin{bmatrix} 0 & -k \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_3 \\ i_4 \end{bmatrix} = Q^T i_R = i_b'$$

$$v_R = k^T v_b \Rightarrow v_R = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ k & 1 \end{bmatrix} v_b' \Rightarrow v_R = E^T v_b'$$

$$v_b'^T i_b' = (E^T v_b')^T (Q^T i_R) = v_b'^T (E Q^T) i_R = 0 \quad (\text{a matter})$$

$E Q^T = \begin{bmatrix} 1 & 1 & 1 \\ k & 1 & 1 \end{bmatrix}^T$   $Q_{t \times R}$  (a matrix)  $i_R$  (a vector)  
 Thus as a circuit exists for every entry since  $v_b'$  &  $i_R$  are independent by choice

$$= -k^T + k = -k + k = 0_{t \times R}$$

