
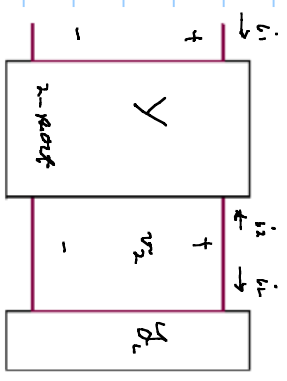


Still base papers to choose
Today: loaded 2-port via Y's
Z, Yout/Min and S matrices, passivity

Homework 2
Van der Pol oscillator

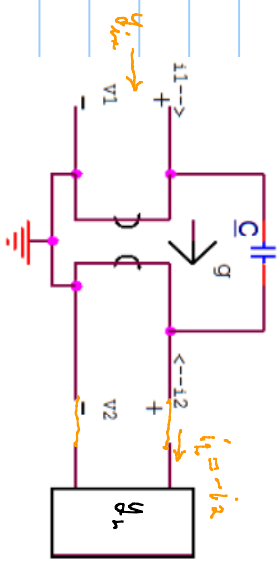

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}, \quad i_L = -i_2 = y_L v_2$$

$$i_2 = -y_L v_2 = y_{21} v_1 + y_{22} v_2 \implies v_2 = \frac{-y_{21} v_1}{y_L + y_{22}}$$

$$i_1 = y_{11} v_1 + (-y_{21} \frac{y_{21} v_1}{y_L + y_{22}})$$

$$y_{in} = \frac{i_1}{v_1} = \frac{y_{11} y_L + y_{12} y_{21} - y_{21}^2}{y_{22} + y_L}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} AC & -AC-g \\ -AC+g & AC \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_1 \\ -i_L \end{bmatrix}$$

del Youtmate

$$= (AC)(AC-g) - (-AC+g)(-AC+g)$$

$$= (AC)^2 - (-AC)^2 + ACg - ACg + g^2 = g^2$$

del how

$$-i_2 = i_L = y_L v_2$$

$$\implies \text{load how } (-AC+g)v_1 + ACv_2 = -y_L v_2$$

$$(-AC-y_L)v_2 = (-AC+g)v_1$$

$$v_2 = \frac{-AC+g}{-AC-y_L} \cdot v_1$$

$$i_1 = ACv_1 + (-AC-g) \left[\frac{-AC+g}{-AC-y_L} \right] v_1$$

$$y = \frac{i_1}{v_1} = AC + \frac{(AC+g)(g-AC)}{AC+y_L}$$

$$= \frac{(AC)^2 + ACg - AC^2 - ACg}{AC+y_L}$$

$$= \frac{ACg_L + g^2}{AC+y_L}$$



$$Y = \begin{bmatrix} gC & -ACg \\ -ACg & AC \end{bmatrix} \Rightarrow i = Yv, v = Zi, Z = Y^{-1} = \frac{1}{\det Y} \begin{bmatrix} AC & AC+g \\ AC-g & AC \end{bmatrix} = \frac{1}{g^2} \begin{bmatrix} AC & AC+g \\ AC-g & AC \end{bmatrix}$$

$$v_1 = \frac{AC}{g} i_1 + (AC - \frac{1}{g}) i_2$$

$$v_2 = \frac{AC}{g} i_1 + g i_2 + AC i_2$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \frac{AC}{g} & AC - \frac{1}{g} \\ \frac{AC}{g} & AC + g \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} A_1 & A_2 \\ A_3 & A_4 \end{bmatrix}, \quad Z = C/g^2$$



$$g = 10^{-3}$$

$$C = 10^{-9}$$

$$L = \frac{10^{-9}}{10^{-6}} = 10^{-3} = 1 \text{ mH}$$

$$Q_2 = C i_2 = [A_2 \ K] i_2$$

$$= [0_2 \ Q_{2R}] v_2$$

$$\begin{bmatrix} 0_2 & Q_{2R} \\ -K^T & A_2 \end{bmatrix} v_2 = \begin{bmatrix} A_2 & K \\ Q_{2R} & A_2 \end{bmatrix} i_2$$

KCL & KVL
As $v_2 = B_2 i_2$



$a =$ connecting

connecting wires for the branch components
 $A v_2 = B i_2, i_2, v_2$

$$Q_2 = g v_2 = [-K^T \ A_2] i_2$$

$$= [Q_{2L} \ Q_{2R}] i_2$$

deriving:

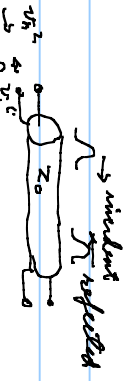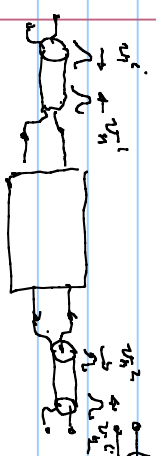

$$e = Z v^i = v^i + Z_0 i^i$$

$$Z v^N = v^N - Z_0 i^i$$


$$v^N = S v^i, \quad v^N = e - Z_0 i^i$$

$$S v^i = e - Z_0 i^i$$

choose $Z_0 = 1$ by normalizing

$$S = \text{scattering matrix}$$
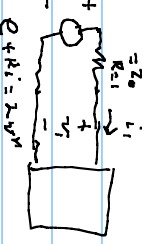
$$\begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} = \begin{bmatrix} v_1^N \\ v_2^N \end{bmatrix} = \begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix}$$




$$v^N = e - Z_0 i^i$$

$$e + R_0 i^i = Z_0 v^N$$

$A v = B i \Leftrightarrow$ if there are port variables then a Y exists or $A = Y, B = 1$ mem
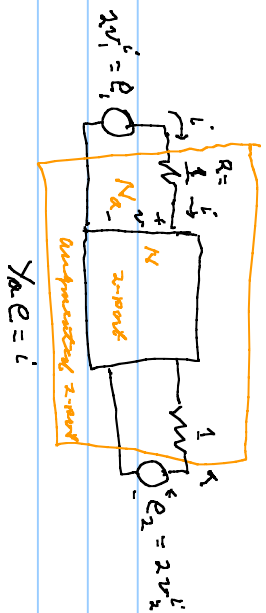
$$\text{th } Z \text{ (" " } A = I_{\text{port}}, B = Z$$



$$Y_a e = i$$

$$Y_a v = Y_a (I_1 - Y_a) e = (I_1 - Y_a) Y_a e = (I_1 - Y_a) i$$

$$\Rightarrow Y_a v = (I_1 - Y_a) i \Rightarrow A = Y_a, B = (I_1 - Y_a) \text{ für } N_a$$

$$\text{Bout } \left. \begin{aligned} v &= v^i + v^o \\ i &= v^i - v^o \end{aligned} \right\} \begin{aligned} A(v^i + v^o) &= B(v^i - v^o) \\ \Rightarrow (A+B)v^o &= (B-A)v^i \end{aligned}$$

$$\Rightarrow S = (B+A)^{-1}(B-A) = (I_1 - Y_a)^{-1} (I_1 - 2Y_a)$$

$$\begin{aligned} e &= v + i = 2v^i & 2v^o &= v - i \\ i &= Y_a e & &= (e - i) - Y_a e \Rightarrow v^o = S v^i \\ v &= e - i & &= e - Y_a e - Y_a e \\ &= e - 2Y_a e & &= (I_1 - 2Y_a) e \end{aligned}$$