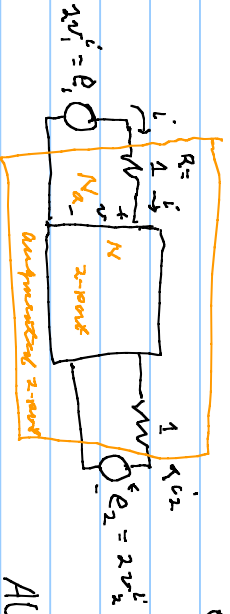


Homework 2

S matrix properties, examples, ODE realizations by Cs and Gvalues



$$e = 2v^i = v + i$$

$$2v^o = v - i$$

$$v^o = v^i + v^o$$

$$i^o = v^i - v^o$$

$$v^o = S v^i$$

$$A v = B i \text{ for } N$$

$$A(v^i + v^o) = B(v^i - v^o)$$

$$(A - B)v^i = -(A + B)v^o$$

$$v^o = (A + B)^{-1} (A - B)v^i$$

$$S = (B + A)^{-1} (A - B)$$

$$e = v + i = v^o$$

$$i = Y_a e$$

$$v = e - i$$

$$= e - Y_a e$$

$$= (I_2 - Y_a) e$$

$$(I_2 - Y_a) i = (I_2 - Y_a) Y_a e = Y_a (I_2 - Y_a) e \Rightarrow Y_a v = (I_2 - Y_a) i$$

$$S = (I_2 - Y_a + Y_a)^{-1} (I_2 - 2Y_a) \text{ for } m\text{-ports } S = I_m - 2Y_a$$

$$S = (B + A)^{-1} (A - B) = (I_m + B^{-1}A)^{-1} B^{-1} B (I_m - B^{-1}A) = (I_m + Y)^{-1} (I_m - Y)$$


$$B^{-1}A \Rightarrow Av = Bv \Rightarrow B^{-1}Av = v = Yv$$

$$Y = B^{-1}A$$

$$S = I_m - 2Y = (I_m + Y)^{-1} (I_m - Y) = (Z + I_m)^{-1} (Z - I_m)$$

Ex: $\sum C \quad y_c = RC, \quad S(s) = (1+RCs)^{-1} (1-RC) = \frac{1-RC}{1+RC}$

$S(j\omega) = \frac{1-j\omega C}{1+j\omega C} \quad ; \quad |S(j\omega)| = \frac{\sqrt{1+(C\omega)^2}}{\sqrt{1+(C\omega)^2}} = 1$

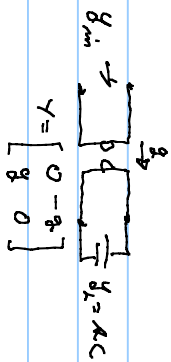

$y = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} \quad y_{in}(s) = \frac{y_{11}G_L + \Delta Y}{G_{in} + Y_L} = \frac{0 + g^2}{RC} = \frac{1}{RC} = \frac{1}{R} \cdot \frac{1}{C} = \frac{1}{RL}$

$\Rightarrow \equiv \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \frac{g^2}{C}$



$i_1 = -g_1 v_2 \quad -i_2 = -g_2 v_2$
 $g_1 v_2 = i_3 = g_1 v_1 \quad i_2 = g_2 v_2 = g_2 \left(\frac{-i_1}{g_1} \right)$

$v_2 = T v_1$
 $i_1 = -T i_2$


$PC(s) = (v_1^T i_1 + v_2^T i_2) = v_1^T [-T] i_2 + (T v_1^T) i_2 = 0$ *cancel in terms*

ODE in circuit


$\ddot{x} + \epsilon(x^2 - 1)\dot{x} + \omega_0^2 x = 0, \quad x(0), \dot{x}(0)$ van der Pol oscillator

$\dot{x} = y$
 $y' = -\epsilon(x^2 - 1)y - \omega_0^2 x$ } state variables equations

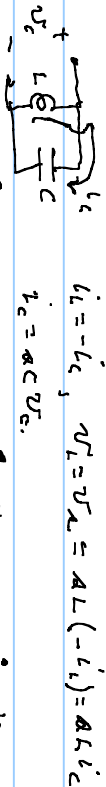$\epsilon = 0$ this is like an LC parallel circuit



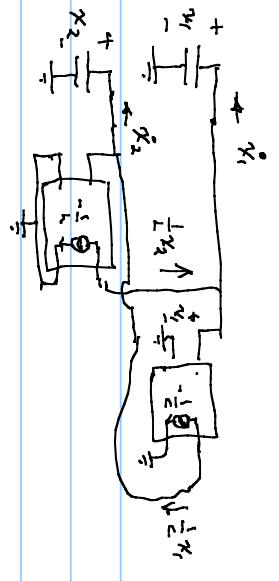$i_c = -i_L, \quad v_L = v_C = AL(-i_c) = AL i_c$
 $L i_c = C v_C \Rightarrow i_c' = \frac{1}{L} v_C, \quad v_C' = \frac{1}{C} i_c$
 $i_c' = \frac{1}{L} v_C, \quad v_C' = \frac{1}{C} i_c$



-