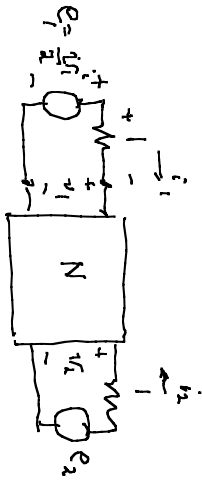


Homework 3

VLSI tutorial  
Good topic paper: Optimal area allocation for resistors and capacitors in continuous-time monolithic filters, H. Fei, R. L. Geige and D. Chen, ISCAS proceedings, 2004, p. 1-865-1-868

Existence of S for passive circuits, L2 functions, Circulator, multiplication of Ss: companion matrix forms, Bilateral Laplace transform



$\Rightarrow$  if  $R$  is passive & we apply  $k_1, k_2$  then  $S(s)$  exists

$S(s)$  is rational in  $s$  & then  $S(s)$  exists as  $S(s)$   $\omega = \omega_j$

$S(s)$  is bounded real if rational all coefficients are real

Other examples are Z only for a ideal transformer.

But nullators are passive but not  $S(s)$ .




$V = 0$   
 $I = 0$   $P(t) \equiv 0$

$V^N = S(s) V^i$   
 $2V^i = V + I$   
 $2V^N = V - I$


if passive  $N$  apply  $N^T(s)$   
 $P(s) = \int_{-\infty}^{\infty} v^T(i(t)) v^i(t) dt$  is square integrable  
if  $\int_{-\infty}^{\infty} v^T(i(t)) v^i(t) dt$  is finite  $L_2$   
when  $\omega \rightarrow \omega_j$   
 $\int_{-\infty}^{\infty} v^T(i(t)) v^i(t) dt = \int_{-\infty}^{\infty} v^T(\omega) v(\omega) + \int_{-\infty}^{\infty} v^T(\omega) i(\omega) + 2 v^T(\omega) i(\omega)$   
non-negative of passive

Circulator, 3 port

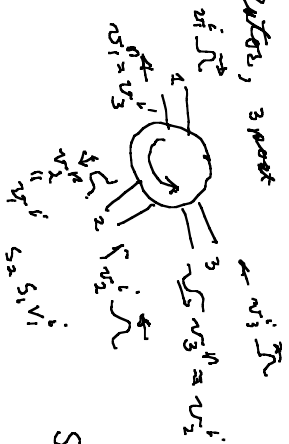

$$S = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix} \Rightarrow V^N = S V^i = \begin{bmatrix} v_2^i \\ v_3^i \\ v_1^i \end{bmatrix}$$
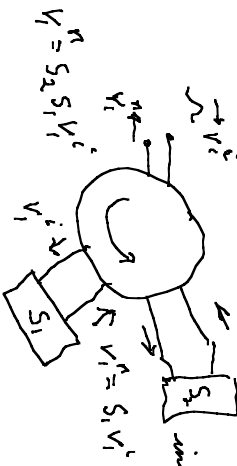
$$S(-\alpha) S(\alpha) = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = I_3$$



useful for synthesis  
 $S_{11} = S_{22} = 0$   
 $S_{12} = S_{21} = 1$   
 $S_{11}$  in BR ←  $\alpha$   $\frac{1-\alpha}{1+\alpha}$   
 if  $S_1$  &  $S_2$  are

Ex:  $S_{in}(\alpha) = \begin{pmatrix} \frac{1-c_1\alpha}{1+c_1\alpha} & 0 \\ 0 & \frac{1-c_2\alpha}{1+c_2\alpha} \end{pmatrix}$



choose  $S_1(\alpha) = \frac{1-c_1\alpha}{1+c_1\alpha} \Rightarrow \frac{1}{2} c_1$   
 $S_2 = \frac{1-c_2\alpha}{1+c_2\alpha} \Rightarrow \frac{1}{2} c_2$   
 $y = c = \alpha$   
 $S_{in} = \frac{1-\alpha}{1+\alpha}$


$\alpha = \sigma + j\omega$ , use in the full complex plane, takes out singularities  
 $\alpha = \text{diagonal transform matrix}$ , needs  $\alpha$  region of convergence of  $S_1$  in  $\text{Re } \alpha > -1/c_1$   
 $\alpha = d/dt$  operator, needs operator domain of functions

$a: \text{in } e^{at}$       $b: \frac{1-cx}{1+x} = \frac{1}{x} \Rightarrow (1-cx)^x = (1+cx)^x$   
 $v - \frac{d}{dx} v^x = v^x + c \frac{d}{dx} v^x \Rightarrow \frac{d}{dx} v^x = v^x \ln v$       $v^x = v^x e^{x \ln v}$       $v^x = v^x e^{x \ln v}$   
 $v^x - c v^x (x \ln v) = v^x e^{x \ln v} + c v^x (x \ln v) e^{x \ln v}$   
 $(1-cx) v^x = (1+cx) v^x$       $\text{then } v = e^{cx}$


$\mathcal{L}\{f(t)\} = \int_{-\infty}^{\infty} f(t) e^{-st} dt$       $\mathcal{L}\{1(t)\} = \int_0^{\infty} 1 e^{-st} dt = \frac{1}{s}$  if  $t > 0$   
 $\mathcal{L}\{1(t)\} = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$  if  $t > 0$   
 $\mathcal{L}\{1(t)\} = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$  if  $t > 0$

Bilateral Laplace transform  
 $\mathcal{L}\{f(t)\} = \int_{-\infty}^{\infty} f(t) e^{-st} dt$       $\mathcal{L}\{1(t)\} = \frac{1}{s}$  if  $t > 0$   
 $\mathcal{L}\{1(t)\} = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$  if  $t > 0$   
 $\mathcal{L}\{1(t)\} = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$  if  $t > 0$

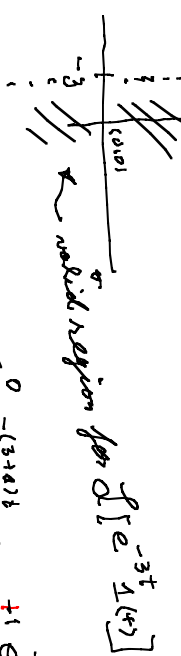Bilateral Laplace transform  
 $\mathcal{L}\{f(t)\} = \int_{-\infty}^{\infty} f(t) e^{-st} dt$       $\mathcal{L}\{1(t)\} = \frac{1}{s}$  if  $t > 0$   
 $\mathcal{L}\{1(t)\} = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$  if  $t > 0$   
 $\mathcal{L}\{1(t)\} = \int_0^{\infty} e^{-st} dt = \frac{1}{s}$  if  $t > 0$



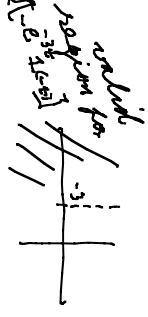$\mathcal{L}\{e^{-3t} 1(t)\} = \int_0^{\infty} e^{-3t} e^{-st} dt = \int_0^{\infty} e^{-(s+3)t} dt = \frac{1}{s+3}$  if  $\text{Re}(s+3) > 0$   
 $\mathcal{L}\{e^{-3t} 1(t)\} = \frac{1}{s+3}$  if  $\text{Re}(s) > -3$   
 $\mathcal{L}\{e^{-3t} 1(t)\} = \frac{1}{s+3}$  if  $\text{Re}(s) > -3$



$\therefore$  Given  $F(s)$  need to know the region of convergence to find  $f(t)$  for  $F(s) = \mathcal{L}\{f(t)\}$

ODE via state comparison matrix

$$\frac{Y_{out}(s)}{Y_{in}} = \frac{1}{As + d + \frac{d_{s-1}}{s-1} + \dots + d_1 s + d_0}$$

$s = \text{degree}$

$$V_{out} = v_0$$

$$V_{in}(s) = (a^s + d_{s-1} a^{s-1} + \dots + d_1 a + d_0) v_0(s)$$

$$\dot{x}_1 = v_0 = x_2$$

$$\dot{x}_2 = x_3$$

$$\dots \quad \dot{x}_{s-1} = x_s$$

$$\text{but } As + v_0 = \overset{\dots \dots \dots}{x_1 \dots \dots \dots} + v_1 \dots \dots \dots - (d_{s-1} x_s \dots \dots \dots)$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \vdots \\ \dot{x}_s \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 \\ 0 & 0 & 1 & \dots & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & \dots & 1 \\ -d_s & -d_{s-1} & \dots & \dots & -d_{s-1} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_s \end{bmatrix} + \begin{bmatrix} d \\ \vdots \\ d \\ 1 \end{bmatrix} v_{in}$$

$$v_0 = [1, 0, \dots, 0]$$

state eq. for  $\frac{v_0}{v_{in}} = \frac{1}{D(s)}$   
 polynomial

allow design via OTA, C, A.

