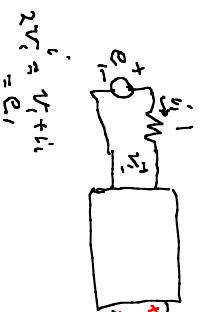


$$2V_2^N = V_2 - i_2 = 2V_2$$



$V_2 = 0$ if only load resistor

$$S_{21} = \frac{V_2^N}{V_1^i} \Big|_{V_2=0} = \frac{V_2}{V_1} = 2 \frac{V_2}{V_1}$$

$$\begin{bmatrix} v_1^i \\ v_2^o \end{bmatrix} = \begin{bmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{bmatrix} \begin{bmatrix} v_1^i \\ v_2^o \end{bmatrix} = 0$$

Normalizations, impedance level & the frequency/time scale

$$Z_m(\omega) = \frac{Z(\omega)}{R} \Rightarrow Z_L(\omega) = aL, \quad Z_C(\omega) = \frac{a}{R} = Z_L(\omega) \Rightarrow h_m = \frac{1}{R}$$

$$Z_C(\omega) = \frac{1}{aC} \Rightarrow \frac{Z_C}{R} = \frac{1}{RC\omega} = C_m = RC, \quad R \rightarrow \frac{R}{R} = \text{normalized}$$

$Z(\omega) = \frac{N(\omega)}{D(\omega)}$; Rest $\omega = \omega_m$, $\rho = \text{normalized frequency}$

$$Z_m(\omega_m) = \frac{N(\omega_m)}{D(\omega_m)} = \frac{N_m(\omega)}{D_m(\omega)} \Rightarrow Z_C(\omega) = \frac{1}{aC} = \frac{1}{\omega_m RC} = \frac{1}{\rho C_m} \Rightarrow Z_m(\omega) = C_m \omega_m C$$

\Rightarrow under R & R scaling $R_m = R/R$, $C_m = R\omega_m C$, $h_m = \omega_m h/R$

ideal op-amp



$v_1 = 0$
 $v_2 = 0$ as a virtual ground (= a tie)
 $i_2 = i_0$ for
 $v_2 = \dots$ independent of i_2


$$\begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} v = \begin{bmatrix} 1 & \Delta \\ 0 & 0 \end{bmatrix} i$$



nodes

More
Practical

(nonlinear)

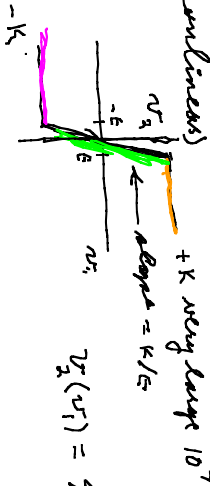

$$v_2(v_1) = \dots$$

$$\begin{cases} K \frac{1}{\epsilon} (v_1 - \epsilon) \\ -K \frac{1}{\epsilon} (-\epsilon - v_1) \\ \frac{K}{\epsilon} v_1 (1 - (v_1 - \epsilon)) \cdot 1 - (v_1 + \epsilon) \end{cases}$$

"
" when
-v1 + epsilon > 0
=> v1

low loss: mainly $\epsilon, \epsilon', \epsilon''$, gyration & transformers

$$\text{Dk: } \mathcal{E}(\omega) = 0 = \int_{-\infty}^{\infty} \frac{v^T i' + \epsilon^T v}{2} dt = \int_{-\infty}^{\infty} \frac{V^T(i(\omega)I(\omega) + I^T(\omega)V(\omega))}{2} d\omega = 0$$

$$= \int_{-\infty}^{\infty} V^T(i(\omega)I(\omega) + I^T(\omega)V(\omega)) d\omega$$

$$= \int_{-\infty}^{\infty} V^T(i(\omega)I(\omega) + I^T(\omega)V(\omega)) d\omega$$

* = complex conjugate
 $\int_{-j}^{j} = \int_j^{-j}$

low loss

If rational $S_C(j\omega) = S(-j\omega)$ and $S_C(s) = S_C(j\omega) \Rightarrow S(-j\omega) = S(-s)$
 with real coefficients

By Parseval's theorem

Parseval's theorem
 Parseval $\Rightarrow S_C^T(j\omega) S_C(j\omega) = I_m \Rightarrow$
 (Parseval) $= S_C^T(j\omega) S_C(j\omega)$

$\Rightarrow \omega = \omega_j \Rightarrow S_C^T(-s) S_C(s) = I_m$ if lossless

$S_C(s) = S_C^T(-s)$ lossless or passive or lossless

$A = \omega_j \Rightarrow A = \sigma + j\omega$
 if $\sigma = 0, A = j\omega$

Ex: $\int_C C, Y(s) = CA$
 $S(s) = (1+Y)(1-Y) \Rightarrow S(-s) = \frac{1-(1-rc)}{1+(1-rc)} = \frac{1+rc}{1-rc} = \frac{1}{S(s)}$
 if $C \geq 0$ $rc \geq 0 \Rightarrow a = -rc$

Given a lossless admittance
 $S_C(s) = 0 \Rightarrow \frac{Y_C(j\omega) + Y_C^T(-s)}{2} = 0_m \Rightarrow Y_C(s) + Y_C^T(-s) = 0_m, m = \# \text{ ports}$

Ex: $\int_L Y(s) = \frac{1}{sL},$ or $s \text{ pole } a = 0, Y_C(s) = \frac{1}{sL}, Y_C(-s) = \frac{1}{-sL} + \frac{1}{sL} = 0$
 for lossless $Y_C(s) = -Y_C^T(-s)$ Ex: \int_C $Y = \begin{bmatrix} 0 & g \\ g & 0 \end{bmatrix}, Y^T = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} = -Y$
 Ex: \int_C $Y = \begin{bmatrix} 0 & g \\ g & 0 \end{bmatrix}, Y^T = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} = -Y$
 lossless


if poles $Y(s)$ is positive real, if rational it is called PR
 if under ZPR it is called LPR
 passive \Rightarrow no poles in $\sigma > 0$ $Y(s) = -Y(-s)$ if LPR

$$n=1 \quad Y(s) = -Y(-s), \quad Y(s) = \frac{N(s)}{D(s)}$$

\uparrow polynomial
 same for $N(s)$ or there
 poles are poles of $Z(s)$

The process need no analytic continuation

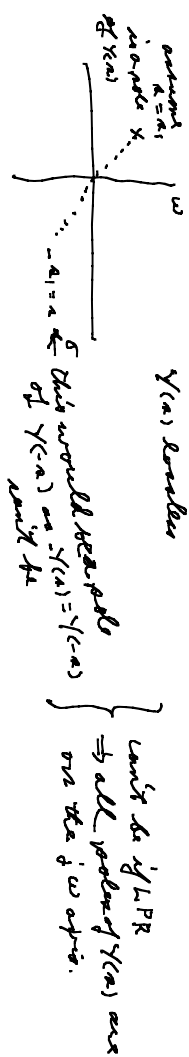from $k = \delta \omega$ to $k = \sigma + j\omega$



$$Y(s) = \frac{N_m s^m + N_{m-1} s^{m-1} + \dots + N_1 s + N_0}{D_g s^g + d_{g-1} s^{g-1} + \dots + d_1 s + d_0} = \frac{A^{N_m} (s^2 + \sigma_1^2)^{N_{m1}} \dots (s^2 + \sigma_{m-1}^2)^{N_{m,m-1}}}{A^{N_g} (s^2 + \sigma_1^2)^{N_{g1}} \dots (s^2 + \sigma_{g-1}^2)^{N_{g,g-1}}}$$

\Rightarrow only 1st order are allowed due to being PR
 then make a partial fraction design from it