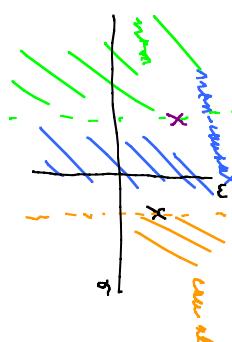


Paper requirements, etc.  
 Causal vs non-causal=anti-causal  
 Richards' function via S & section for  
 synthesis

Ladders for zeros of transmission  
 Constant R circuits & Vol(s)/V(i(s) design  
 $\exp(-At)$   
 op-amp curve tracer  
 Chain matrix




An interesting paper:  
 Emil Cauer, Wolfgang Mathis, and Rainer Pauli, "Life and Work of Wilhelm Cauer (1900 – 1945),"  
 Proceedings of the MTNS2000, Perpignan, France, June 19 – 23, 2000, 10 pages.

A good paper for ladder synthesis:  
 Alexander J. Casson \* and Esther Rodriguez-Villegas, "A Review and Modern Approach to LC Ladder Synthesis."

Richards' function  $R_y(s)$  for  $y(s)$  [ $R_y$  is PR if  $y$  is PR when  $k>0$ ; and  $s^2-k^2$  cancels to give  $\delta[R]=\delta[y]-1$  if  $k$  is a zero of  $E[y(s)]$ , that is  $E[y(k)=(y(k)+y(-k))/2=0$ ; physically  $y_L$  is a load admittance. The result extends to complex  $k$  for  $Rk>0$  and a similar Richards' function is useful for impedances and  $Y$ :


$$\begin{aligned}
 R_k &= \frac{\text{Re}[y(s)]}{\text{Im}[y(s)]} \left[ \frac{1 - \frac{A}{k} \cdot \frac{y(s)}{y(-s)}}{\frac{y(s)}{y(-s)} - \frac{A}{k}} \right]; \quad S_{R_k} = (B+A)(B-A), \quad Y(s) \Rightarrow L = Y \omega \Rightarrow B = \omega \Rightarrow B_A \omega = i; \quad Y = BA \\
 &= (1 + \delta A)^{-1} B (1 - B^{-1} A) \\
 &= (1 - R_k)/(1 + R_k) = \left( 1 - \left( 1 - \frac{A}{k} \cdot \frac{y(s)}{y(-s)} \right) \left( \frac{y(s)}{y(-s)} - \frac{A}{k} \right) \right) = \frac{\frac{y(s)}{y(-s)} - \frac{A}{k} - 1 + \frac{A}{k} \cdot \frac{y(s)}{y(-s)}}{\frac{y(s)}{y(-s)} - \frac{A}{k} + 1 - \frac{A}{k} \cdot \frac{y(s)}{y(-s)}} \\
 &= \frac{\frac{A}{k} \left( -1 + \frac{y(s)}{y(-s)} \right) + \left( -1 + \frac{y(s)}{y(-s)} \right)}{\frac{A}{k} \left( 1 - \frac{y(s)}{y(-s)} \right) + \left( 1 + \frac{y(s)}{y(-s)} \right)} = \frac{(A+k) \left( -1 + \frac{y(s)}{y(-s)} \right)}{(k-a) \left( 1 + \frac{y(s)}{y(-s)} \right)}. \quad \text{or zero & pole cancel } (-A+k) \text{ disappears & other terms in } BR = S_{R_k}
 \end{aligned}$$

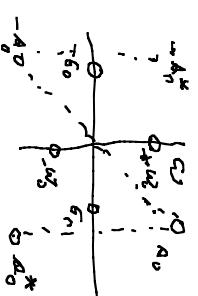zeros of  $E_{\text{tr}}[y_{\text{rec}}]$  =  $\frac{y_{\text{rec}} + y_{\text{err}}}{2}$




any real axis point is a zero for  $E_{\text{tr}}[y_{\text{rec}}]$  if  $y_{\text{rec}}$  is LPR

Blind Y(s) LPR

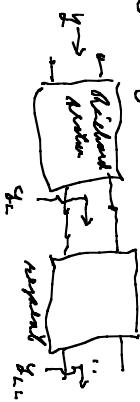

ends after  $\delta[y_L]$  terms gives an  $\infty$  number of possible results

1st power poles @  $\omega = .2$

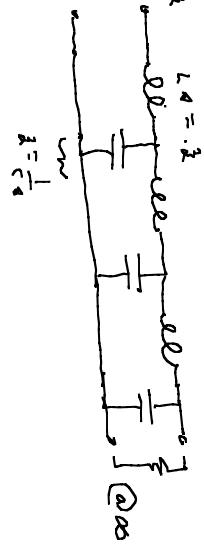

no auto. 0  
then transmission  
zeros @  $\infty$ .

$$\frac{V_0}{V_i} = \frac{kr}{k^2 + 1 + do} \rightarrow \text{charact of load with } R$$

Design for 2-port terminated in a resistor

$$+ \frac{V_1}{V_2} = \frac{V_2(4s)}{V_1(4s)}$$



$$V_2 = \frac{V_2(4s)}{V_1(4s)} V_1 \Rightarrow A_{21} = \frac{V_2}{V_1} = \frac{-G_{21}}{G_1 + G_{22}}$$

$$A_{21} = \frac{V_2}{V_1} = \frac{-G_{21}}{G_1 + G_{22}} \text{ normalize } G_L = 1 = 1/R_L$$

$$-G_{12} V_2 = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow -G_{12} V_2 = V_{21} V_1 + V_{22} V_2$$

$$A_{2r} = \frac{V_2}{V_1} = \frac{-g_{21}}{1 + g_{21}}, \quad g_{21} \text{ LPR} \quad g_{21} = \frac{m_{22}}{d_{22}}, \quad g_{21} =$$

$$= \frac{-g_{21}}{1 + m_{22}/d_{22}} = \frac{-g_{21} \cdot d_{22}}{m_{22} + d_{22}}$$

$$\approx \frac{g_{21}}{(a^4 + 5a^3 + 4) + (3a^3 + 9a)}$$


form from  $A_{2r} = \frac{N}{D} \approx \frac{N}{2r[1] + D[1, 0]}$

$$= \frac{N/(D[1, 0])}{1 + \frac{g_{21}[1, 0]}{D[1, 0]}} = \frac{-g_{21}}{1 + g_{21}[1, 0]}$$

$$-g_{21} = N/(3a^3 + 9a)$$

Symmetrizing  $g_{21}$  by 1st corner (as all 4 zeros of transmission are at  $\infty$ )
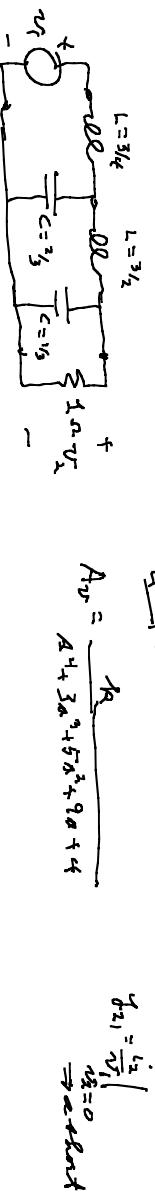
$$g_{21} : \frac{\frac{1}{3}a}{\frac{3a^3 + 9a}{a^4 + 3a^3 + 4}} \left[ \frac{\frac{3}{2}a}{\frac{3a^3 + 9a}{2a^2 + 4}} \right] \left[ \frac{\frac{3}{2}a}{\frac{3a^3 + 9a}{3a^2 + 6a}} \right] \left[ \frac{\frac{2}{3}a}{\frac{2a^2 + 4}{3a^2 + 4}} \right] \left[ \frac{\frac{3}{4}a}{\frac{3a}{4}} \right]$$



$$A_{2r} = \frac{T_R}{A^4 + 3a^3 + 5a^2 + 9a + 4}$$

$$g_{21} = \frac{L_{21}}{R_{21}} \quad R_{21} = 0$$

→ evident

$$\text{to find } R_{21}, \quad A_{2r}(0) = \frac{T_R}{4} \Rightarrow \frac{V_2}{V_1} = \frac{V_1}{V_1 - (R_{21}=0)} \quad A_{2r}(0) = 1 = -\frac{T_R}{4} \Rightarrow T_R = 4$$

$$A_{2r} = \frac{4}{a^4 + 3a^3 + 5a^2 + 9a + 4}; \quad g_{21} = \frac{-4}{3a^2 + 9a}$$

$$S[A_{2r}] = 4 \quad S[R_{21}] = 3$$

