

Choice of denominator for Y22

Curve tracing theory
Curve tracing op-amp circuit
Partial pole removal
Constant R lattice


$$\begin{aligned} \frac{Y_3}{V_1} &\approx -\frac{Y_{21}}{1 + Y_{22}} = \frac{Kc}{A^4 + A^3 + 10A^2 + 4A + 9} = \frac{Kc}{1 + \frac{A(A^3 + 4A)}{A^2 + 9}} \\ &= \frac{Kc / (A^3 + 4A)}{1 + \frac{A(A^3 + 4A)}{A^2 + 9}} \end{aligned}$$

$$Y_{22a} = \frac{A^4 + 10A^2 + 9}{A^3 + 4A}$$

$$Y_{22ab} \approx \frac{A^3 + 4A}{A^4 + 10A^2 + 9}$$



Y22a no degree-3
not used for Y3/V1

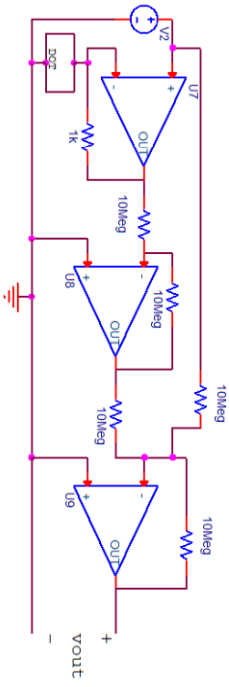


$$V_2 = \frac{K(A^2+2)}{A^4 + A^3 + 10A^2 + 4A + 9}$$

pole 2 @ ∞
2 poles on jw axis

check y_{22}
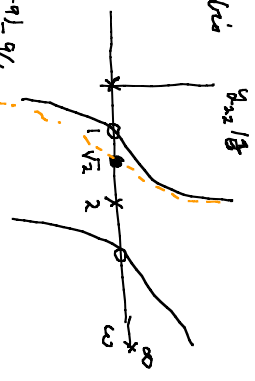
$$= \frac{A^4 + 10A^2 + 9}{A^3 + 4A} = \frac{(A^2+1)(A^2+9)}{A(A^2+4)}$$



$$y_{22} = \frac{K_0}{A} + K_{20}A + \frac{2K_{21}A}{A^2+4}$$

$K_{20} = 1$ $K_{21} = \frac{A^2+4}{A^2+4} = 1$

$K_{20} = 1$ $K_{21} = \frac{A^2+4}{A^2+4} = 1$

$$= \frac{9/4 + A + \frac{15A}{A^2+4}}$$

$$\left(\frac{9/4 + A + \frac{15A}{A^2+4}}{A^2+4} \right) = 0 \Rightarrow \left(\frac{9/4 + A + \frac{15A}{A^2+4}}{A^2+4} - \frac{15A}{A^2+4} \right) = 0$$



$$\Rightarrow \frac{9/4 + A}{A^2+4} = 0 \Rightarrow 9/4 + A = 0 \Rightarrow A = -9/4$$

derive for pull out $\frac{7/2 A}{A^2+4} = y_1$

$$y_2 = y_{22} - \frac{7/2 A}{A^2+4}$$


$$= \frac{9/4 + A + \frac{15A}{A^2+4}}{A^2+4} - \frac{7/2 A}{A^2+4}$$
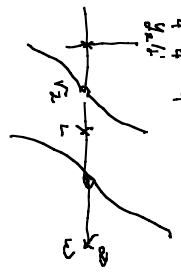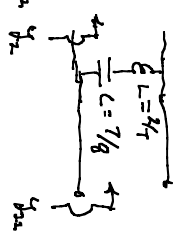
$$= \frac{9/4 + A + \frac{15A}{A^2+4} - \frac{7/2 A}{A^2+4}}{A^2+4} = \frac{9/4 + A + \frac{13A}{A^2+4}}{A^2+4}$$



$$\Rightarrow \frac{9/4 + A}{A^2+4} = 0 \Rightarrow 9/4 + A = 0 \Rightarrow A = -9/4$$
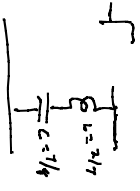
$$\Rightarrow \frac{9/4 + A}{A^2+4} = 0 \Rightarrow 9/4 + A = 0 \Rightarrow A = -9/4$$



$$g_2 = \frac{1}{g_2} = \frac{1}{\frac{1}{4}(\alpha^2 + 4)}$$

$$= \frac{\alpha^3 + 4\alpha}{\alpha^4 + 4\alpha^2 + 4} = \frac{\alpha^3 + 4\alpha}{(\alpha^2 + 2)^2}$$

$$\frac{\alpha^2 + 2}{\alpha^4 + 4\alpha^2 + 4}$$


$$\frac{\alpha^4 + 2\alpha^2}{18\alpha^2 + 9}$$

$$g_2 = \frac{\alpha^3 + 4\alpha}{(\alpha^2 + 2)}$$

$$= \frac{(\alpha^3 + 4\alpha)}{(\alpha^2 + 2)} = \frac{2K\alpha^2}{\alpha^2 + 2} + \frac{2K\alpha}{\alpha^2 + 2}$$


Remember the roots @ $\alpha^2 = -2$ which gives the 0 of transmission ($\alpha^2 + 2$) and when it's cancel for the other two
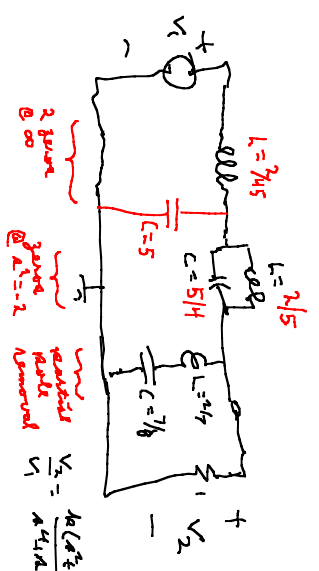
$$= \frac{4\alpha}{\alpha^2 + 2} + \frac{2\alpha}{\alpha^2 + 2}$$



Note: more reactive elements
 $6 > 5 \Rightarrow [v_2/v_1] = 4$

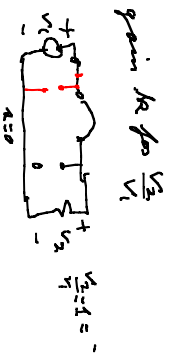
$$\frac{V_2}{V_1} = \frac{K(\alpha^2 + 2)}{\alpha^4 + 2\alpha^2 + 4}$$



gain K for V_2/V_1

$$K = \frac{2K}{9} = 1 \Rightarrow K = \frac{9}{2}$$

Curve Tracing

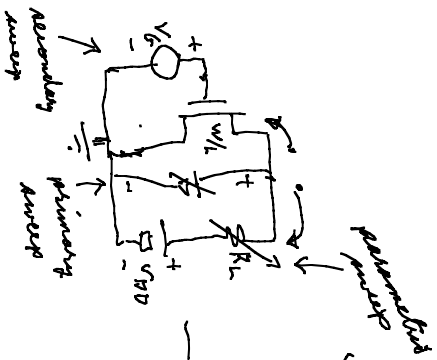

Ohm Transistor

