

schedule presentations; final exam  
poles of z<sub>ij</sub>  
lattice vs bridge tee & Constant R examp  
OTA circuit

exp(-A1) and delta\_x(0)  
sensitivity  
adjoint

$$V2/V1(s) = [1 - (z_a/R)^2] / [1 + 2(z_a/R) + (z_a/R)^2] = \frac{[1 - (z_a/R)] [1 + (z_a/R)]}{[1 + (z_a/R)]^2} = \frac{[1 - (z_a/R)]}{[1 + (z_a/R)]}$$

$$R^2 = z_a z_b \Leftrightarrow G^2 = y_a y_b \quad G = 1/R$$



$$Z = \frac{1}{\frac{1}{z_a} + \frac{1}{z_b}} = \frac{z_a z_b}{z_a + z_b}$$


$$Y = \frac{1}{Z} = \frac{z_a + z_b}{z_a z_b} = \frac{1}{z_a} \begin{bmatrix} z_a + z_b & z_b - z_a \\ z_a - z_b & z_a + z_b \end{bmatrix}$$

bridge tee.

$$Y = y_1 \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} + \frac{1}{Z} \begin{bmatrix} z_a + z_b & z_b - z_a \\ z_a - z_b & z_a + z_b \end{bmatrix}$$

$$y_{11} = \frac{1}{Z} (g_b + g_a)$$

$$y_{21} = \frac{1}{Z} (g_b - g_a)$$

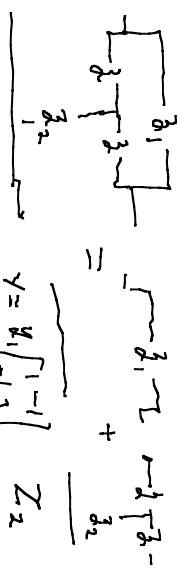

$$Z_2 = \frac{z_1 z_2}{z_1 + z_2}$$

$$Y = y_1 \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} + \frac{1}{Z_2} \begin{bmatrix} z_1 + z_2 & z_2 - z_1 \\ z_2 - z_1 & z_1 + z_2 \end{bmatrix}$$

$$y_{11} = \frac{1}{Z_2} + \frac{z_1 + z_2}{z_1 z_2} = \frac{z_1 + z_2}{z_1 z_2} + \frac{z_1 + z_2}{z_1 z_2} = \frac{2(z_1 + z_2)}{z_1 z_2}$$

$$y_{21} = \frac{z_2 - z_1}{z_1 z_2} + \frac{z_2 - z_1}{z_1 z_2} = \frac{2(z_2 - z_1)}{z_1 z_2}$$

$$y_a = 2y_1 + \frac{2+2\beta_2}{\beta_1(\beta_1+2\beta_2)} = 2y_1 + \frac{1}{\beta_1} \Rightarrow \left[ \begin{array}{c} 1 \\ 2 \\ \beta_1 \end{array} \right] \left[ \begin{array}{c} 1 \\ 2 \\ \beta_1 \end{array} \right] y_1$$

∴ given bridge we can get a lattice  
if  $\beta_1 = 1/y_1$ ,  $\beta_2 = \beta_1$  are PR both circuits are passive

Other constant R,  $\det \beta = R^2 = \beta_{12}\beta_{21}$  }  $G = 1/R$


$$\det Y = \frac{1}{\det Z} = \frac{1}{G^2} = \frac{1}{y_a} \cdot \frac{1}{y_b} \Rightarrow G^2 = y_a y_b$$

$$G^2 = \frac{y_1 \beta_1 (\beta_1 + \beta_2) + \beta_2 y_2 (\beta_1 + 2\beta_2) + 1}{\beta_1 (\beta_1 + 2\beta_2) \beta_2 (\beta_1 + 2\beta_2)}$$

$$\text{if } y_a y_b = G^2 \Rightarrow G^2 \beta_1^2 + 2G^2 \beta_1 \beta_2 = 1 + 2y_1 \beta_1 \beta_2 \Rightarrow \beta_1^2 + (2\beta_2 - 2y_1/G^2) - 1/G^2 = 0 \Rightarrow \text{given } \beta$$


$$\beta = (\beta_2 - y_1/G^2) \pm \frac{1}{2} \sqrt{4(\beta_2 - y_1/G^2)^2 + 4G^2} \quad \text{if } y_1/G^2 = \beta_2 = \frac{1}{y_2} \Rightarrow G^2 = y_1 y_2$$
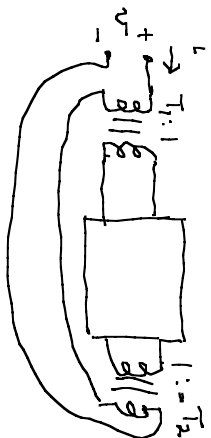
$$\text{then } \beta = 0 \pm G \Rightarrow \beta = G \text{ if passive, } G > 0$$



To obtain lattice of  $\beta_{12}$  &  $\beta_{21}$  in  $\beta_{11}$  &  $\beta_{22}$  if passive
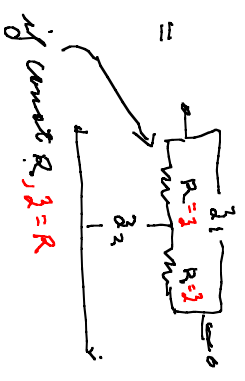
$$\begin{aligned} \frac{V_2}{V_1} &= [T_1 \ T_2] \begin{bmatrix} \beta_{11} & \beta_{12} \\ \beta_{21} & \beta_{22} \end{bmatrix} \begin{bmatrix} T_1 \\ T_2 \end{bmatrix} \\ &= T_1^2 \beta_{11} + (\beta_{12} + \beta_{21}) T_1 T_2 + \beta_{22} T_2^2 \end{aligned}$$



$$y_a = 2y_1 + \frac{1}{2}y_2$$

$$y_b = 2y_2 + y_3$$

if  $\text{const } R_1, R_2 = R$

$$\dot{x} = Ax + Bu$$

$$y = Cx + Du$$

if  $u = v$  then the transfer function is an admittance  
 if  $u = v$  then the transfer function is an admittance  
 input output  
 $x = \text{capacitor voltage}$   
 $C \rightarrow 1, R_1, R_2 = R$   
 dimensions of state  
 $\frac{dy}{dt} = y \Rightarrow \text{capacitor current}$

$$\begin{bmatrix} \dot{x} \\ y \end{bmatrix} = \begin{bmatrix} A \\ C \end{bmatrix} \begin{bmatrix} x \\ u \end{bmatrix}$$

↑  
states

↑  
voltage

$$\Rightarrow Y_C = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

admittance values  
 make with OTR

if  $u=0$  then  $\dot{x} = Ax$

if  $x = e^{-At} x_0$  then  $\dot{x} = \frac{d}{dt} (e^{-At} x_0)$

for a number  $e^{-At} = 1 + \frac{1}{1!} (-A)t + \frac{1}{2!} (-A)^2 t^2 + \dots = \sum_{l=0}^{\infty} \frac{1}{l!} (-A)^l t^l$

$$\Rightarrow e^{-At} = \sum_{l=0}^{\infty} \frac{1}{l!} (-A)^l t^l = \sum_{l=0}^{\infty} \frac{(-1)^l}{l!} A^l t^l$$

$$\frac{d}{dt} e^{-At} = \sum_{l=0}^{\infty} \frac{(-1)^l}{l!} A^l l t^{l-1} = \sum_{l=1}^{\infty} \frac{(-1)^l}{(l-1)!} A^l t^{l-1} = -A e^{-At}$$

state variable equations  
 can be made with OTR  
 for  $Y_C$  & capacitor for  $\dot{x}$

$$\dot{x} = Ax + \delta x_0 \quad \delta \text{ (Kilohertz) - unit impulses}$$

$\Rightarrow$  finite matrix  $(A^{-1}x_0 - A)^{-1}$  has  $k$  poles  $\Rightarrow$  finite number of poles

$$A^{-1}x_0 \delta[x] = A \delta[x] + x_0 \Rightarrow \delta[x] = (A^{-1}x_0 - A)^{-1} x_0$$

For get  $x(t)$  we invert using the poles

$$ECL: \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix} x + \delta \begin{bmatrix} x_{01} \\ x_{02} \end{bmatrix} ; \delta[x] = \left( \begin{bmatrix} A & 0 \\ 0 & A \end{bmatrix} - \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix} \right)^{-1} x_0$$


$$\begin{bmatrix} A & -1 \\ A+3 & 2 \end{bmatrix}^{-1} = \frac{1}{A(A+3)+2} \begin{bmatrix} A+3 & +1 \\ -2 & A \end{bmatrix} = \frac{1}{A^2+3A+2} \begin{bmatrix} A+3 & +1 \\ -2 & A \end{bmatrix} = \frac{1}{(A+2)(A+1)} \begin{bmatrix} A+3 & +1 \\ -2 & A \end{bmatrix}$$

$$A^2+3A+2 = \left( A + \frac{3}{2} + \frac{1}{2} \sqrt{9-8} \right) \left( A + \frac{3}{2} - \frac{1}{2} \sqrt{9-8} \right) = -\frac{3}{2} \pm \frac{1}{2} \sqrt{9-8} = -2, -1$$


$$\begin{aligned} K_{11} &= \frac{A+3}{(A+2)(A+1)} \quad K_{12} = \frac{+1}{(A+2)(A+1)} \\ K_{21} &= \frac{-2}{(A+2)(A+1)} \quad K_{22} = \frac{A}{(A+2)(A+1)} \end{aligned}$$

$$\Rightarrow \begin{bmatrix} A & -1 \\ 2 & A+3 \end{bmatrix}^{-1} = \frac{1}{A+2} \begin{bmatrix} -1 & 1 \\ 2 & 2 \end{bmatrix} + \frac{1}{A+1} \begin{bmatrix} 2 & +1 \\ -2 & -1 \end{bmatrix} \Rightarrow e^{-At} 1(t) = \left\{ \begin{bmatrix} -1 & 1 \\ 2 & 2 \end{bmatrix} e^{-2t} + \begin{bmatrix} 2 & +1 \\ -2 & -1 \end{bmatrix} e^{-t} \right\} 1(t)$$

for  $A = \sigma + j\omega, \sigma > 0$

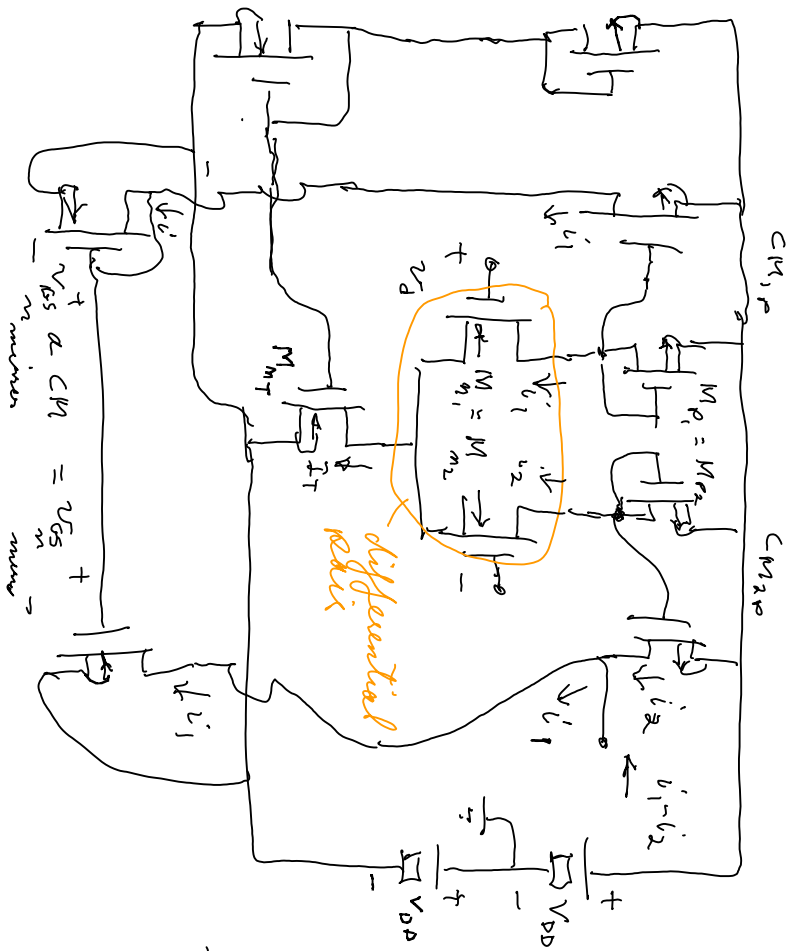

differential pair

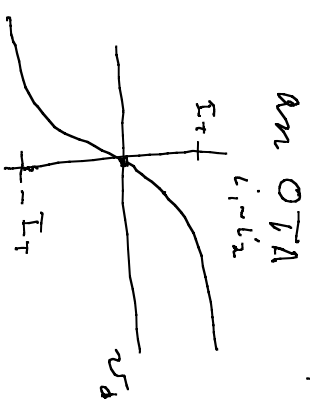

a good VLSI circuit

$$i_1 = i_2 = I_T \tanh\left(\frac{v_d}{2V_T}\right)$$

$V_T = \text{thermal voltage}$   
if  $M_{n1} \approx M_{n2} \Rightarrow$  BJT