
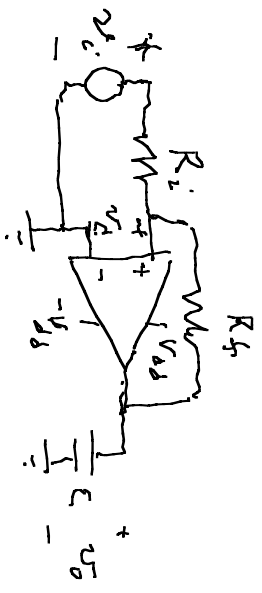




Synthesis from state equations


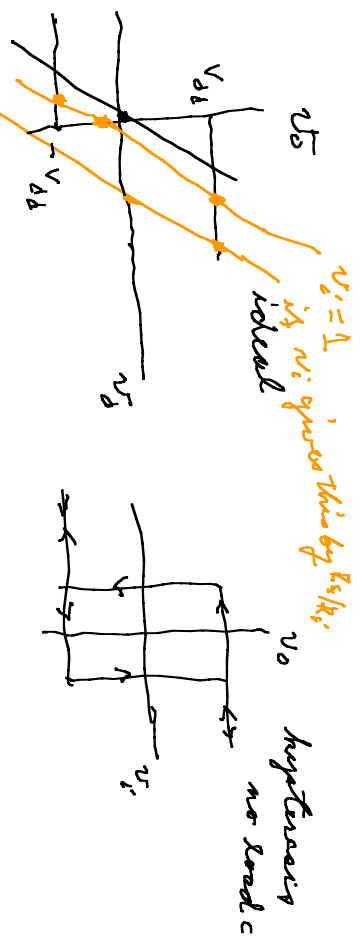


⇒



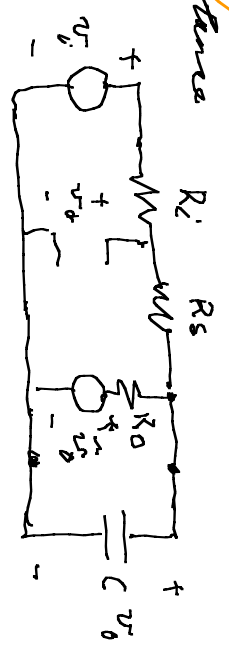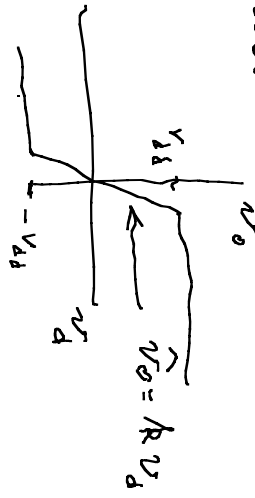practical op-amp need $R_o =$ output resistance



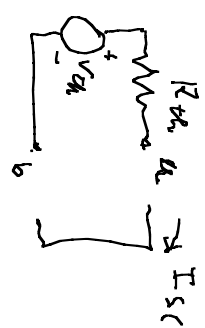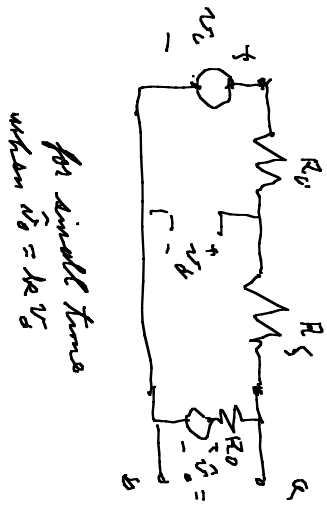


$v_{th} = v_{oc}$ *abgeschlossen*
 $R_{th} = \frac{v_{oc}}{I_{sc}}$ *unter a..b*

$$v_{oc} = \frac{g_i (R_0 + k R_3)}{(1-k) + g_i (R_0 + R_3)} v_i \sim -g_i R_3 v_i$$

$$I_{sc} = \frac{R_0 + k R_3}{R_0 (R_1 + R_2)} v_i \sim \frac{k R_3}{R_0 (R_1 + R_3)} v_i$$
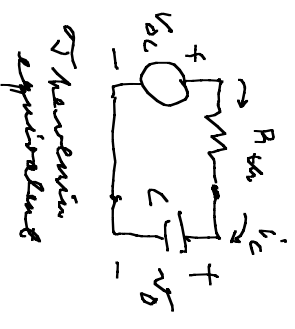
$$= \frac{R_0 (R_1 + R_3) [g_i (R_0 + k R_3)]}{(R_0 + k R_3) [(1-k) + g_i (R_0 + R_3)]} \approx \frac{-g_i R_3 (R_0 (R_1 + R_3))}{k R_3} = -R_{eq}$$



Nortonäquivalent

$$C v_0 = i_c = \frac{v_{oc} - v_0}{R_{th}} \Rightarrow C v_0 + \frac{1}{R_{th}} v_0 = \frac{1}{R_{th}} v_{oc}$$

$\Rightarrow v_0 + \frac{1}{R_{th} C} v_0 = \frac{1}{C} v_{oc}$ *after t=0 before op amp saturates*

$$v_0 - \frac{1}{R_{th} C} v_0 \approx \frac{1}{C} v_{oc} \times 1(t) \quad -\infty < t < \text{time to saturation}$$


Let find impulse response: $v_0(t) = e^{-\frac{t}{R_{th} C}} 1(t)$ *realistic* $v_0 - \frac{1}{R_{th} C} v_0 = \delta(t)$

to find $v_o(t)$ - v_{oc} applied $\Rightarrow v_o(t) = v_o(t) \times \frac{1}{1 + R_y C} v_{oc} \cdot 1(t)$


$$v_o(t) = \int_{-\infty}^{\infty} v_o(\tau) \frac{1}{1 + R_y C} v_{oc} 1(t-\tau) d\tau = \int_{-\infty}^{\infty} e^{+\frac{1}{R_y C} \tau} 1(\tau) \cdot \left(\frac{-v_{oc}}{R_y C} \right) 1(t-\tau) d\tau$$

$$= \int_0^t e^{\frac{1}{R_y C} \tau} \left(\frac{-v_{oc}}{R_y C} \right) d\tau \cdot 1(t) = \left(\frac{-v_{oc}}{R_y C} \right) \cdot \frac{1}{R_y C} \cdot e^{+\frac{1}{R_y C} \tau} \Big|_0^t \cdot 1(t) = \left(\frac{-v_{oc}}{(R_y C)^2} \right) \left[e^{+\frac{1}{R_y C} t} - 1 \right] 1(t)$$

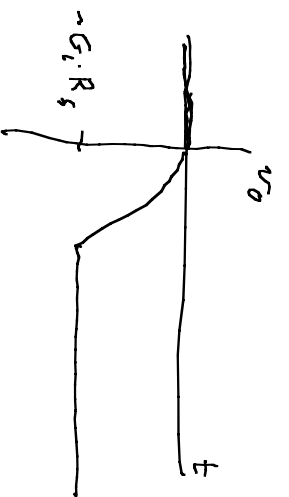8. Hence $v_o^{\infty} = v_{oc} \text{ or } -v_d$



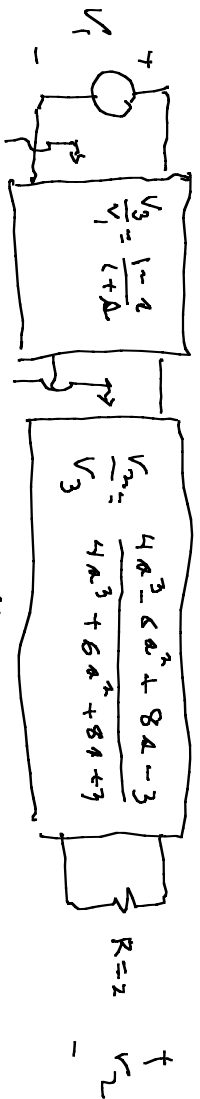Draw the circuit which is the cascade of two constant R lattices, with R=2, to give
 $V_2/V_1 = [(1-3s)(4s^3-6s^2+8s-3)] / [(1+3s)(4s^3+6s^2+8s+3)]$
 Does it matter which section comes first? Why?




$3a/2 = 3a$
 $2 = 2$

$$\frac{V_2}{V_1} = \frac{1-a}{1+a} = \frac{6a^2+7}{4a^3+8a}$$

$$\frac{V_3}{V_2} = \frac{4a^3 - 6a^2 + 8a - 3}{4a^3 + 6a^2 + 8a + 3}$$
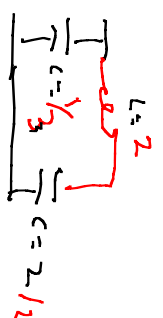
$$\frac{V_3}{V_1} = \frac{6a^2+7}{4a^3+8a} \cdot \frac{4a^3 - 6a^2 + 8a - 3}{4a^3 + 6a^2 + 8a + 3}$$



$$\frac{1-a^2}{(1+a)^2} = \frac{(1-2s)(1+s)}{(1+s)(1+s)} = \frac{1-2s}{1+s}$$