

Solutions 610 final Fall 2020

#1. $f(s) = (s^3 + 4s) / (s^4 + 7s^2 + 10)$; remove poles @ ∞ by continued fraction

$$\begin{aligned}
 & \frac{s^3 + 4s}{s^4 + 7s^2 + 10} \xrightarrow{+ 2s} \frac{1}{s} + \frac{2s}{s^4 + 7s^2 + 10} \\
 & \frac{2s}{s^4 + 7s^2 + 10} \xrightarrow{\frac{1}{3}s} \frac{1}{3s} + \frac{2s}{3s^3 + 10} \\
 & \frac{2s}{3s^3 + 10} \xrightarrow{+ 19/3} \frac{19/3}{3s} + \frac{2s}{3s^3 + 10} \\
 & \frac{2s}{3s^3 + 10} \xrightarrow{\frac{9}{2}s} \frac{9/2}{3s} + \frac{2s}{3s^3 + 10} \\
 & \frac{2s}{3s^3 + 10} \xrightarrow{\frac{2}{30}s} \frac{2/30}{3s} + \frac{2s}{3s^3 + 10} \\
 & \frac{2s}{3s^3 + 10} \xrightarrow{\frac{10}{2}s} \frac{10/2}{3s} + \frac{2s}{3s^3 + 10} \\
 & \frac{2s}{3s^3 + 10} \xrightarrow{\frac{2}{3}s} \frac{2/3}{3s} + \frac{2s}{3s^3 + 10} \\
 & \frac{2s}{3s^3 + 10} \xrightarrow{0} \frac{2/3}{3s} + \frac{2s}{3s^3 + 10}
 \end{aligned}$$

$$\Rightarrow z = \frac{1}{s + \frac{1}{\frac{1}{3}s + \frac{1}{\frac{9}{2}s + \frac{1}{\frac{2}{30}s + \frac{10}{2}s + \frac{2}{3}s}}}}}$$

$$\Rightarrow z(s) \rightarrow \begin{array}{|c|c|} \hline C=1 & C=\frac{9}{2} \\ \hline L=1/3 & L=1/15 \\ \hline \end{array}$$

#2. $f(s) = [(2s^2 + 4) + (s^2 + 2s)] / [(4s^2 + 2) + (s^3 + 8s)] = N(s)/D(s)$

$N(s) \Rightarrow \text{odd/even} = 2$

$z = \frac{s(s^2 + 2)}{2(s^2 + 2)} = \frac{s}{2} \Rightarrow N(s) = (s^2 + 2)(s + 2) \leftarrow \text{Hurwitz, not strict with simple 0}$

@ $s = \pm j\sqrt{2}$
& one in LHP
@ $s = -2$


$D(s) \Rightarrow \text{odd/even} = 2$

$z = \frac{s^3 + 8s}{4s^2 + 2} \Rightarrow 4s^2 + 2 \mid s^3 + 8s$

$$\begin{array}{r}
 \frac{1}{4}s \\
 \hline
 4s^2 + 2 \mid s^3 + 8s \\
 \underline{4s^2 + \frac{1}{2}s} \\
 \frac{15}{2}s \\
 \underline{\frac{15}{2}s + \frac{15}{4}} \\
 \frac{15}{4} \\
 \underline{\frac{15}{4}} \\
 0
 \end{array}$$

$\Rightarrow z = \frac{1}{4}s + \frac{1}{\frac{8}{15}s + \frac{1}{\frac{4}{15}s}} \Rightarrow \text{PR} \times \mathcal{S}[D] = 3 = \mathcal{S}[z] \Rightarrow \text{strictly Hurwitz}$

3 a)

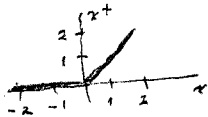

Two capacitor currents

$$C_1 \dot{x}_1 = \text{current down into } C_1 = G_{i1}(x_2^+ - x_1) + i_1 - G_{e1}x_1$$

$$C_2 \dot{x}_2 = \text{ " " " } C_2 = G_{i2}(x_1^+ - x_2) + i_2 - G_{e2}x_2$$

$$\Rightarrow \begin{bmatrix} C_1 & 0 \\ 0 & C_2 \end{bmatrix} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -G_{e1} - G_{i1} & 0 \\ 0 & -G_{e2} - G_{i2} \end{bmatrix} x + \begin{bmatrix} 0 & G_{i1} \\ G_{i2} & 0 \end{bmatrix} \begin{bmatrix} x_1^+ \\ x_2^+ \end{bmatrix} + \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

isolating $-x$ divide by $\begin{bmatrix} G_{e1} + G_{i1} & 0 \\ 0 & G_{e2} + G_{i2} \end{bmatrix}$

$$\Rightarrow \underbrace{\begin{bmatrix} \frac{C_1}{G_{e1} + G_{i1}} & 0 \\ 0 & \frac{C_2}{G_{e2} + G_{i2}} \end{bmatrix}}_{(C)} \frac{dx}{dt} = -x + \underbrace{\begin{bmatrix} 0 & \frac{G_{i1}}{G_{e1} + G_{i1}} \\ \frac{G_{i2}}{G_{e2} + G_{i2}} & 0 \end{bmatrix}}_W x^+ + \underbrace{\begin{bmatrix} \frac{1}{G_{e1} + G_{i1}} & 0 \\ 0 & \frac{1}{G_{e2} + G_{i2}} \end{bmatrix}}_B i$$

b) \rightarrow

and $x^+ = \text{output voltages}$

$$v_o = \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}}_C x^+$$

b) \rightarrow

- c) 1) when $x_i^+ = 0 \Rightarrow$ cancel $x^+ = x \Rightarrow \textcircled{1} \dot{x} = (-I_2 + W)x + Bi = Ax + Bi, v_o = Cx \Rightarrow A = -I_2 + W$
 2) when $x_i^+ = 0 \Rightarrow$ cancel $W = 0 \Rightarrow \textcircled{2} \dot{x} = -I_2 x + Bi = Ax + Bi, v_o = 0 \Rightarrow A = -I_2$

#4, $i_1 = g_1 v_y$, $i_2 = g_2 v_y$; $i_y = g v_y = -g_3 (v_1 - v_2)$

$\Rightarrow v_y = \frac{g_3}{g} (v_1 - v_2)$

$\Rightarrow i_1 = \frac{g_1 g_3}{g} (v_1 - v_2)$, $i_2 = -\frac{g_2 g_3}{g} (v_1 - v_2) \Rightarrow$

$\Rightarrow i = Y v \Rightarrow Y = \frac{g_3}{g(a)} \begin{bmatrix} g_1 & -g_1 \\ g_2 & -g_2 \end{bmatrix}$ if $g_2 = -g_1$ $\Rightarrow Y = \frac{-g_1 g_3}{C a} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$
 $2 g = C a$

a)

$\Rightarrow h < 0$ if $\frac{C}{g_1 g_3} > 0 \Rightarrow$ if $C > 0$ then sign $g_1 = +$ & sign $g_3 = -$
 (= condition for $h < 0$)

b) if $v_2 = 0$, $Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = g_{11} v_1 = i_1 \Rightarrow g_{11} = -g_1 g_3 / Y(a)$

#5

$Y = \begin{bmatrix} y & -y-g \\ -y+g & y \end{bmatrix}$; if $y_{load} = G = Y/R$ then $(-G - y_{22}) v_2 = y_{21} v_1 \Rightarrow$

$\Rightarrow y_{in} = y_{11} + y_{12} \left(\frac{-1}{G + y_{22}} y_{21} \right) = \frac{\Delta_1 + G y_{11}}{G + y_{22}}$; $\Delta_y = y_{11} y_{22} - y_{12} y_{21}$
 = determinant Y

For $y_{in} = G = \frac{\Delta_y + G y_{11}}{G + y_{22}} \Rightarrow G^2 + G y_{22} = \Delta_y + G y_{11} \Rightarrow G^2 = y_{12} y_{21}$

a) \Rightarrow constant R if $g = \pm G$

b) From above $v_2/v_1 = \frac{-y_{21}}{G + y_{22}} = \frac{-(-y+g)}{G+y} = \frac{y-g}{y+G} = \begin{cases} 1 & \text{if } g = -G \\ \frac{y-G}{y+G} & \text{if } g = +G \end{cases}$