
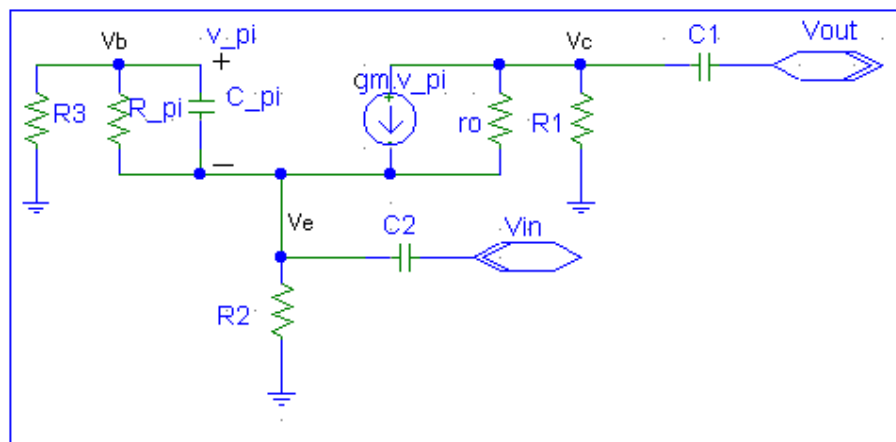


Solution to Problem 2 - Homework 4 - ENEE 302

AD Revised 05/14/02 & 05/19/02

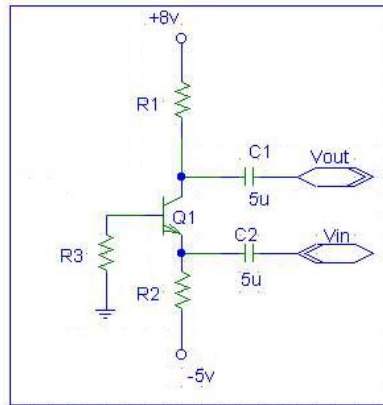2. For the following common-base circuit:
- Determine the gain $A_v(s) = V_{out} / V_{in}$ for all frequencies assuming $C_\mu = 0$.
 - Determine Z_i and Z_o , input and output impedances for all frequencies as functions of s .
 - Plot $A_v(s)$ using Pspice and the BN2x2 npn transistor for $R_1=3.6K$, $R_2=3.9K$, $R_3 = 390K$, $C_1= 5\mu F$, $C_2=5\mu F$.



Above, is the small signal model of the circuit.

Here, $r_\pi = \frac{\beta \times I_C}{V_T}$, $r_o = \frac{V_A}{I_C}$, $g_m = \frac{I_C}{V_T}$ and C_π depends on the transistor parameters.

where I_C , the DC bias current, is calculated from the basic KVL in the circuit around the base-emitter- V_{EE} loop:

$$0 = R_3 \times \frac{I_C}{\beta} + 0.7 + \frac{I_C}{\alpha} \times R_2 - 5.0$$

The impedance of capacitor C will be considered $\frac{1}{C \times s}$ in writing KVL and KCL equations since the behavior of the circuit in all frequencies is wanted.

* Below, are the basic KVL and KCL equations required to calculate Zi :

$$\text{KVL @ c: } \frac{v_c}{R_1} + \frac{v_c - v_e}{r_o} + g_m(v_b - v_e) = 0 ; C_1 \text{ is connected to } \infty \text{ load!}$$

$$\text{KVL @ b: } \frac{v_b - v_e}{r_\pi \parallel c_\pi} + \frac{v_b}{R_3} = 0$$

$$\text{KVL @ e: } (v_e - v_{in}) \times c_2 s + \frac{v_e - v_b}{r_\pi \parallel c_\pi} + \frac{v_e}{R_2} + \frac{v_e - v_c}{r_o} - g_m(v_b - v_e) = 0$$

Assuming $r_o \geq R_1$ and $i_e \approx \beta \times i_b$, the followings can be obtained after simplifying the circuit equations:

The input impedance is $\frac{v_{in}}{I_{c2}} = \frac{v_{in}}{(v_{in} - v_e) \times c_2 s}$, which after simplification will be

$$\text{the following: } Z_i = \frac{1}{C_2 \times s} + (R_2 \parallel [(\frac{r_\pi}{\beta} \parallel c_\pi) + \frac{R_3}{\beta}]);$$

Note that this impedance is the series of $\frac{1}{C_2 \times s}$ with the impedance that is seen looking from C_2 in the circuit, which is.

$$R_2 \parallel [(\frac{r_\pi}{\beta} \parallel c_\pi) + \frac{R_3}{\beta}].$$

* Below, are the basic KVL and KCL equations required to calculate Zo :

$$\text{KVL @ c: } \frac{v_c - v_o}{R_1} + \frac{v_c - v_e}{r_o} + g_m(v_b - v_e) = 0$$

$$\text{KVL @ b: } \frac{v_b - v_e}{r_\pi \parallel c_\pi} + \frac{v_b}{R_3} = 0$$

$$\text{KVL @ e: } v_e \times c_2 s + \frac{v_e - v_b}{r_\pi \parallel c_\pi} + \frac{v_e}{R_2} + \frac{v_e - v_c}{r_o} - g_m(v_b - v_e) = 0 ; \text{ Note } v_{in} = 0.$$

Assuming $r_o \geq R_1$ and $i_e \approx \beta \times i_b$, the followings can be obtained after simplifying the circuit equations:

The output impedance is $\frac{v_{out}}{I_{c1}} = \frac{v_{out}}{(v_{out} - v_c) \times c_1 s}$, which after simplification will be

$$\text{the following: } Z_o = \frac{1}{C_1 \times s} + R_1$$

Note the output impedance is the series of $\frac{1}{C_1 \times s}$ with the impedance that is seen looking from C_1 in the circuit which is R_1 with a good approximation. ($r_o \geq R_1$)

* Below, are the basic KVL and KCL equations required to calculate A_v :

$$\text{KVL @ c: } \frac{v_c}{R_1} + \frac{v_c - v_e}{r_o} + g_m(v_b - v_e) + (v_o - v_c) \times C_1 s = 0$$

$$\text{KVL @ b: } \frac{v_b - v_e}{r_\pi \parallel c_\pi} + \frac{v_b}{R_3} = 0$$

$$\text{KVL @ e: } (v_e - v_{in}) \times C_2 s + \frac{v_e - v_b}{r_\pi \parallel c_\pi} + \frac{v_e}{R_2} + \frac{v_e - v_c}{r_o} - g_m(v_b - v_e) = 0$$

The following equations can be rearranged to solve for base, collector and emitter voltages:

$$\left\{ \begin{array}{l} g_m v_b + \left(\frac{1}{R_1} + \frac{1}{r_o} - C_1 s \right) v_c + \left(\frac{-1}{r_o} - g_m \right) v_e = C_1 s \times v_o \\ \left(\frac{1}{r_\pi \parallel c_\pi} + \frac{1}{R_3} \right) v_b + \left(\frac{-1}{r_\pi \parallel c_\pi} \right) v_e = 0 \\ \left(\frac{-1}{c_\pi \parallel r_\pi} - g_m \right) v_b + \left(\frac{-1}{r_o} \right) v_c + \left(C_2 s + \frac{1}{r_\pi \parallel c_\pi} + \frac{1}{R_2} + \frac{1}{r_o} + g_m \right) v_e = C_2 s \times v_{in} \end{array} \right.$$

Finally, below is the expression for gain:

$$A_v(s) = \frac{-R_2}{R_1} \times \frac{R_1 + r_o + r_o R_1 C_1 s}{r_o R_1 C_1 s} \times \frac{C_2 s (R_3 (r_\pi + c_\pi) + r_\pi c_\pi R_2)}{\beta R_2 (r_\pi + c_\pi) + R_3 (r_\pi + c_\pi) + r_\pi c_\pi + C_2 s (R_3 (r_\pi + c_\pi) + r_\pi c_\pi R_2)}$$

Note for high frequencies, the second and third term get close to one and the gain is close to $-R_1/R_2$.

Note that initially assuming C_1 and C_2 short (very high frequencies), then the gain will be like a normal common-base amplifier:

$A_v \cong -\frac{R_1}{R_2}$, but for low frequencies C_1 and C_2 behave like open circuit and the gain will be zero.

The cut-off frequency where the gain will rise from 0 is calculated as below:

$$w_1 = \frac{1}{2\pi \times C_1 \times R_1}$$

$$w_2 = \frac{1}{2\pi \times C_2 \times (R_2 \parallel (r_e + \frac{R_3}{\beta}))}$$

w_1 is the frequency associated with C_1 and is calculated by multiplying these effective R.C seen from C_1 and so is w_2 calculated for C_2 .

So, the overall gain expression will be the following:

$$A_v(j\omega) = \begin{cases} 0 & \omega < \min(\omega_1, \omega_2) \\ -\frac{R_1}{R_2} & \omega > \min(\omega_1, \omega_2) \end{cases}$$