

HOMEWORK 1

02/13/02 DK

Due:02/21/02

NOTE: Only the problems marked with points are to be turned in and graded.
 Simulate using the diode D1N4002 for the PSpice problems.

1. Figure 1 is the circuit for a full wave rectifier. The input voltage is $V1 = 5\sin(200\pi t)$. Using PSpice and normal calculations find the output voltage V_o . (25 pts)

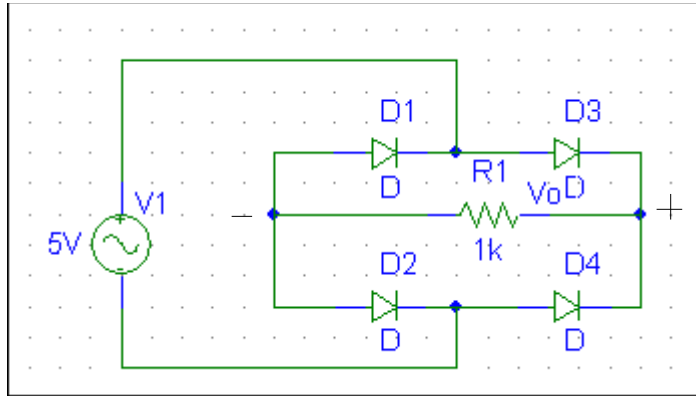


Fig.1

2. In Fig. 2 find the value of $i(1)$, $i(2)$ and $i(3)$. (PSpice simulation not needed).

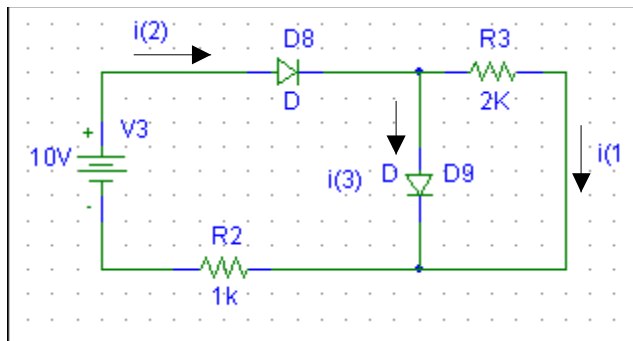


Fig. 2

3. Determine the output waveform for the network given in Fig. 3 for the two cases when $V_9 = 5V$, $10V$ and $V_i = 20 \sin(200\pi t)$. How would you name this circuit? Also show the output $V_o(t)$ using PSpice. (25 pts)

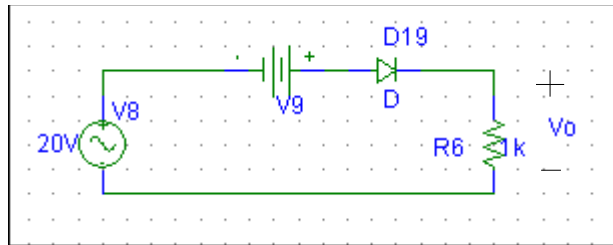


Fig. 3

4. What is the output voltage waveform V_o in Fig. 4, when the inputs are:
 a. $V_1 = 5V$, $V_2 = 0V$, $V_3 = 0V$, $V_4 = 0V$
 b. $V_1 = 0V$, $V_2 = 0V$, $V_3 = 0V$, $V_4 = 0V$
 Also show the output using PSpice. (50 pts)

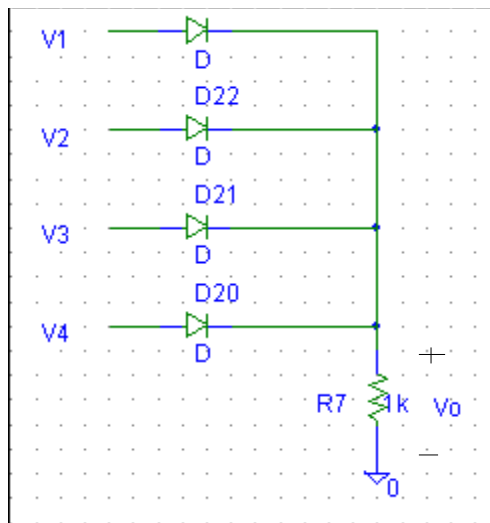


Fig. 4

5. Can transistors act as diodes? If so draw the circuit diagram and explain.