

ENEE 302 Homework Set 2 Due Tu 03/09/04

for all these problems use the mnmosis and mpmosis transistors with (unless otherwise specified)  $L=W=10\mu$ ,  $V_{dd}=5V=-V_{ss}$ .

#1. 25 points (design of current sources)

Give analytic design (that is, use equations) of current sources to give 1.2mA via the following circuits:


- A current "sink" with the current determined by a resistor R (attached to Vdd) and the left and right NMOS transistors identical with the sources and bulks tied to Vss.
- A current "source" with the current determined by a resistor R (attached to Vss) and the left and right PMOS transistors identical with sources and bulks tied to Vdd.
- Replace the resistor R by a PMOS for a) and an NMOS for b) and repeat parts a) and b) except now allow the W/L of the sink or source transistor to vary as needed.

#2. 25 points (Spice check of current source designs)

- Run Spice to check all of the results of problem #1 above. Explain any differences between the simulation versus the analytic results. For this use a load that is ground.
- For the "sink" current source of problem #1c) make a Spice plot showing the NMOS curve with the PMOS curve for a load line. From that find the voltage at the Q point for the left side of the circuit. Calculate this Q point voltage analytically and discuss any differences.
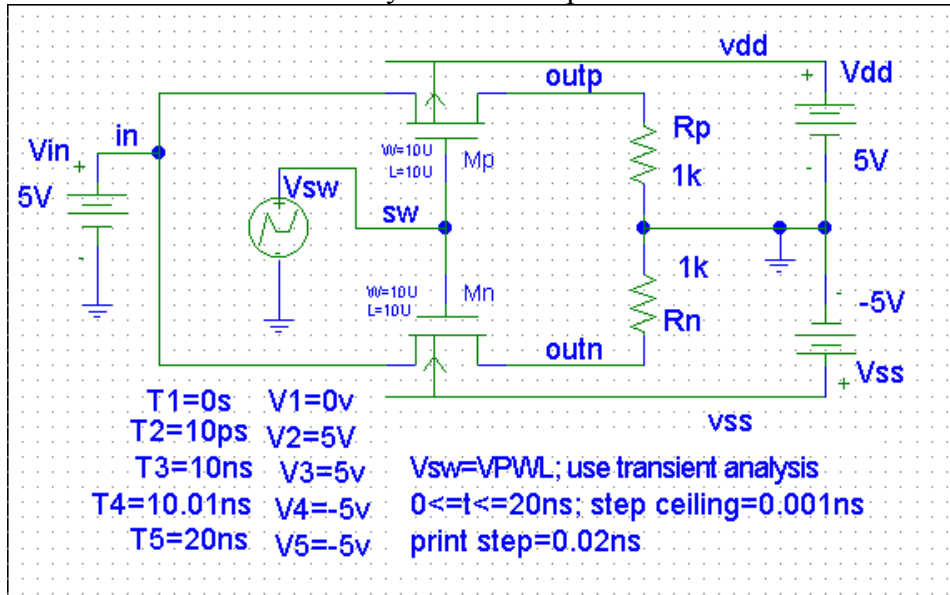
#3. 25 points (CMOS switches)

Setup the following circuit in Spice plot  $V_{in}$ ,  $V_{outp}$ , and  $V_{outn}$  for  $0 < t < 20ns$ . Zoom into  $0 < t < 0.3ns$ . Write equations justifying the non-transient behavior and discuss the transient behavior and why it is to be expected.



#4. 25 points (switches for pass transistor logic)

Set up and run the pass transistor logic circuit of Figure 10.30, p. 990, [= Figure 13.30 p. 1088 of fourth edition] of the text. Check that it gives the designated logic function.