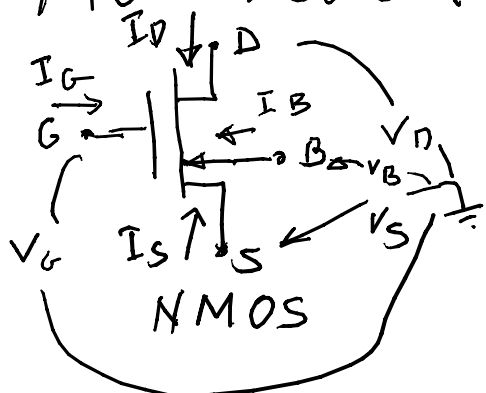


MOS model

M


EE302
02/08/05




D = drain if voltage at D is larger than voltage at S
(if reverse then D → source
S → drain)

at DC, $I_G \equiv 0$ if B tied to S then $I_B = 0$
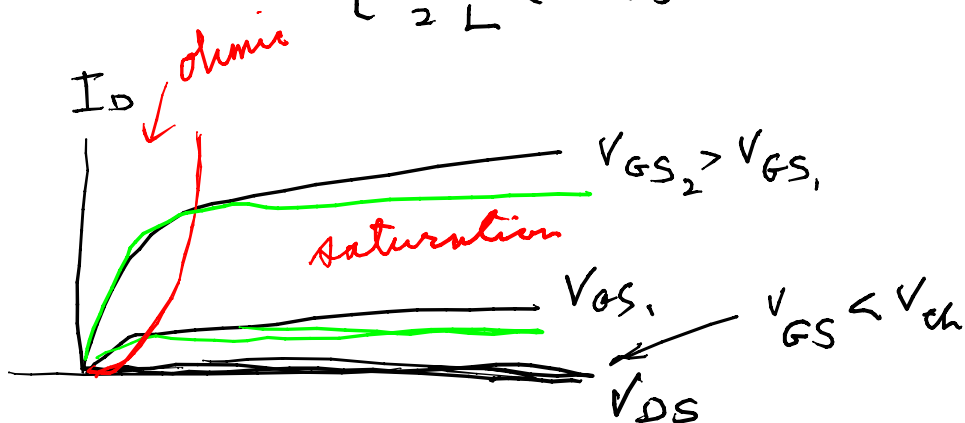
$$I_D = \begin{cases} 0 & V_{GS} < V_{th} & \text{off} & \text{P.260} \\ \frac{K_P W}{2 L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) & \text{if } V_{DS} \geq V_{GS} - V_{th} \geq 0 \\ \frac{K_P W}{2 L} (2(V_{GS} - V_{th})V_{DS} - V_{DS}^2) (1 + \lambda V_{DS}) & \text{if } V_{GS} - V_{th} \geq V_{DS} \geq 0 \end{cases}$$



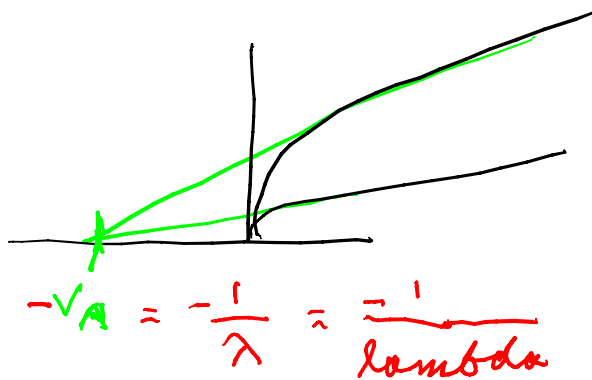if $V_{BS} = 0$
then $V_{th} = V_{T0}$
in Apire



for MNMOSIS: $K_P = 5.048 \times 10^{-5} \text{ A/V}^2$; $\lambda = 1.843384 \times 10^{-2} \text{ V}^{-1}$
 $V_{T0} = 0.858153 \text{ V}$ $\gamma = 0.198$

for MPMOSIS: $K_P = 1.908 \times 10^{-5} \text{ A/V}^2 < K_{P_{nchannel}}$


$$V_{T0} = -0.88927 \text{ V}; |V_{T0p}| > |V_{T0n}|$$

$$\lambda = 5.011626 \times 10^{-2} \frac{1}{\text{V}} \quad \gamma = 0.6289$$

for V_{th} vs V_{T0} , $\gamma \cdot (4.33) \cdot 1.258$ (Body effect)

$$V_{th} = V_{T0} + \gamma (\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F})$$

MOS diode

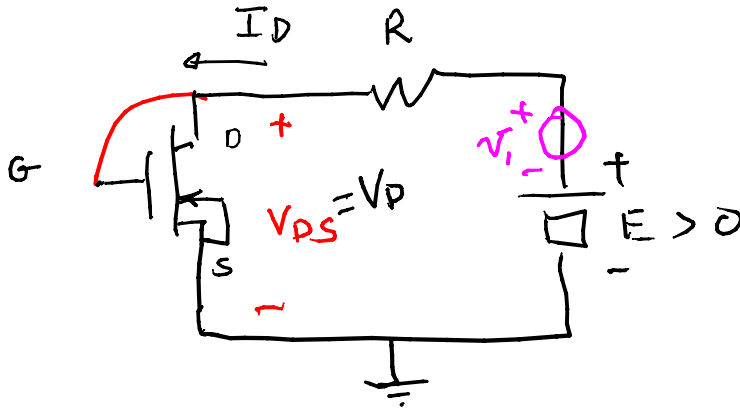


here $V_{th} = V_{T0}$
 if $V_{T0} = 0.88$
 then if $G = S$
 no current
 will flow

here $V_{GS} = V_{DS}$

$$\text{or } V_{GS} - V_{T0} < V_{DS}$$

if $V_{GS} > V_{T0}$ then turned
 on and in saturation
 region



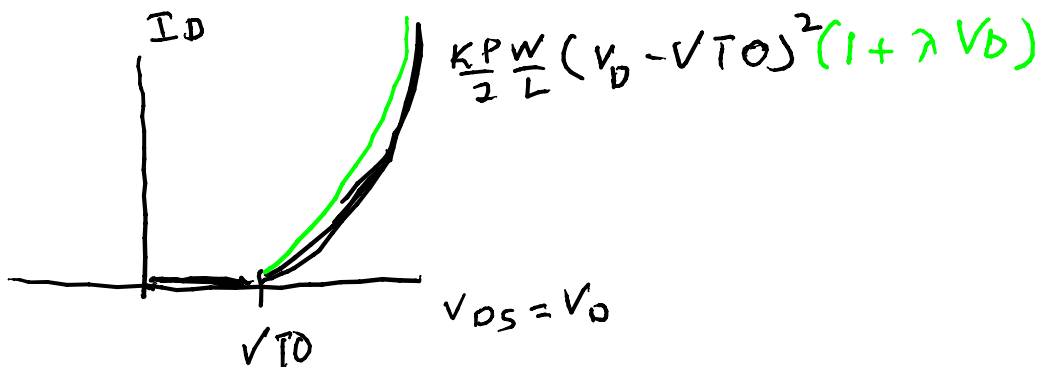
$$I_D = \begin{cases} 0 & 0 \leq V_{DS} = V_{GS} < V_{T0} \\ \frac{K_P W}{2 L} (V_{DS} - V_{T0})^2 & V_{DS} > V_{T0} \end{cases}$$



for right hand side $V_D = -RI_D + E$

$$\Rightarrow I_D = -\frac{1}{R}(V_D - E) = -GV_D + E/R$$

$$= -G(V_D - E)$$

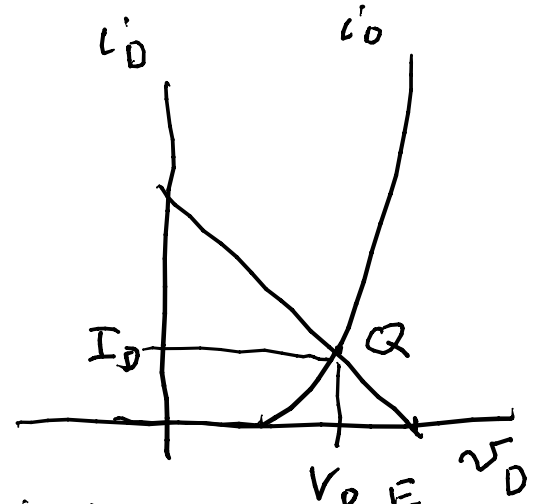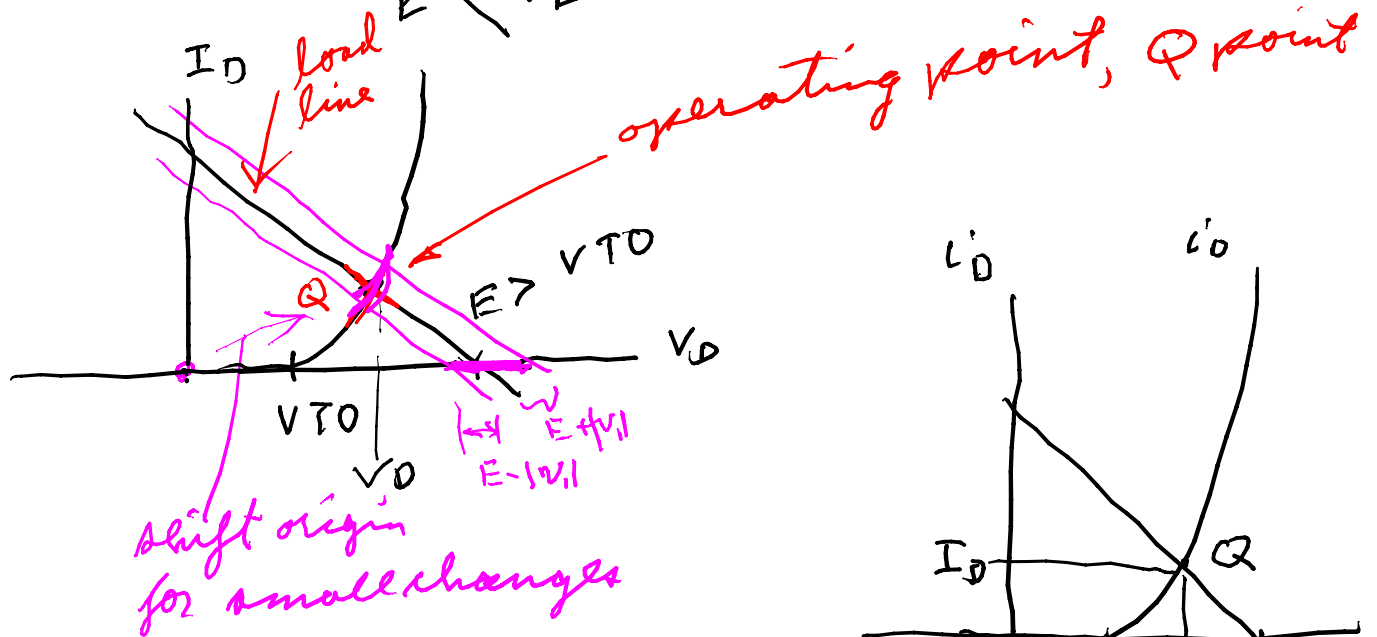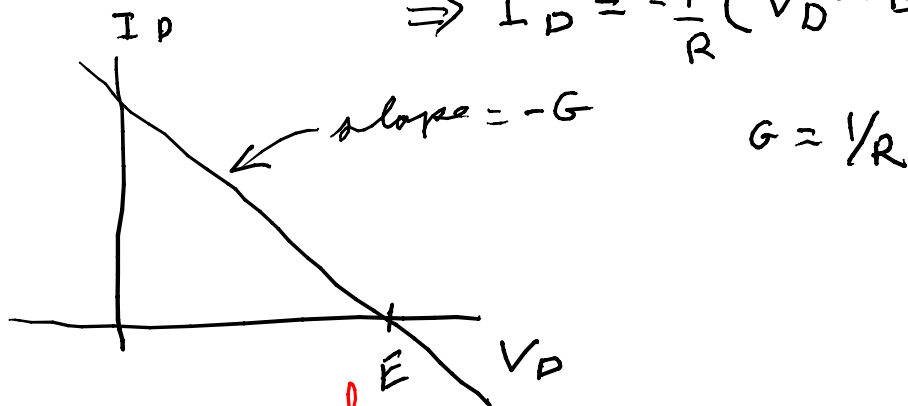


Taylor series expansion.

$$i_D = I_D + \frac{\partial i_D}{\partial v_D} (v_D - V_D) + \frac{\partial^2 i_D}{2 \partial v_D^2} (v_D - V_D)^2 + \dots$$

\uparrow total current \uparrow at Q pt \uparrow Q

$$\therefore i_D' = i_D - I_D = \frac{\partial i_D}{\partial v_D} v_D \Rightarrow$$

$$i_D' = g_d \cdot v_D$$

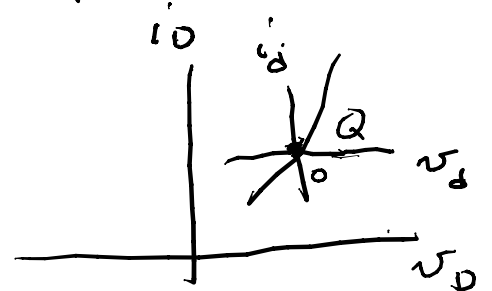

$$I_D = \frac{K_P W}{2 L} (V_D - V_{T0})^2 ; g_d = \frac{K_P W}{L} (V_D - V_{T0})$$

small signal equivalent = $\frac{K_P W}{L} (V_D - V_{T0})$

