

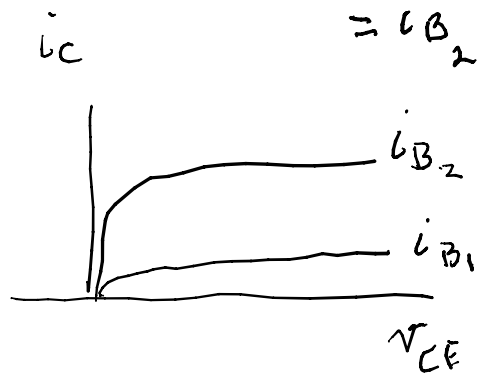


# Darlington pair for BJT

EE302  
02/15/05

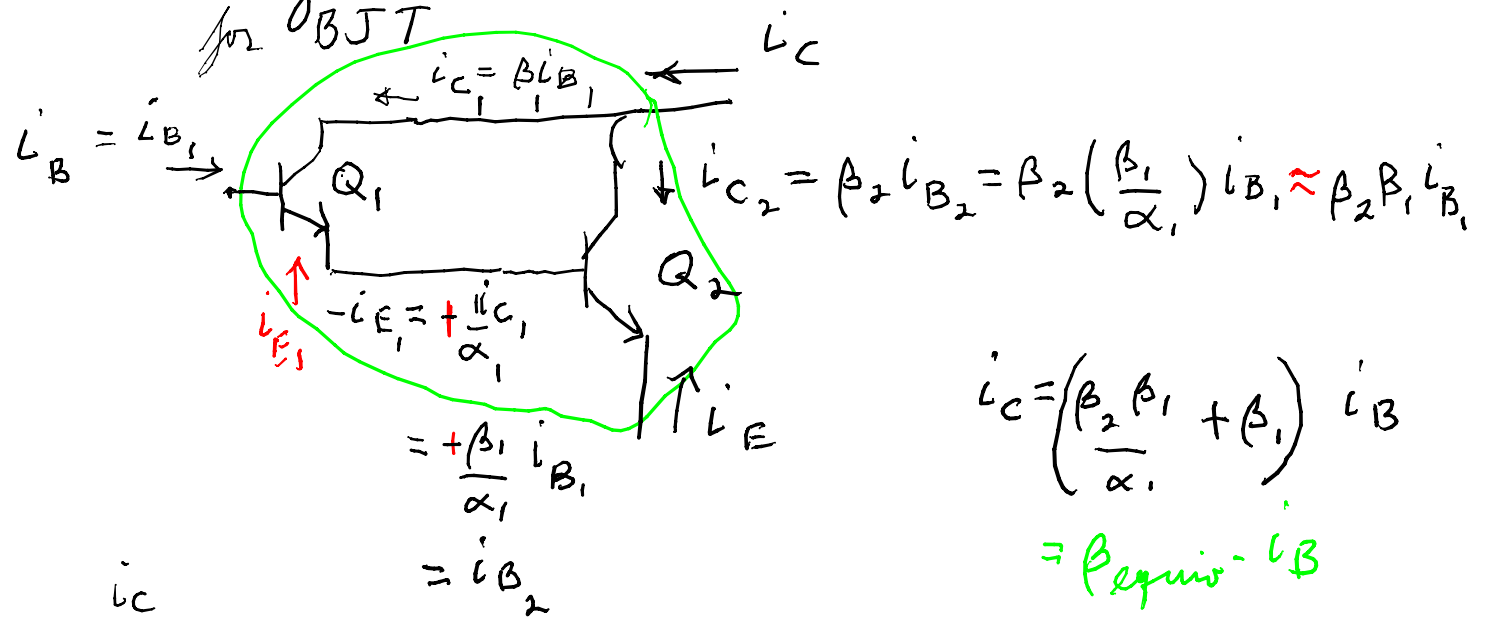

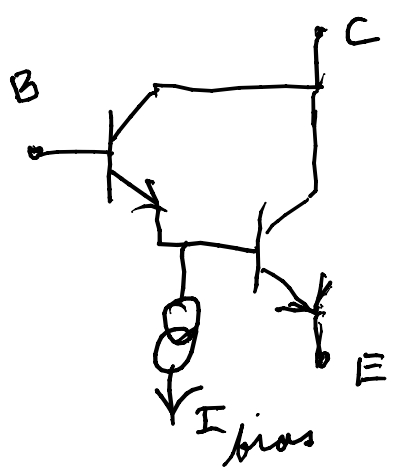to bias  $Q_1$ , as  $i_{B_1} < i_{B_2}$  we force a bias current on  $i_{E_1}$ .



gives very large  $\beta$  for signals


$$\beta_{eq} \approx \beta^2$$

ex if  $\beta = 100$ ,  $\beta^2 = 10^4$


Using a BJT for signals:  
 convention for designating  $v, i$

$i_B = \text{total}$ ,  $I_B = \text{bias}$ ,  $i_b = \text{signal}$
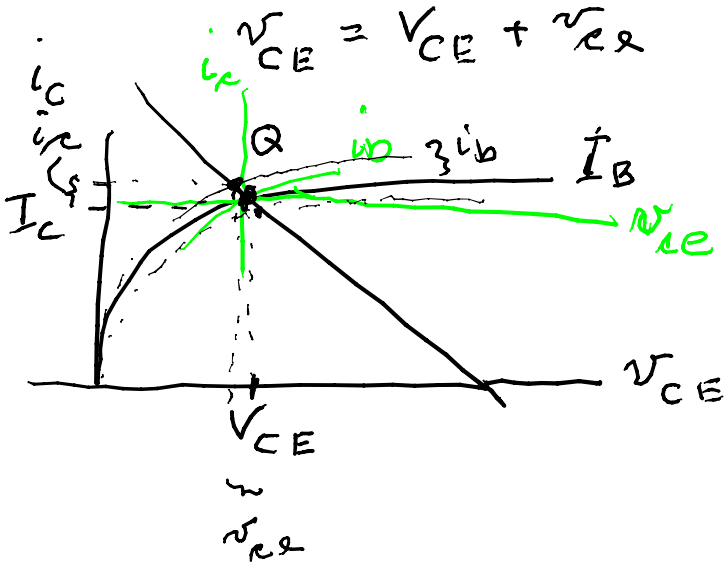
$$i_B = I_B + i_b \Rightarrow i_b = i_B - I_B$$



$$v_{re} = v_{CE} - V_{CE}$$

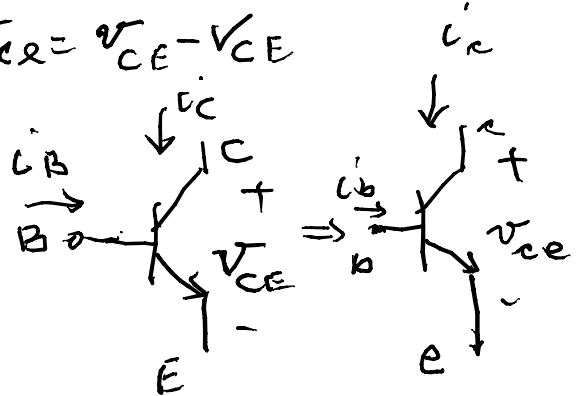


$$i_C = f(i_B, v_{CE}) = f(I_B, V_{CE}) + \left. \frac{\partial f}{\partial i_B} \right|_{\substack{Q \\ i_B = I_B \\ v_{CE} = V_{CE}}} (i_b - I_B) + \dots$$

$$\Rightarrow \left. \frac{\partial f}{\partial v_{CE}} \right|_Q (v_{CE} - V_{CE}) + \frac{\partial^2}{\partial i_B \partial v_{CE}} + \dots$$

$$\approx f(I_B, V_{CE}) + \beta i_b + g_{re} \cdot v_{re}$$
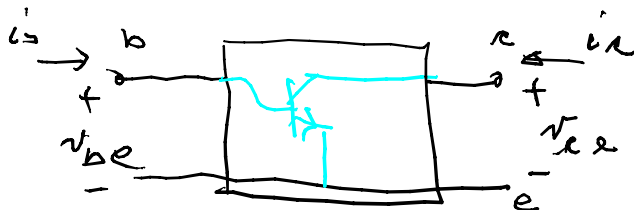
$$= I_C + \beta i_b + g_{re} v_{re} \Rightarrow i_c = \beta i_b + g_{re} v_{re}$$



$$i_c = \beta i_b + g_{re} v_{re}$$



admittance matrix of a 2-port

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} ; \rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} i_b \\ i_c \end{bmatrix} ; \begin{bmatrix} v_{be} \\ v_{ce} \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$= \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad \text{gives a } \pi \text{ equivalent circuit} \\ \text{see p. 448 for BJT}$$

here  $y_{12} = 0$  for the BJT for low frequencies
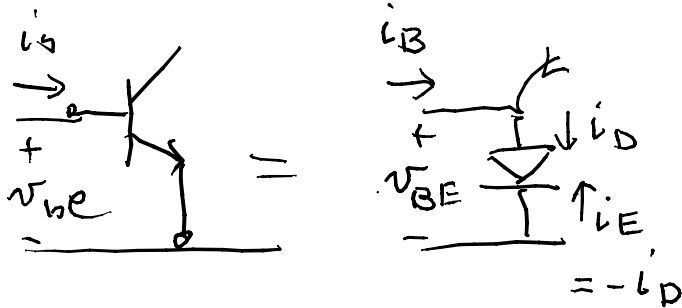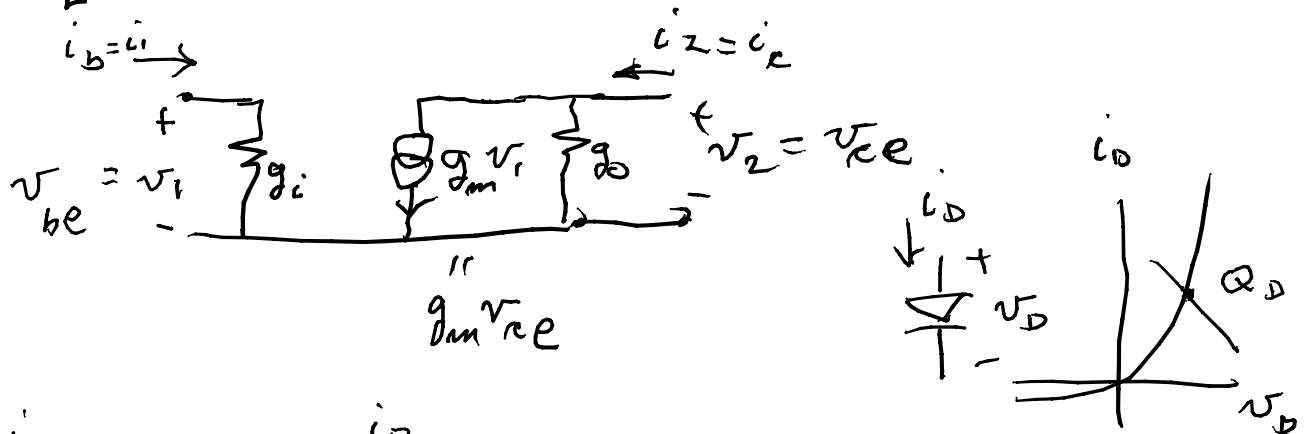
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & 0 \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_i & 0 \\ g_m & g_o \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



$$i_D = I_S (e^{v_D/V_T} - 1)$$

$V_T = \text{Thermal voltage}$   
 $= \frac{kT}{q} \approx 0.026 \text{ V}$   
 @ room T

$$i_D = I_D + \frac{\partial i_D}{\partial v_D} \cdot (v_D - V_D) + \dots$$

$$i_d = i_D - I_D = \frac{I_S}{V_T} e^{v_D/V_T} v_d + \dots$$

assume  $\approx 0$  by small changes around  $Q_D$  point

$$= \frac{I_D}{V_T} v_d = g_d v_d$$

for our transistor  $i_e = -i_d = -g_d \cdot v_{be} = -\frac{I_E}{V_T} \cdot v_{be}$


$i_c = \beta i_b, i_e = -\frac{1}{\alpha} i_c$

$i_e = -\frac{1}{\alpha} i_c = -\frac{\beta}{\alpha} i_b = -\frac{I_E}{V_T} v_{be}$

$I_c = \beta I_B, I_E = -\frac{1}{\alpha} I_c$

$\Rightarrow i_b = \frac{\alpha}{\beta} \frac{I_E}{V_T} \cdot v_{be} = -\frac{I_c}{\beta V_T} v_{BE}$

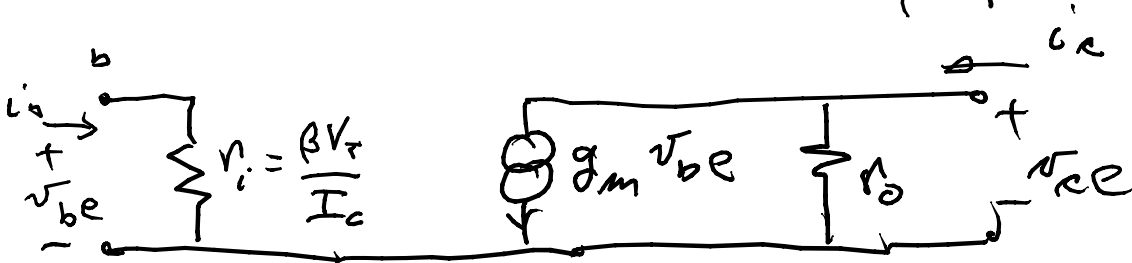$i_b = \frac{I_c}{\beta V_T} \cdot v_{be} = g_i v_{be}, g_i = \frac{I_c}{\beta V_T}$




$g_m = \left. \frac{\partial i_c}{\partial v_{BE}} \right|_Q$  ;  $-i_c = \alpha i_E \cdot v_{BE}/V_T$   
 $-i_E = I_{SE} e^{v_{BE}/V_T}$

$\left. \frac{\partial i_E}{\partial v_{BE}} \right|_Q = -\frac{I_{SE}}{V_T} e^{v_{BE}/V_T} = -\frac{I_E}{V_T}$

$\left. \frac{\partial i_c}{\partial v_{BE}} \right|_Q = -\alpha \left( -\frac{I_E}{V_T} \right)$

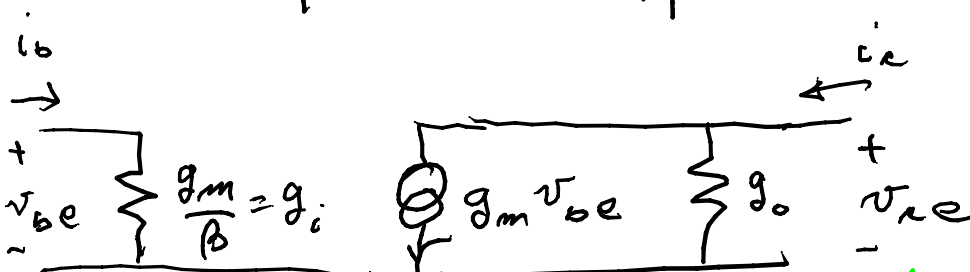
$Q = \frac{I_c}{V_T}$  ;  $g_m = \frac{I_c}{V_T}$  ;  $g_i = \frac{I_c}{\beta V_T} = \frac{g_m}{\beta}$



$g_m = \frac{|I_c|}{V_T}$

$g_o = g_m \cdot \frac{V_T}{V_A}$

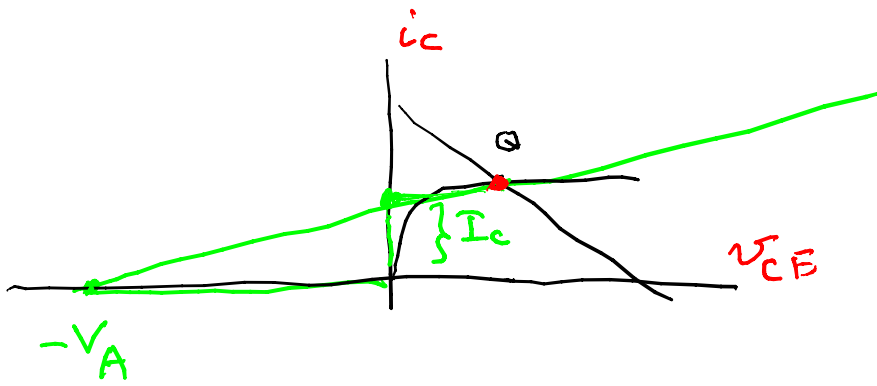assumes  $r_{i2} = 0$   
 small signal equivalent circuit for a grounded emitter



NPN transistor

$$\text{slope} = \frac{I_C}{V_A} = \frac{I_C}{V_T} \cdot \frac{V_T}{V_A}$$

$$\frac{\partial i_c}{\partial V_{CE}} = g_m \cdot \frac{V_T}{V_A}$$

=  $g_o$

$V_A = \text{Early Voltage} > 0$

same equivalent circuit for a pnp if  $I_C \Rightarrow |I_D|$