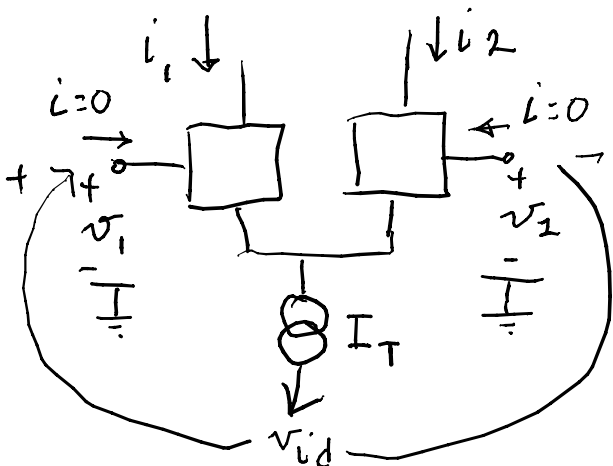


# Differential pairs

693 = CMOS, 738 = BJT, 1052 = ECL

EE302  
02/17/05





$$v_{id} = v_1 - v_2$$

$i_1 + i_2 = I_T =$  tail current

normally  $i_1$  increases if  $v_1$  is raised if  $v_2$  is fixed

if  $v_1$  is fixed &  $v_2$  raised  $i_2$  increases

usually look at  $i_1 - i_2$

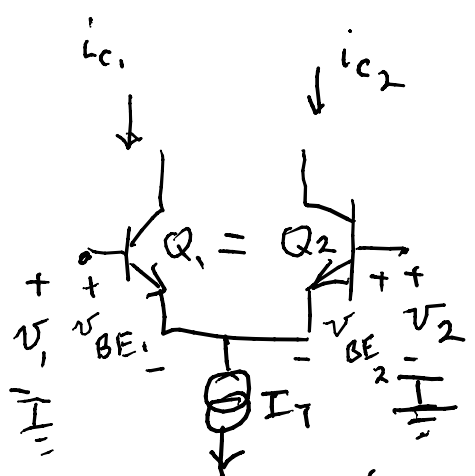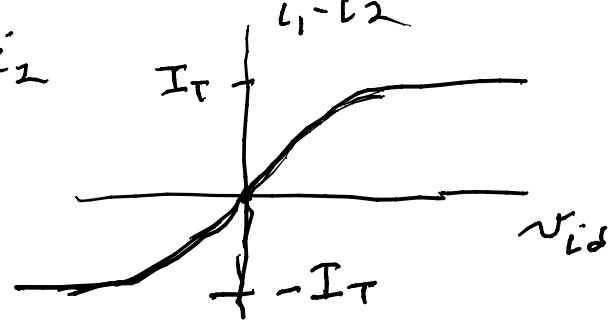

$$i_{c1} + i_{c2} = I_T$$

$$v_{id} = v_{BE1} - v_{BE2}$$

$$i_{c1} \approx \alpha(-i_{E1}); i_{c2} \approx \alpha(-i_{E2})$$

$$i_{E1} \approx I_S e^{v_{BE1}/V_T}; i_{E2} = I_S e^{v_{BE2}/V_T} \text{ if } Q_1 \& Q_2 \text{ in the forward active region}$$

$$V_T = \text{thermal voltage} = \frac{kT}{q} \approx 26 \text{ mV} @ 300 \text{ K}$$

$$\begin{aligned}
 i_{C_1} - i_{C_2} &= \alpha (i_{E_1} - (-i_{E_2})) = \alpha (i_{E_2} - i_{E_1}) \\
 &= \alpha I_S (e^{+v_{BE_2}/V_T} - e^{v_{BE_1}/V_T}) \\
 &= \alpha I_S e^{v_{BE_2}/V_T} (1 - e^{[v_{BE_1} - v_{BE_2}]/V_T}) \\
 &= \alpha I_S e^{v_{BE_2}/V_T} (1 - e^{v_{id}/V_T})
 \end{aligned}$$

$$i_{C_1} + i_{C_2} = I_T$$

$$\text{sum: } 2i_{C_1} = I_T + \alpha I_S e^{v_{BE_2}/V_T} (1 - e^{v_{id}/V_T})$$

$$\begin{aligned}
 \text{difference: } 2i_{C_2} &= I_T - \alpha I_S e^{v_{BE_2}/V_T} (1 - e^{v_{id}/V_T}) \\
 &= I_T + i_{C_2} (1 - e^{v_{id}/V_T}) \quad \text{or } \alpha i_E = -i_C
 \end{aligned}$$

$$i_{C_2} [2 - (1 - e^{v_{id}/V_T})] = I_T$$

$$i_{C_2} = \frac{I_T}{1 + e^{v_{id}/V_T}} ; \quad i_{C_1} = \frac{I_T}{1 + e^{-v_{id}/V_T}} \quad \text{by symmetry of the circuit}$$

$$\begin{aligned}
 i_{C_1} - i_{C_2} &= I_T \left[ \frac{1}{1 + e^{-v_{id}/V_T}} - \frac{1}{1 + e^{+v_{id}/V_T}} \right] \\
 &= I_T \left[ \frac{(1 + e^{+v_{id}/V_T}) - (1 + e^{-v_{id}/V_T})}{(1 + e^{-v_{id}/V_T})(1 + e^{+v_{id}/V_T})} \right]
 \end{aligned}$$




$$\begin{aligned}
 &= I_T \left[ \frac{1 + e^{-v_{id}/V_T} + e^{v_{id}/V_T}}{1 + e^{-v_{id}/V_T} + e^{v_{id}/V_T}} - \frac{1 + e^{-v_{id}/V_T} + e^{v_{id}/V_T}}{1 + e^{-v_{id}/V_T} + e^{v_{id}/V_T}} \right] \\
 &= I_T \left[ \frac{e^{v_{id}/2V_T} [e^{-v_{id}/2V_T} + e^{v_{id}/2V_T}] - e^{-v_{id}/2V_T} [e^{v_{id}/2V_T} + e^{-v_{id}/2V_T}]}{e^{-v_{id}/2V_T} [e^{v_{id}/2V_T} + e^{-v_{id}/2V_T}] e^{v_{id}/2V_T} [e^{-v_{id}/2V_T} + e^{v_{id}/2V_T}]} \right]
 \end{aligned}$$

$$= I_T \left[ \frac{e^{v_{id}/2V_T} - e^{-v_{id}/2V_T}}{e^{v_{id}/2V_T} + e^{-v_{id}/2V_T}} \right] = I_T \times \frac{2 \sinh(v_{id}/2V_T)}{2 \cosh(v_{id}/2V_T)}$$

$i_{c1} - i_{c2} = -i_{out}$

$$= I_T \tanh\left(\frac{v_{id}}{2V_T}\right) = i_{c1} - i_{c2}$$

$$-50 \text{ mV} \approx -2V_T$$

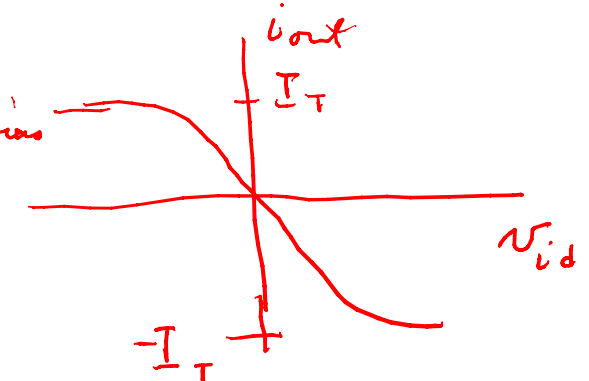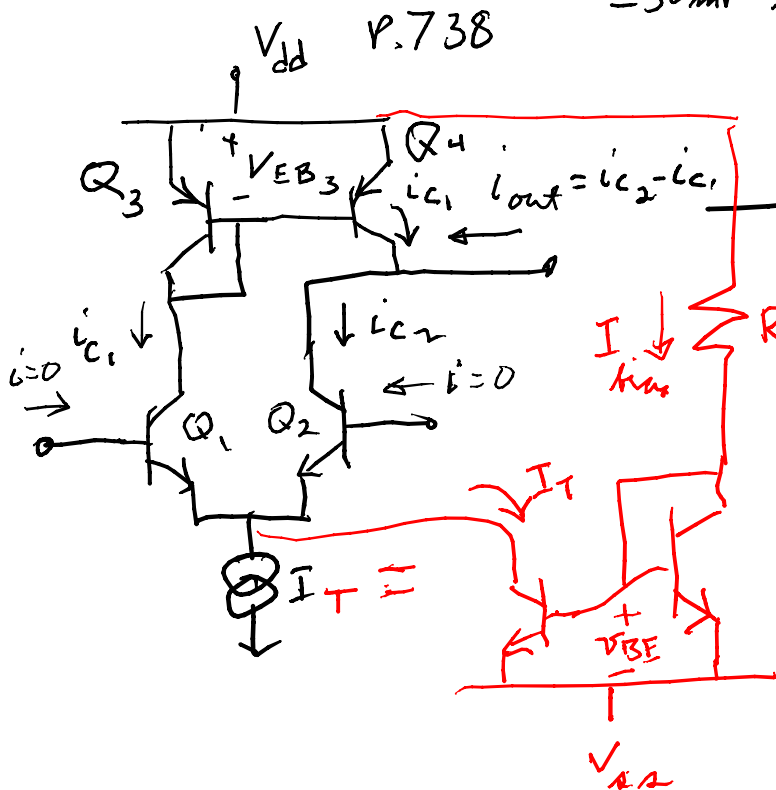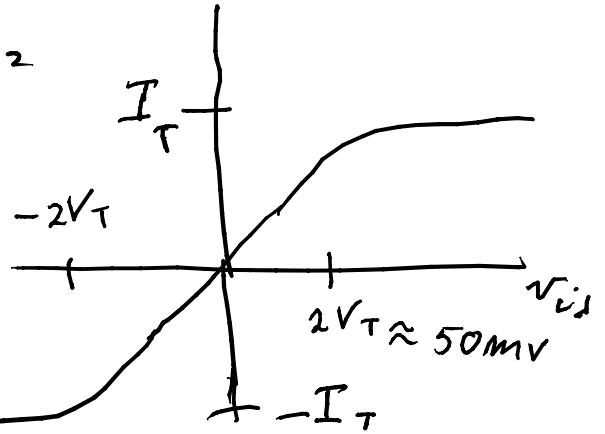

$$V_{BE} \approx 0.6 \text{ V}$$

$$I_{bias} = (V_{DD} - V_{A2} - 0.6 \text{ V}) / R_{bias}$$

||  
 $I_T$

if  $I_T = 3 \text{ ma}$

$$\Rightarrow R_{bias} = \frac{(V_{DD} - V_{A2} - 0.6)}{I_T = 3 \times 10^{-3}} = \frac{9.4}{3} \times 10^3 = 3.13 \text{ k}\Omega$$

if  $V_{DD} = 5 \text{ V}$   
 $V_{A2} = -5 \text{ V}$

More practical

