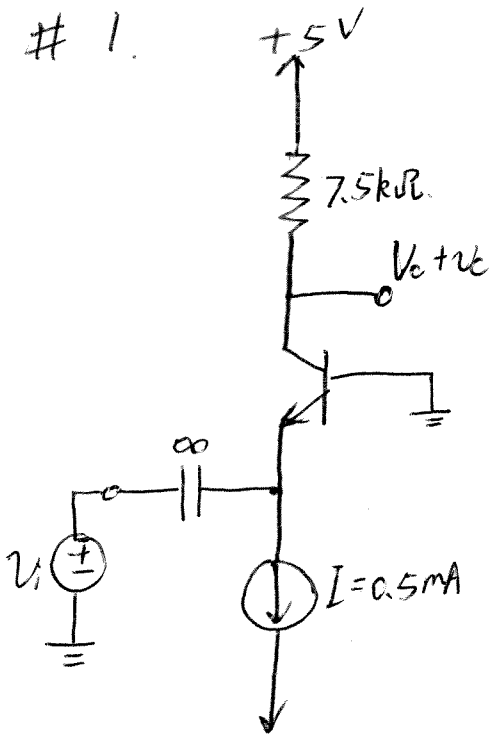


ENEE 302 HW3.

Solutions by Y. Z.

1.



(a) $I_E = 0.5 \text{ mA}$

For $\beta = 100$,


$$I_C = \frac{\beta}{\beta + 1} I_E = \frac{100}{101} I_E$$

$$= 0.495 \text{ mA}$$

$$\therefore V_C = 5V - 7.5k\Omega \times 0.495 \text{ mA}$$

$$= 1.29 \text{ V}$$
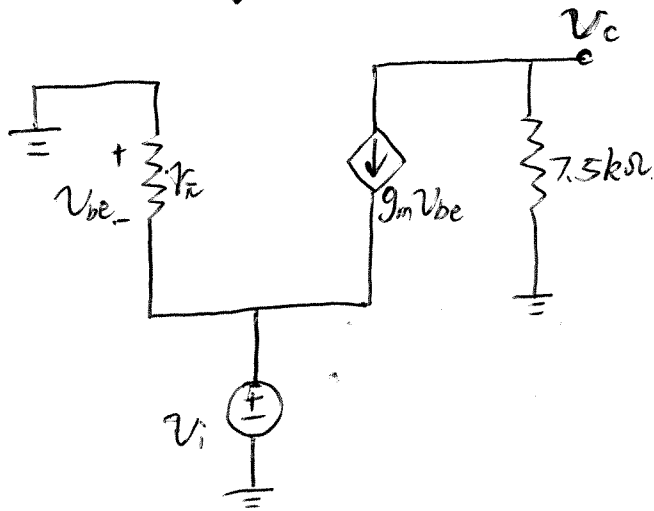
$$g_m = \frac{I_C}{V_T} = \frac{0.495 \text{ mA}}{25 \text{ mV}} = 0.0198 \text{ A/V}$$



Observe that $V_{be} = -v_i$

The output voltage v_c is found to be

$$v_c = -g_m v_{be} \times 7.5 \text{ k}\Omega$$



⇒ The voltage gain is

$$\frac{v_c}{v_i} = \frac{-g_m v_{be} \times 7.5 \text{ k}\Omega}{-v_{be}}$$

$$= g_m \times 7.5 \text{ k}\Omega$$

$$= 148.5 \text{ V/V}$$

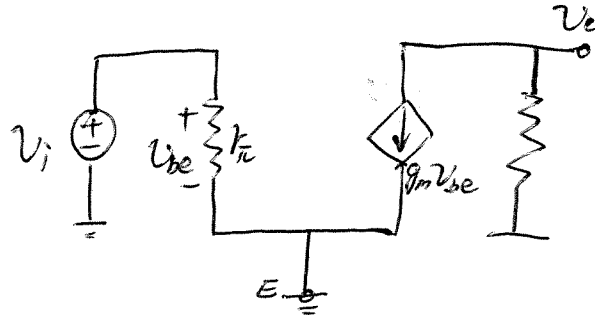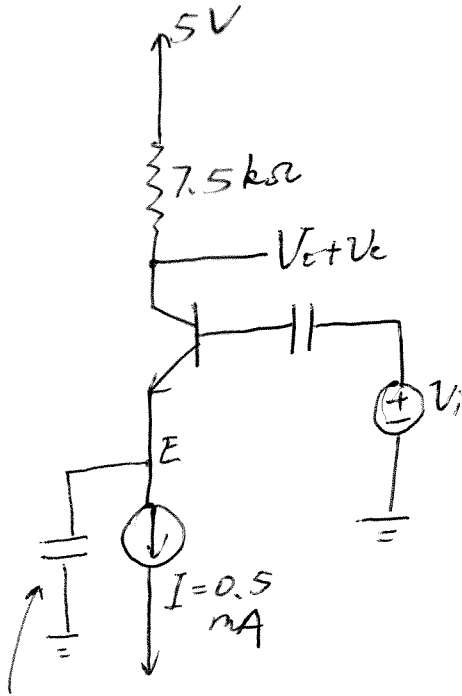(b) Now move the voltage source V_i and its capacitor onto the base



$$V_c = -g_m V_{be} \times 7.5 \text{ k}\Omega$$

$$\text{Now } V_i = V_{be}$$


$$\Rightarrow \frac{V_c}{V_i} = \frac{-g_m V_{be} \times 7.5 \text{ k}\Omega}{V_{be}}$$

$$= -g_m \times 7.5 \text{ k}\Omega$$

$$= -148.5 \text{ V/V}$$

bypass capacitor to provide shortcircuit to ground, see PP. 467, or else use R_e , which we do not know the value here.

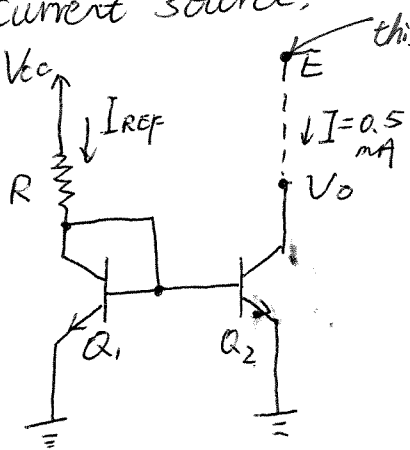(c) To replace the ideal current source with a simple BJT current source, see PP. 569 Figure 6.10.



Q_1 and Q_2 are matched BJT with $\beta = 100$, $I_o = 0.5 \text{ mA}$

From (6.26), ignore V_A term

$$I_o = \frac{I_{REF}}{1 + \frac{2}{\beta}} \quad \left(\frac{2}{\beta} \text{ is due to two base currents to } Q_1 \text{ and } Q_2 \right)$$

$$\Rightarrow I_{REF} = I_o \left(1 + \frac{2}{\beta} \right) = 0.5 \text{ mA} \times \left(1 + \frac{2}{100} \right) = 0.51 \text{ mA}$$

From (6.25)


$$I_{REF} = \frac{V_{CC} - V_{BE}}{R} = 0.5 \text{ mA}$$

∴ For a given V_{CC} , we can calculate R

For example, For $V_{CC} = 5V$,

$$R = \frac{V_{CC} - V_{BE}}{0.5 \text{ mA}} = \frac{(5 - 0.7) V}{0.5 \text{ mA}} = 8.43 \text{ k}\Omega$$

2. (a)

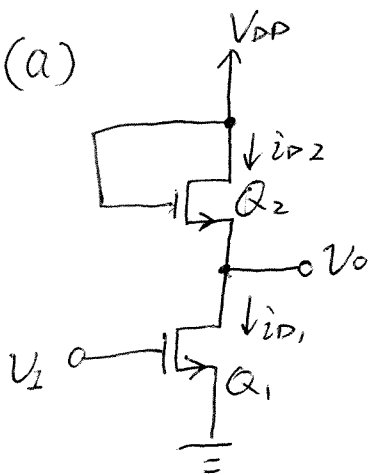

Q_2 is always in saturation

For $V_{t1} \leq V_i \leq V_o + V_{t1}$, Q_1 is also in saturation.

For Q_1 , $V_{gs1} = V_i$

$$I_{D1} = \frac{1}{2} K_n' \frac{W_1}{L_1} (V_i - V_t)^2$$

For Q_2 , $V_{gs2} = V_{DD} - V_o$, $I_{D2} = \frac{1}{2} K_n' \frac{W_2}{L_2} (V_{DD} - V_o - V_t)^2$

$$I_{D1} = I_{D2} \Rightarrow \frac{1}{2} K_n' \frac{W_1}{L_1} (V_i - V_t)^2 = \frac{1}{2} K_n' \frac{W_2}{L_2} (V_{DD} - V_o - V_t)^2$$


$$\Rightarrow \sqrt{\frac{W_1}{L_1}} (V_i - V_t) = \sqrt{\frac{W_2}{L_2}} (V_{DD} - V_o - V_t)$$

$$\Rightarrow V_o = V_{DD} - V_t + \sqrt{\frac{(W/L)_1}{(W/L)_2}} V_t - \sqrt{\frac{(W/L)_1}{(W/L)_2}} V_i$$


For $(W/L)_1 = \frac{50 \mu\text{m}}{0.5 \mu\text{m}}$, $(W/L)_2 = \frac{5 \mu\text{m}}{0.5 \mu\text{m}}$, The voltage gain is

$$\frac{V_o}{V_i} = - \sqrt{\frac{(W/L)_1}{(W/L)_2}} = - \sqrt{10} = -3.16$$

(b)

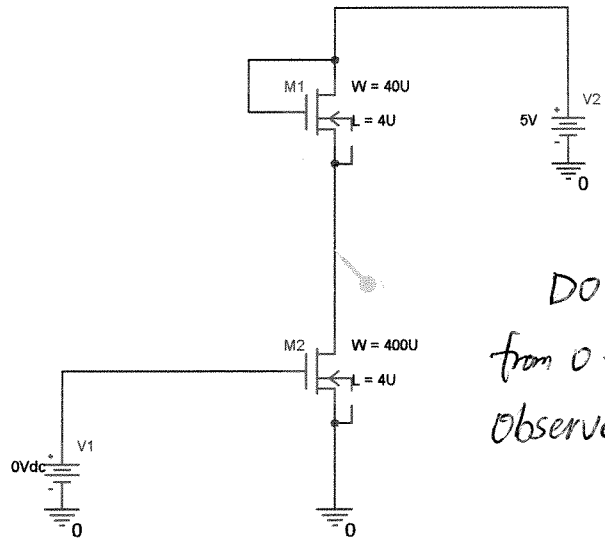

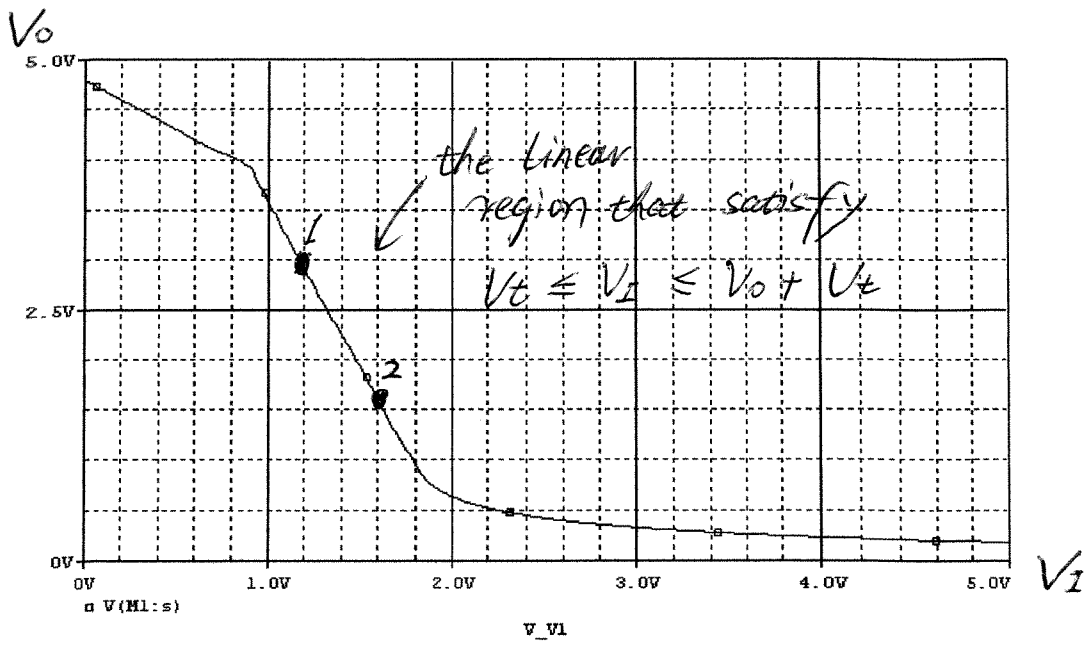DO a DC sweep from 0 - 5V on V_I , observe V_o .



Choose two points from the region $V_t \leq V_I \leq V_o + V_t$

$$\begin{aligned}
 V_{I1} = 1.2V \quad V_{o1} = 2.92V \\
 V_{I2} = 1.6V \quad V_{o2} = 1.62V \quad \Rightarrow \quad \frac{\Delta V_o}{\Delta V_I} = -3.25
 \end{aligned}$$

Agrees well with predicted value -3.16

3. The small-signal model for NMOS (PP. 297)

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 90 \times 10^{-6} \times \frac{20}{2} \times 100 \times 10^{-6}}$$

$$= 4.24 \times 10^{-4} \text{ A/V}$$

$$V_A = 16 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = \frac{16 \text{ V}}{100 \times 10^{-6} \text{ A}} = 160 \text{ k}\Omega$$

$$\chi = \frac{\gamma}{2 \sqrt{2 \phi_f + V_{SB}}} = \frac{0.5}{2 \sqrt{2 \times 0.34 + 1}} = 0.193$$

$$g_{mb} = \chi g_m = 0.193 \times 4.24 \times 10^{-4} = 8.2 \times 10^{-5} \text{ A/V}$$

$$g_m = \frac{2 I_D}{V_{ov}} \Rightarrow V_{ov} = \frac{2 \times 10^{-4}}{4.24 \times 10^{-4}} = 0.48 \text{ V}$$

The small-signal model for PMOS

$$g_m = \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 30 \times 10^{-6} \times \frac{20}{2} \times 100 \times 10^{-6}}$$

$$= 2.45 \times 10^{-4} \text{ A/V}$$

$$V_A = 24 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = \frac{24 \text{ V}}{100 \times 10^{-6} \text{ A}} = 240 \text{ k}\Omega$$

$$\chi = 0.193$$

$$g_{mb} = 0.193 \times 2.45 \times 10^{-4} = 4.7 \times 10^{-5} \text{ A/V}$$

$$V_{ov} = \frac{2 \times 0.1}{0.24} = 0.83 \text{ V}$$