

1.

a). For PMOS, $|V_{gs}|_p = V_{dd} - V_o$, $|V_{ds}|_p = V_{dd} - V_o$.

(13) For NMOS, $V_{gsn} = V_o$, $V_{dsn} = V_o$

$$I_{DP} = I_{DN} \Rightarrow$$

$$\frac{1}{2} k_{PP} \cdot \frac{W_{P0}}{L_P} \cdot (|V_{gs}|_p - |V_{tp}|)^2 =$$

$$\frac{1}{2} k_{PN} \cdot \frac{W_n}{L_n} (V_{gsn} - V_{tn})^2$$

$$\Rightarrow W_{P0} = \frac{k_{PN}}{k_{PP}} \cdot \left[\frac{(|V_{gs}|_p - |V_{tp}|)^2}{(V_{gsn} - V_{tn})^2} \right]^{-1} \cdot W_n$$

$$= 2 \cdot \left[\frac{(V_{dd} - V_o - |V_{tp}|)^2}{(V_o - V_{tn})^2} \right]^{-1} \cdot W_n$$

$$= 2 \cdot \left[\frac{(3 - 1.5 - 1)^2}{(1.5 - 1)^2} \right]^{-1} \cdot W_n$$

$$= 2W_n$$

$$= 20 \mu$$

b). With $\lambda_n = 0.01 V^{-1}$, $|\lambda_p| = 0.02 V^{-1}$

(12) $I_{DP} = I_{DN} \Rightarrow$

$$\frac{1}{2} k_{PP} \cdot \frac{W_{P0}}{L_P} (|V_{gs}|_p - |V_{tp}|)^2 (1 + |\lambda_p| \cdot |V_{ds}|_p)$$

$$= \frac{1}{2} k_{PN} \cdot \frac{W_n}{L_n} (V_{gsn} - V_{tn})^2 (1 + \lambda_n V_{dsn})$$

$$\begin{aligned}
\Rightarrow W_{Pn} &= \frac{k_{Pn}}{k_{Pp}} \frac{(V_{DSn} - V_{tn})^2}{(1 + \lambda_p |V_{DSp}|)^2} \cdot \frac{(1 + \lambda_n V_{DSn})}{(1 + \lambda_p |V_{DSp}|)} \\
&= W_{P0} \cdot \frac{(1 + \lambda_n V_{DSn})}{(1 + \lambda_p |V_{DSp}|)} \\
&= W_{P0} \cdot \frac{(1 + 0.01 \times 1.5)}{(1 + 0.02 \times 1.5)} \\
&= W_{P0} \cdot 0.9854 \\
&= 19.7 \mu
\end{aligned}$$

c). In part b, when we consider the Early effect, the drain voltage has effect on the drain current in the MOS saturation region. This will make the calculation of W_p slightly different from the case where Early effect is ignored.

2. a) At $t=0$,

$$(5) \quad V_a = 5V, \quad V_b = 0V.$$

$V_a > V_b$. For the pass transistor (NMOS)

a is the drain, b is the source.

b) The differential equation for $V_a(t)$ is

$$(15) \quad i_{DN} \cdot dt = -C_{in} dV_a(t)$$

For $V_b(t)$,

$$i_{DN} \cdot dt = C_{out} dV_b(t)$$

In saturation region

$$\begin{aligned} i_{DN} &= \frac{1}{2} K_P \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} K_P \frac{W}{L} \cdot (5 - V_b - V_t)^2 \end{aligned}$$

c) There are two possibilities for the final states of V_a and V_b when charging and discharging are complete.

(15)

Possibility 1: $V_a = V_b$ and $V_b < 4V$

Possibility 2: $V_b = 4V$, and $V_a \geq 4V$

For both possibilities, V_b cannot exceed $4V$.
Because when $V_b \geq 4V$ ($V_{dd} - V_{to} = 4V$),
the nmos pass transistor is shut down
due to $V_{gs} < V_{to}$.

When the charging of C_{out} and discharging
of C_{in} begin, C_{in} keeps discharging, so
 V_a keeps decreasing. The charges that
were initially stored on C_{in} move
towards C_{out} , so V_b keeps increasing.
If before V_b rises to $4V$, V_a has
dropped to the same magnitude of V_b ,
then no charge will move any more since
 $V_a = V_b$. This is one possibility of final
states. But if V_b rises to $4V$ and
 V_a is still larger than V_b , case will be
different. Charges stop moving because
when V_b rises to $4V$, the pass transistor is

shut down. So V_b will be fixed at 4V,
and V_a stays at its own level ($V_a > 4V$).

This case is possibility No. 2.

Which one is the final state in this problem?

This depends on the capacitance values of C_{in} and C_{out} , because these values decide the speed of voltage increase or drop.

Let's start from possibility one, and see if this can happen or not.

From the fact that the total charges on these two capacitors are constant all the time, we have the equation

$$C_{in} \cdot V_a(t=0) = C_{in} \cdot V_a(t_{final}) + C_{out} \cdot V_b(t_{final})$$

charges at the beginning
charges at the end.

If $V_a(t_{final}) = V_b(t_{final})$, we can calculate

$$V_{a,b}(t_{final}) = \frac{C_{in}}{C_{in} + C_{out}} \cdot V_a(t=0) = \frac{20PF}{20PF + 2PF} \times 5$$

$$= 4.54 V > 4V$$

$V_b(t_{\text{final}})$ cannot be larger than 4V from our previous analysis. So possibility one is ruled out.

Let's consider the other possibility,

where $V_b(t_{\text{final}}) = 4V$,

From constant charge, we have

$$C_{in} \cdot V_a(t=0) = C_{in} \cdot V_a(t_{\text{final}}) + C_{out} \cdot 4V$$

$$\Rightarrow V_a(t_{\text{final}}) = -\frac{C_{out}}{C_{in}} \cdot 4V + V_a(t=0)$$

$$= 5 - \frac{1}{10} \times 4V$$

$$= 4.6V$$

This satisfies $V_a > 4V$.


So this possibility is the real final state of the circuit.

$$V_a(\text{final}) = 4.6V$$

$$V_b(\text{final}) = 4V$$

A is the drain, B is the source.

3. a) (25)

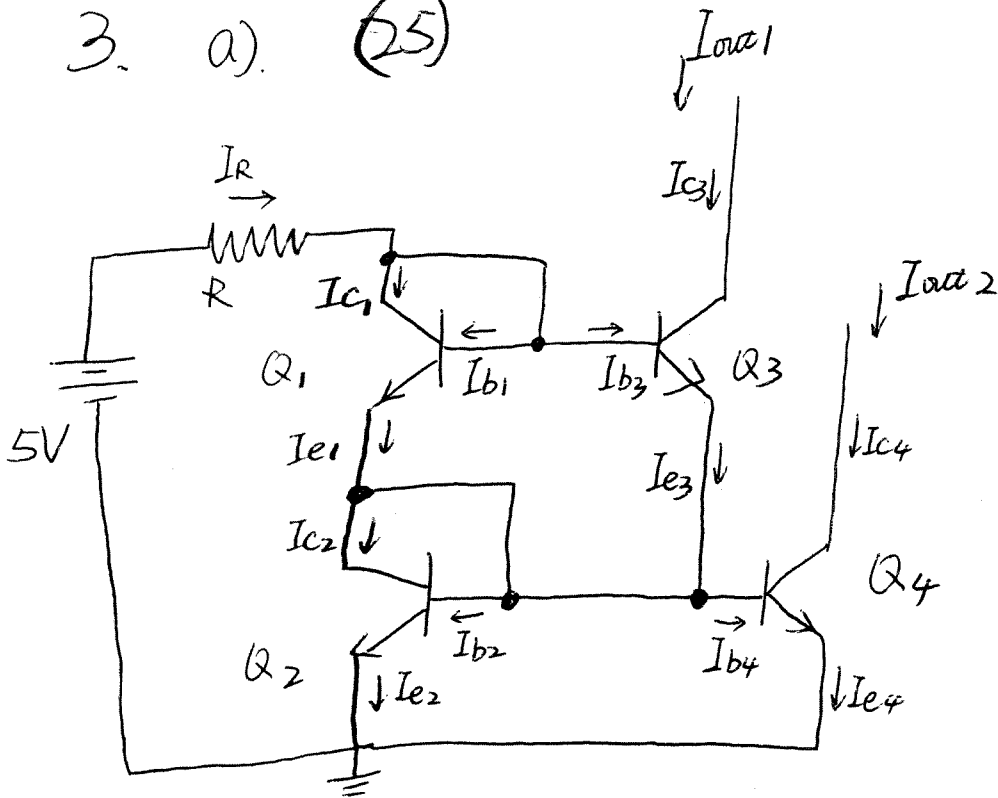

To find R that give $I_{out2} = I_{C4} = 0.2 \text{ mA}$,
 we need to know the current that flows
 through R (I_R) and the voltage drop
 across R (V_R).

To find I_R , see below derivations:

$$I_R = I_{C1} + I_{B1} + I_{B3}$$

$$= I_{C1} + 2I_{B1} \quad (I_{B1} = I_{B3})$$

$$= \left(1 + \frac{2}{\beta}\right) I_{C1} \quad (I_C = \beta I_B)$$

P8

$$= \left(1 + \frac{2}{\beta}\right) \cdot \frac{\beta}{\beta+1} I_{e1} \quad (I_c = \frac{\beta}{\beta+1} I_e)$$

to find I_{e1} , observe for Q_2 and Q_4 , we have

$$I_{e1} + I_{e3} = I_{c2} + I_{b2} + I_{b4},$$

$$\Rightarrow 2I_{e1} = I_{c2} + I_{b2} + I_{b4} \quad (I_{e1} = I_{e3})$$

$$\Rightarrow I_{e1} = \frac{1}{2} (I_{c2} + I_{b2} + I_{b4})$$

$$= \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{c2} \quad (I_{b2} = I_{b4})$$

$$= \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{c4} \quad (I_c = \beta I_b)$$

$$= \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{out2}$$

$$\text{SO } I_R = \left(1 + \frac{2}{\beta}\right) \frac{\beta}{\beta+1} I_{e1}$$

$$= \frac{1}{2} \left(1 + \frac{2}{\beta}\right)^2 \frac{\beta}{\beta+1} I_{out2}$$

$$= \frac{1}{2} \times \left(1 + \frac{2}{5}\right)^2 \cdot \frac{5}{5+1} \times 0.2 \text{ mA}$$

$$= 0.163 \text{ mA}$$

Next step is to find the two diode drop V_{BE1} and V_{BE2} , so we can know the

Voltage drop across R.

to find V_{BE1} , we need to know I_{e1} .

From Previous calculation,

$$I_{e1} = \frac{1}{2} \left(1 + \frac{2}{\beta}\right) I_{out2} = 0.14 \text{ mA}$$

From I_E formula

$$I_e = I_s \cdot \exp\left(\frac{V_{BE}}{V_T}\right) \quad \text{and } V_{BE} = 0.7 \text{ V}$$

\uparrow constant $\Rightarrow I_e = 1 \text{ mA}$

~~$$I_{e1} =$$~~

$$V_{BE1} = V_T \log \frac{I_{e1}}{1 \text{ mA}} + 0.7 \text{ V}$$

$$= 0.026 \log \frac{0.14 \text{ mA}}{1.0 \text{ mA}} + 0.7 \text{ V}$$

$$= 0.649 \text{ V}$$

to find V_{BE2} , we need to know I_{e2} .

$$I_{e2} = \frac{\beta+1}{\beta} I_{c2} = \frac{\beta+1}{\beta} I_{out2} = 0.24 \text{ mA}$$

$$V_{BE2} = V_T \log \frac{0.24 \text{ mA}}{1 \text{ mA}} + 0.7 \text{ V} = 0.663 \text{ V}$$

So, Voltage drop on R is

$$V_R = 5 - V_{BE1} - V_{BE2} = 5 - 0.649 - 0.663$$

$$= 3.688 \text{ V}$$

$$\text{So } R = \frac{V_R}{I_R} = \frac{3.688 \text{ V}}{0.163 \text{ mA}} = 22.62 \text{ k}\Omega.$$

$$\text{b). } I_{\text{out}1} = I_{C3} = I_{C1} = \frac{\beta}{\beta+1} I_{e1}$$

$$\text{(5)} \quad = \frac{5}{6} \times 0.14 \text{ mA}$$

$$= 0.117 \text{ mA}$$