


ENEE 303 Spring 2006 final

Open book, open notes, 100 points. If stuck go on to the next problem.

Unless otherwise stated assume complete complementarity with $KP_n=KP_p=KP=10^{-4}$ A/V², $VTO_n=-VTO_p=1$ V, $\lambda_{n,p}=\lambda=0.01$, $W=L=10\mu\text{M}$, $C_{gs}=C_{gd}=1\text{pF}$, $V_{dd}=-V_{ss}=5$ V.

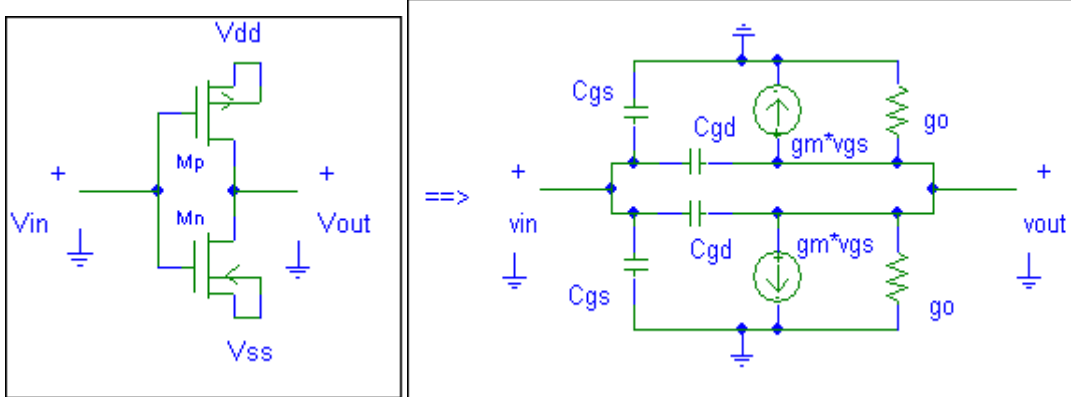1. (50 points, 40 minutes)

Recently the inverter has become important for small signal use. Thus, consider the following inverter (on the left) for which the admittance equivalent circuit of each component is given on the right.



- Combine all the parallel components of the equivalent circuit and draw the 2-port result. Then give the 2x2 admittance matrix $Y(s)$ for the resulting 2-port.
- Note that the bias $V_{in}=V_{out}=0$ V. Determine the bias drain currents and the resulting g_m and g_o .
- Load the inverter in a capacitor C_L to ground and find the resulting transfer function $V_{out}(s)/V_{in}(s)$.

2. (50 points, 40 minutes)

For DC operation of the following circuit find V_{out} versus I_{in} . Use the Ebers-Moll model (page 409) exponential behavior of the BJT at room temperature with $I_{SE}=10^{-12}$ A; assume an open-circuit load.

a) Sketch V_{out} versus I_{in} assuming M2 is in saturation.

b) Discuss the range of validity of the assumption of a) and give the equations to solve to determine the limits of I_{in} to insure M2 is in saturation.

