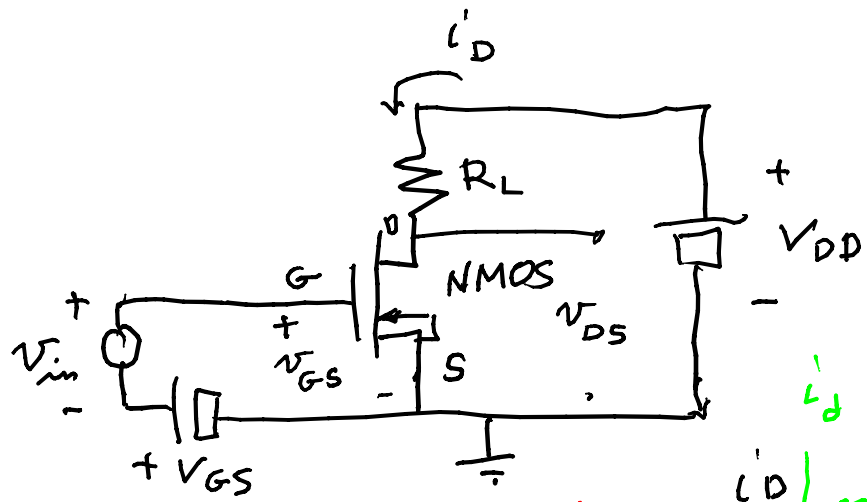


# Common source amplifiers

EE303  
02/06/06



$0 \leq |v_{in}(t)| \ll V_{GS}$   
 $V_{DD} > 0$   
 $V_{GS} \rightarrow V_{T0}$

$$i_D = f(v_{DS}, v_{GS})$$



$$v_{DS} = -R_L i_D + V_{DD}$$

$$i_D = (V_{DD} - v_{DS}) \cdot G_L$$

$$G_L = 1/R_L$$

$$v_{GS} = V_{GS} + v_{in} \quad \text{if} \quad v_{in} = V_{in} \sin \omega_0 t; \quad |V_{in}| \ll V_{GS}$$

small signal

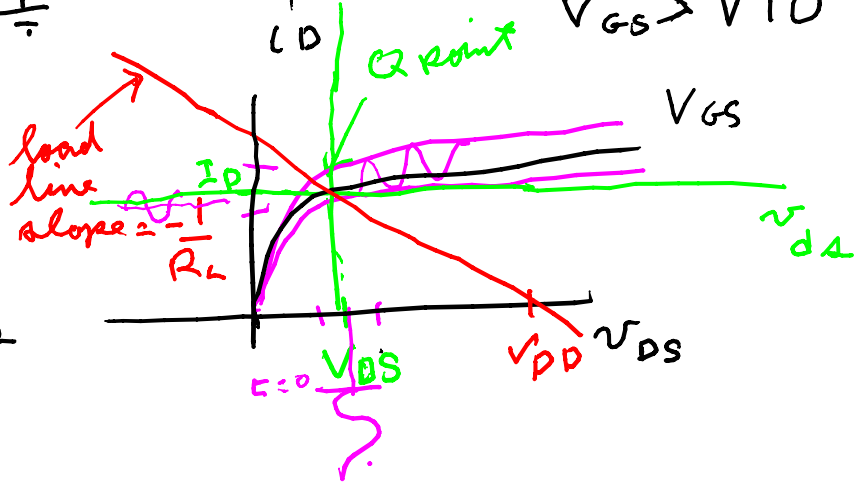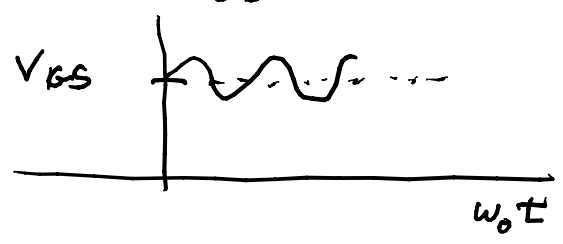

$$i_D(v_{DS}, v_{GS}) = i_D = i_D(v_{DS}, V_{GS}) + \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} (v_{GS} - V_{GS}) + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{v_{DS}=V_{DS}} (v_{DS} - V_{DS})$$


Q point

drop for small signals  $\Rightarrow$  linear behavior

$$+ \frac{\partial^2 i_D}{\partial v_{GS} \partial v_{DS}} (v_{GS} - V_{GS}) + \dots$$

$$i_D = I_D + \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q (v_{gA}) + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q (v_{dA})$$

$$i_d = g_m v_{gA} + g_o v_{dA}$$

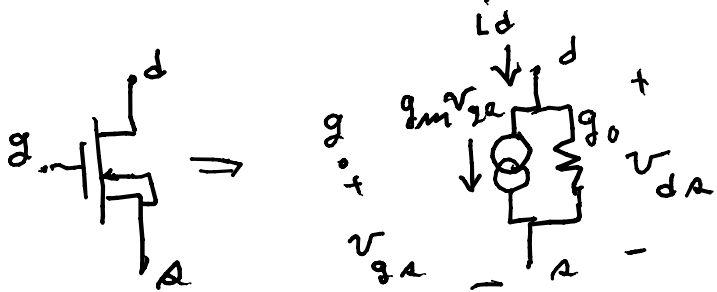


here  $i_d = i_D - I_D$

$$v_{gA} = v_{GS} - V_{GS}$$

$$v_{dA} = v_{DS} - V_{DS}$$

↑ signal      ↑ total      ↑ bias

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q \quad ; \quad g_o = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q$$

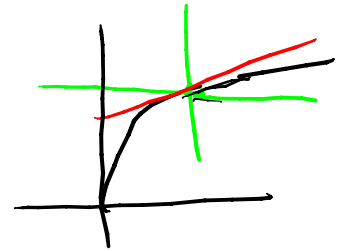


if in saturation;  $v_{GS} - V_{TO} \leq v_{DS}$

then 
$$i_D = \frac{K_P \cdot W}{2 \cdot L} (v_{GS} - V_{TO})^2 (1 + \lambda v_{DS})$$

$$\lambda = \frac{1}{V_A} \frac{V_A}{V_{TO}}$$


$$\left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = \left( \frac{K_P \cdot W}{2 \cdot L} \right) \cdot 2 (v_{GS} - V_{TO}) (1 + \lambda v_{DS})$$

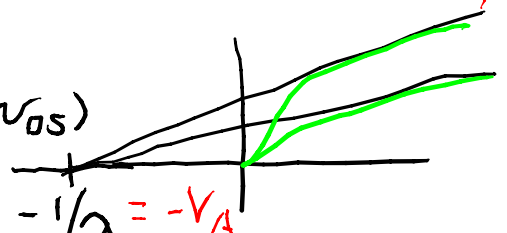

$$\left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = g_m = \frac{\left( \frac{K_P \cdot W}{2 \cdot L} \right)^2 (V_{GS} - V_{TO}) (1 + \lambda V_{DS})}{2 \cdot I_D} = \frac{2 \cdot I_D}{(V_{GS} - V_{TO})}$$

$$\left. \frac{\partial I_D}{\partial V_{DS}} \right|_Q = \lambda \left( \frac{K_P}{2} \frac{W}{L} \right) (V_{GS} - V_{T0})^2 = \frac{\lambda I_D}{(1 + \lambda V_{DS})} \approx \lambda I_D$$

amplifier becomes for small signals

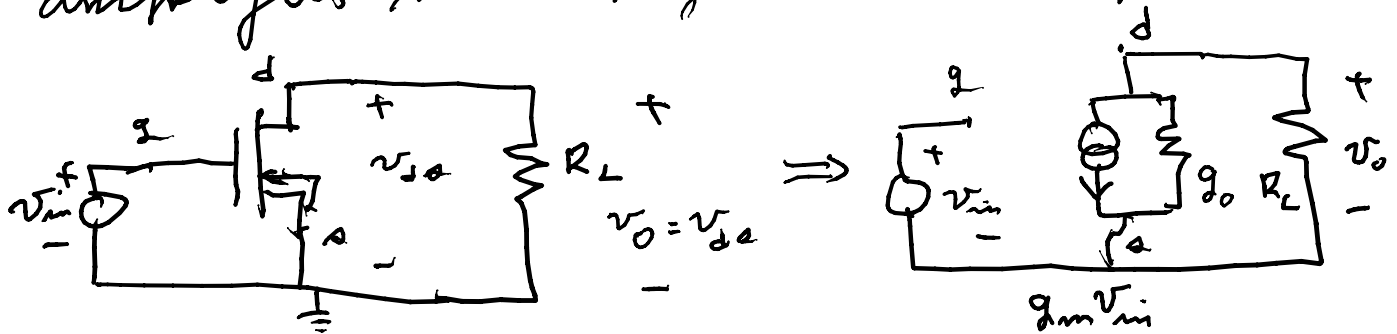

now linear

$$\frac{v_o}{v_{in}}: v_o = -(g_m v_{in}) \left( \frac{r_o R_L}{r_o + R_L} \right) \approx -g_m R_L \cdot v_{in}$$

if  $g_o \approx 0 \Rightarrow r_o = \frac{1}{g_o} = \infty$

$$\frac{v_o}{v_{in}} \approx -g_m R_L$$

small signal gain  
at small  $\omega$   
(as ignored input capacitance)

Typical:

$$K_P = 1 \times 10^{-5} \frac{A}{V^2}, \quad W = L = 10 \mu = 10 \mu$$

$$V_{T0} = 0.8 \text{ V}$$

$$\lambda = 0.01$$

$$V_{GS} = 3 \text{ V}, \quad V_{DS} = 4 \text{ V}$$

$$g_m: I_D = \frac{1}{2} \times 10^{-5} \times \frac{1}{1} (3 - 0.8)^2 (1 + 0.01 \times 4)$$

$$= \frac{(2.2)^2}{2} \times 1.04 \times 10^{-5} = 2.517 \times 10^{-3} \times 10^{-2} = 0.025 \text{ mS}$$

$$\text{gain} \approx -2: \text{ then } R_L = 2/g_m = 0.8 \text{ k}\Omega$$

