

EE303  
02/08/06


4007 transistor Spice models

```
.model nch mnmos(Level=1 Tox=300n Uo=600 Kp=20.54u W=144u L=8u Vto= 1.3
+      Lambda=15m Cbd=4p Cbs=4p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
.model pch pmos(Level=1 Tox=300n Uo=300 Kp=10.32u W=328u L=8u Vto=-1.5
+      Lambda=15m Cbd=8p Cbs=8p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
```

note differences in  $K_P$  &  $W$  between N & P devices

for the 4007 NMOS


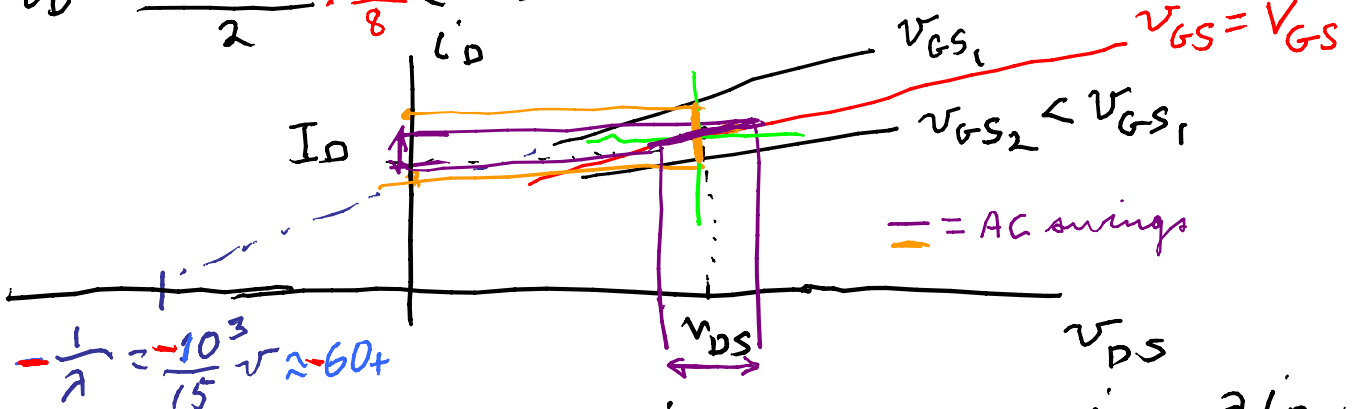
$$i_D = \frac{20.54 \times 10^{-6}}{2} \times \frac{144}{8} (V_{GS} - 1.3)^2 (1 + 15 \times 10^{-3} V_{DS}) \text{ in saturation}$$






$$g_m = \frac{i_D}{v_{gs}} = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{DS}=V_{DS}, V_{GS}=V_{GS}}$$

$$g_o = \frac{i_D}{v_{ds}} = \left. \frac{\partial i_D}{\partial V_{DS}} \right|_{V_{DS}=V_{DS}, V_{GS}=V_{GS}}$$

$\approx \frac{I_D}{V_{GS}}$  Q point

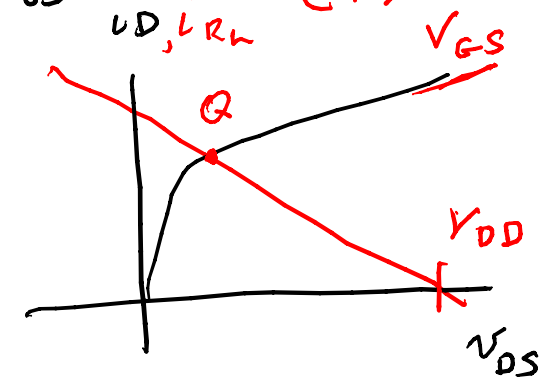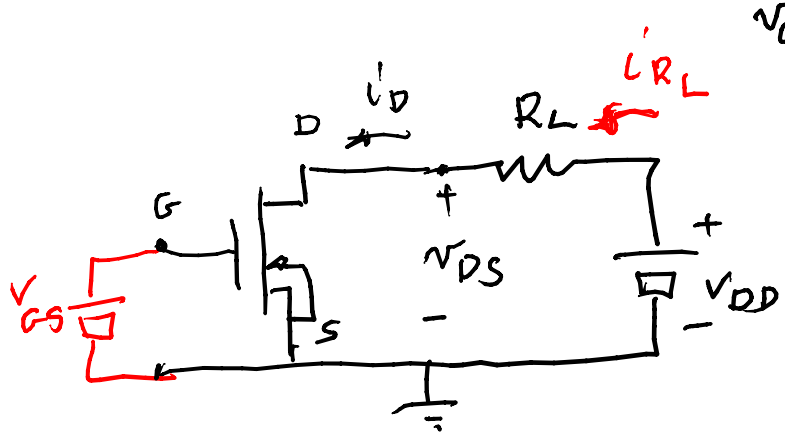

small signal

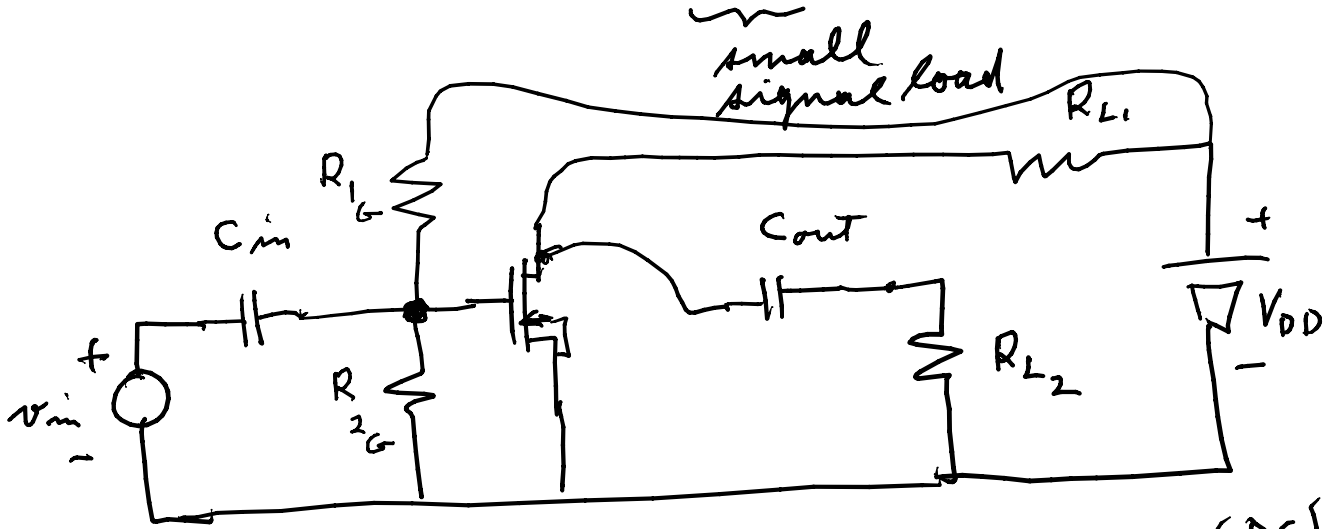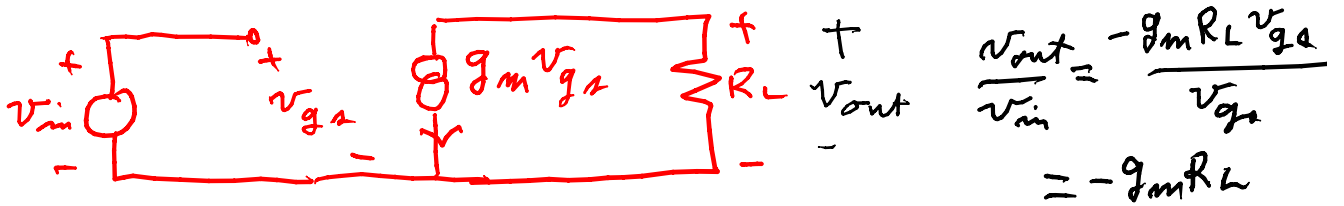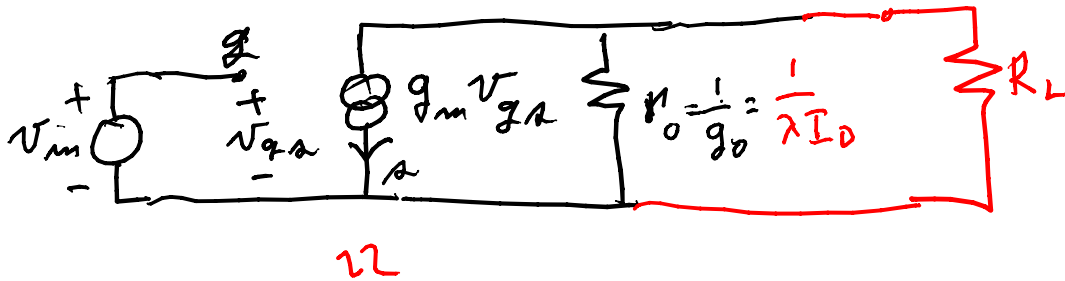

open @ DC  $\Rightarrow Z_{C_{out}} = \frac{1}{s C_{out}} @ s=0 (DC) \approx \infty = \text{open circuit @ DC}$

choose  $C_{in}$  &  $C_{out}$  very large  
 so @ freq. of  $v_{in}(t) = V_{in} \sin(\omega t)$   
 $\omega = 2\pi f$

has  $|Z_C(j\omega)| \ll 1 \Rightarrow \text{short @ AC}$

now for  $g_m R_L = g_m \left[ \frac{R_{L1} R_{L2}}{R_{L1} + R_{L2}} \right] \parallel (R_{1G} + R_{2G}) \approx g_m R_{L||}$

$$V_{GS} = \left( \frac{R_{2G}}{R_{1G} + R_{2G}} \right) V_{DD}$$

choose  $R_{1G}$  &  $R_{2G}$  very large

(note the transistor gate looks like a capacitor at DC  $\Rightarrow$  open circuit for bias, so no DC gate current  $\Rightarrow R_{1G}$  &  $R_{2G}$  act as a voltage divider for bias)

