

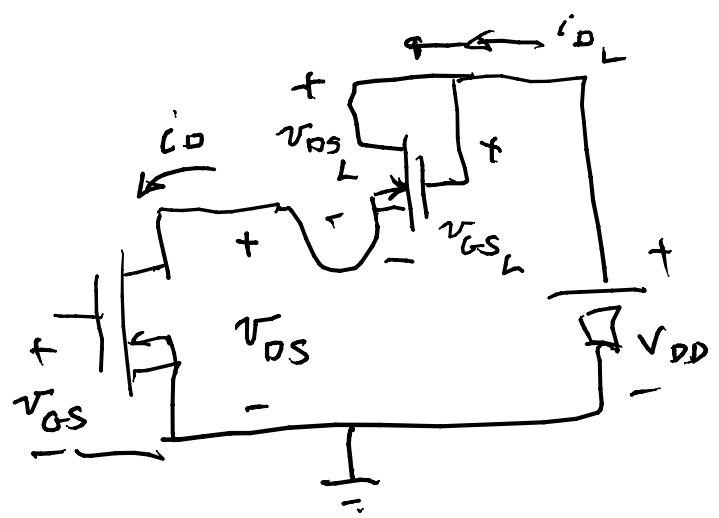
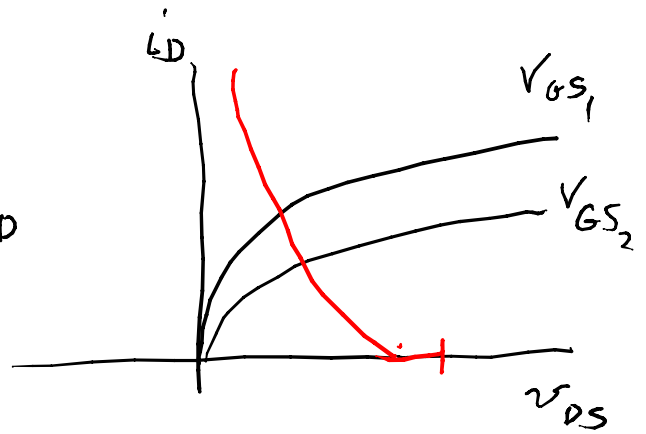


EE303


02/13/06

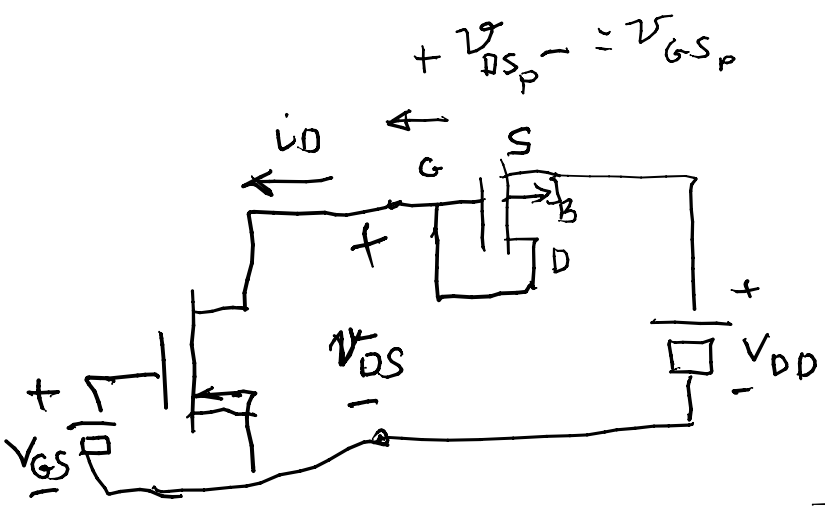

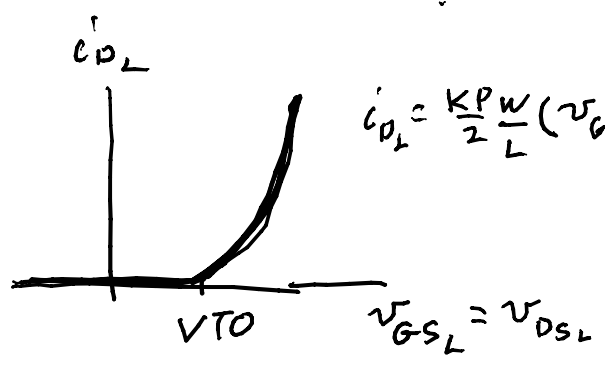$v_{GS_L} = v_{DS_L}$   
 in sat if  
 $0 \leq v_{GS_L} - V_{T0} \leq v_{DS_L}$   
 if on true if  $v_{GS_L} = v_{DS_L}$






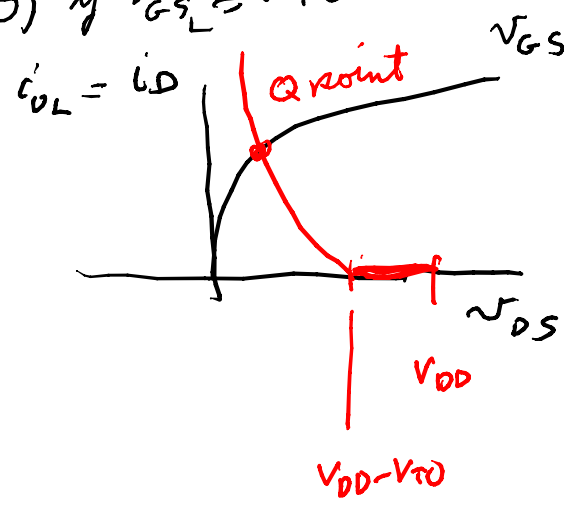
$$i_{D_L} = \frac{K_P W}{2 L} (v_{GS_L} - V_{T0})^2 \text{ if } v_{GS_L} \geq V_{T0}$$




$$i_{D_L} = i_D$$





$$v_{DS} = V_{DD} - v_{DS_L}$$

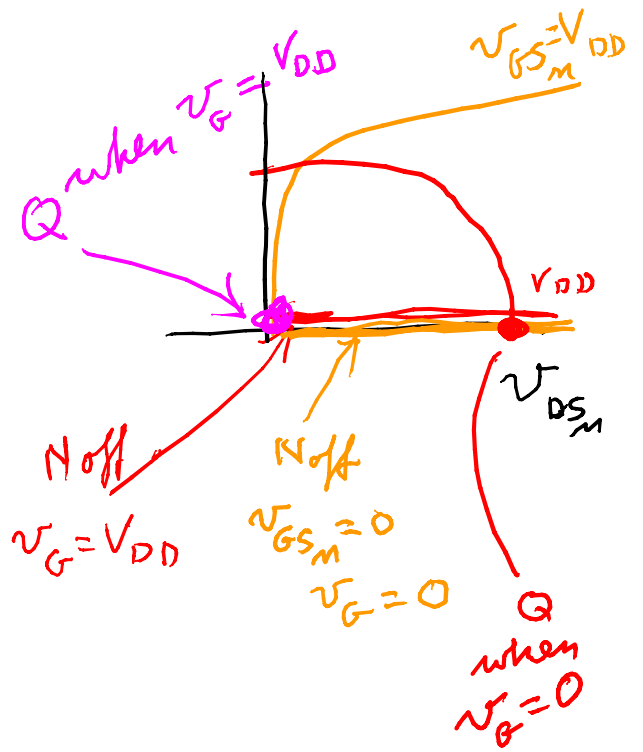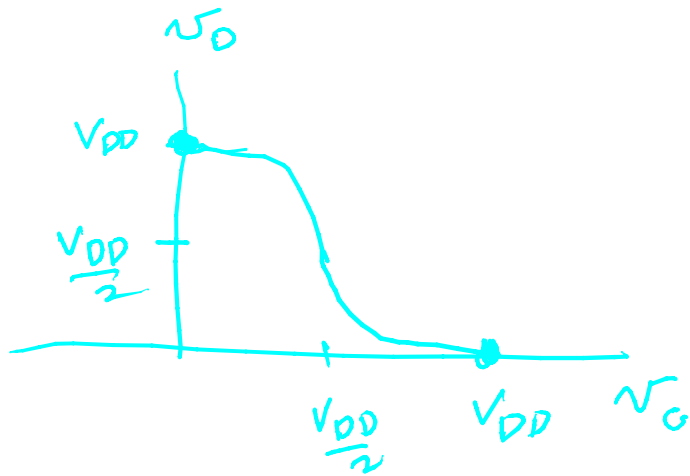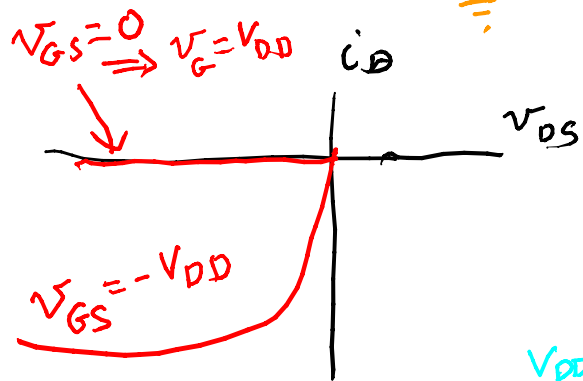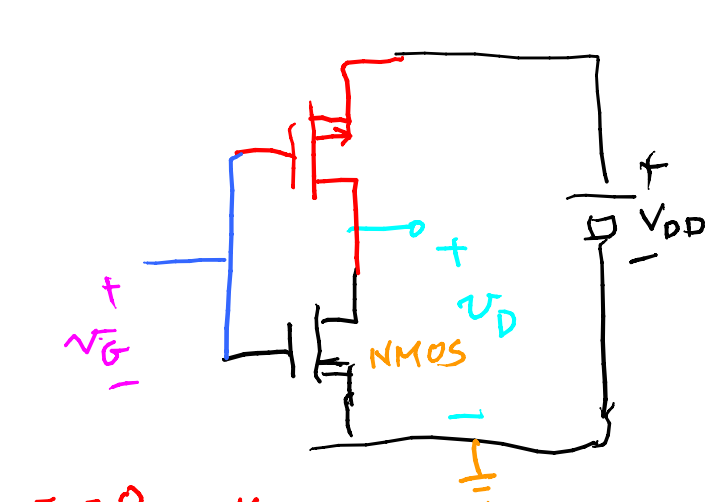

Current Mirrors

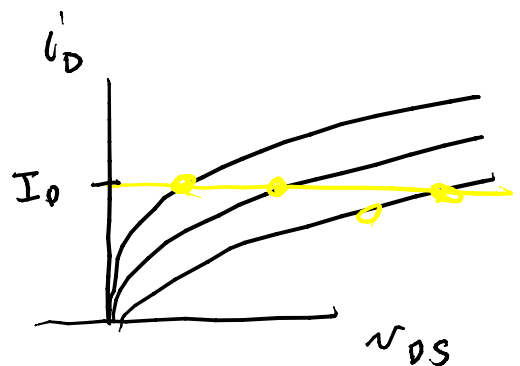


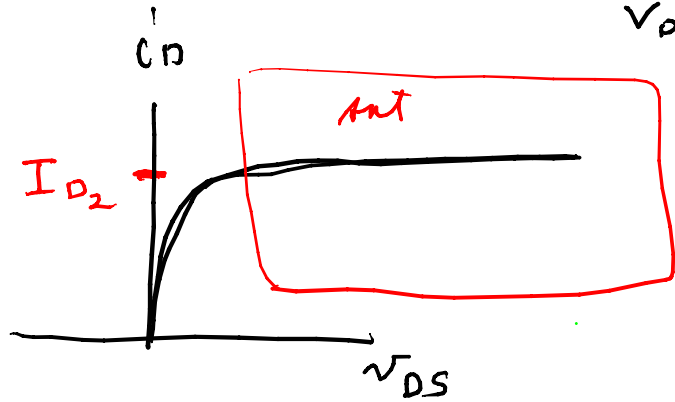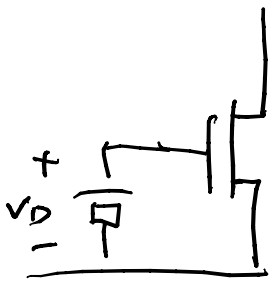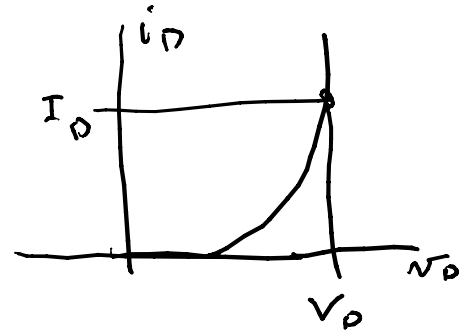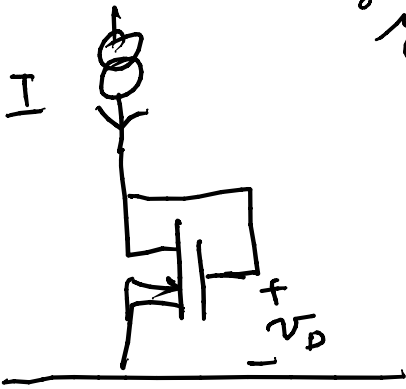connect D-G gives a single valued  $v$  vs  $i$   
if a diode connected MOS is on




$$I_{D2} = \frac{K_P}{2} \frac{W}{L} (V_{GS} - V_{TO})^2$$

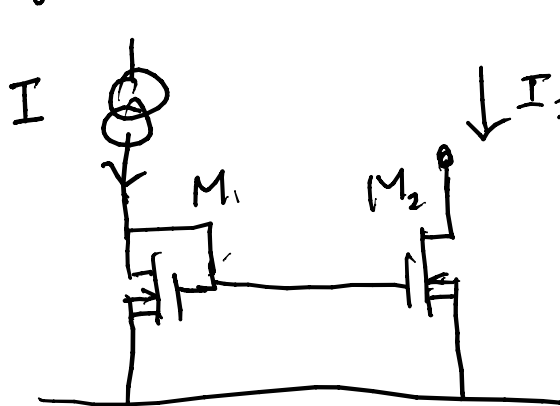if stay in saturation on  $M_2$  then  $I_2$  mirrors  
the first





$$I_2 = \left( \frac{(W/L)_2}{(W/L)_1} \right) I_1$$





a current  
sink (mirror)

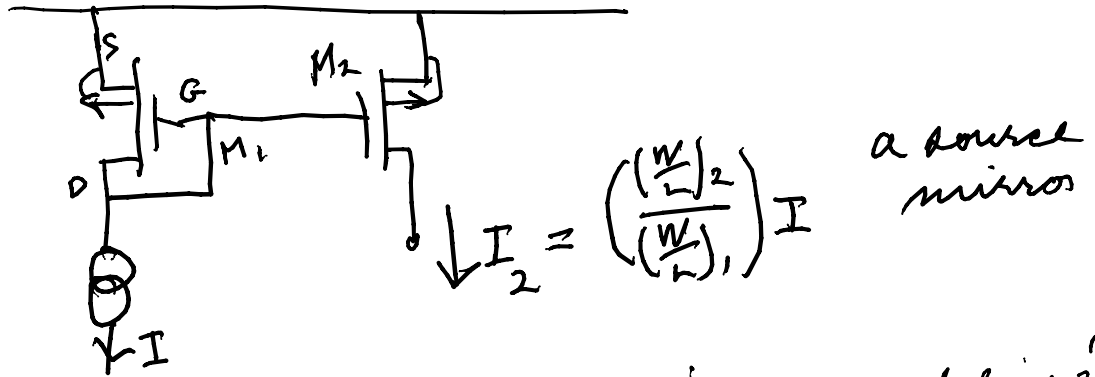

BJT

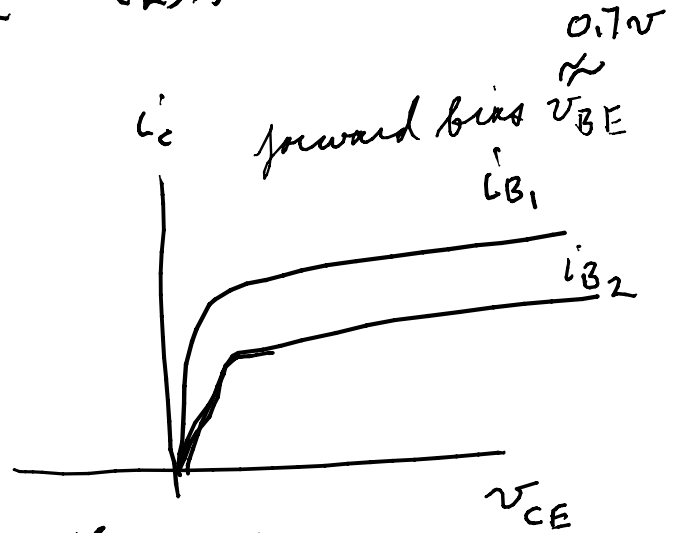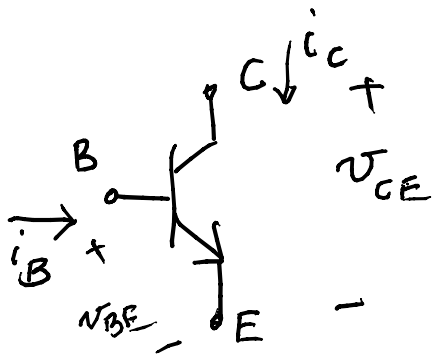

current controlled current source

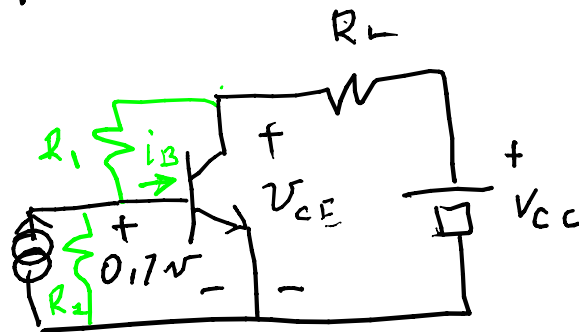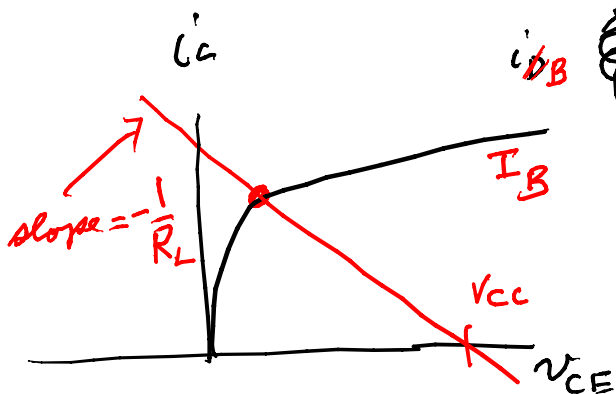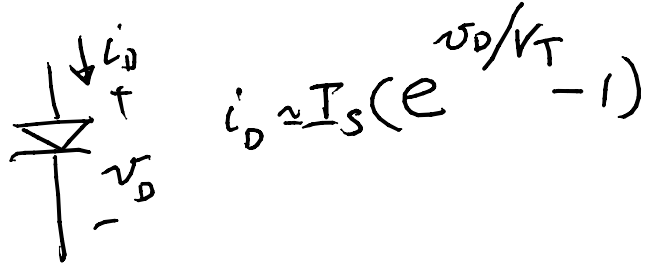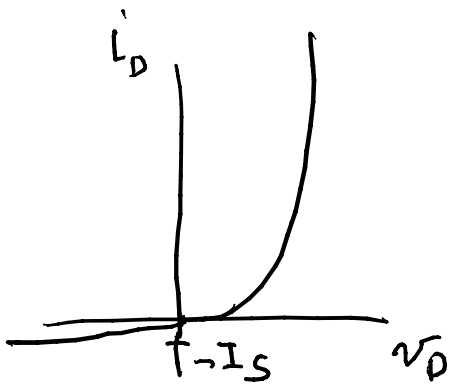

$i_B \neq 0$  so  $R_1$  &  $R_2$  not quite a voltage divider  $\Rightarrow R_2$  has 0.7V DC on it and  $I_B + I_{R_2}$  flows in  $R_1$  for biasing

