

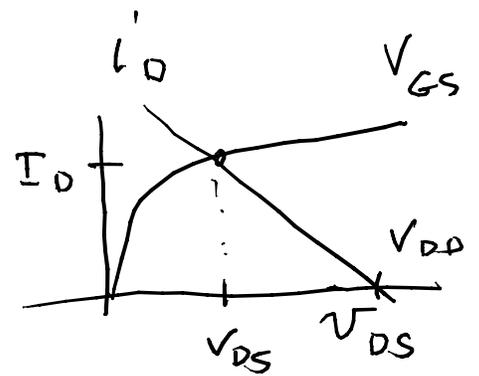
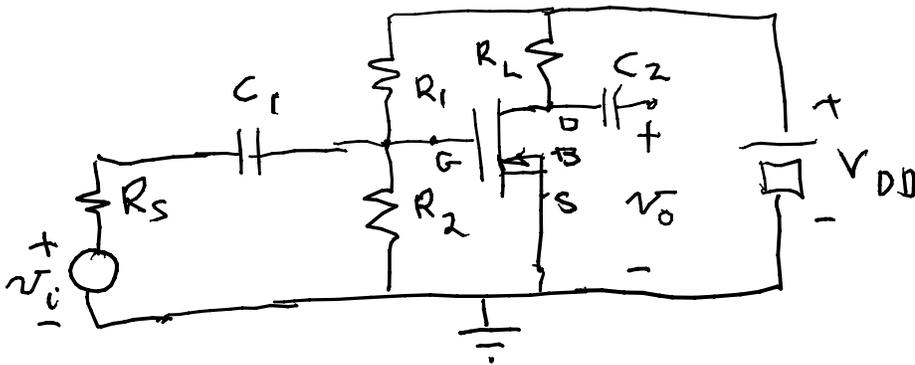


EE303
02/15/06

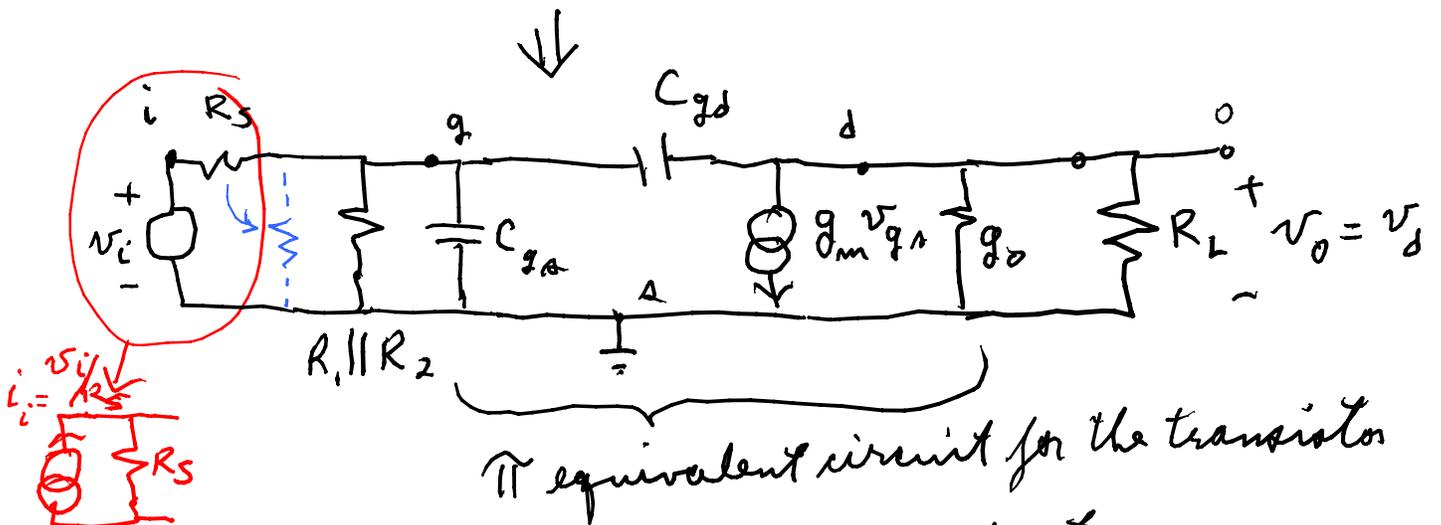

for small signals; equivalent circuit

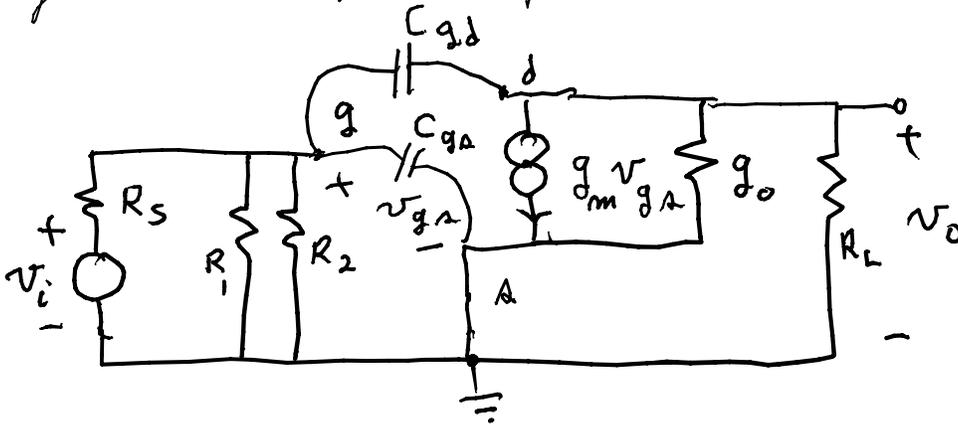


as $\text{freq} \rightarrow \infty$, the capacitors become shorts
 $v_o \rightarrow 0$

$$i_i' = y_{11} v_i + y_{12} v_o = \left[y_{11} \left(-\frac{y_{22}}{y_{21}} \right) + y_{12} \right] v_o = \frac{-\det Y}{y_{21}} \cdot v_o$$

$$\frac{v_o}{i_i'} = \frac{y_{21}}{-\det Y_{\text{nodal}}} = - \left(\frac{g_m - \alpha C_{gd}}{\det Y_{\text{nodal}}} \right) \quad \det Y = y_{11} y_{22} - y_{12} y_{21}$$

Notes added after class

$$y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0} \Rightarrow \text{short at port 1} = g$$

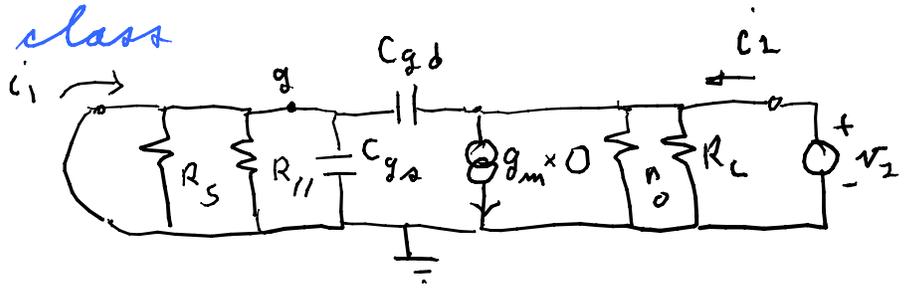

$$= g_o + G_L + \alpha C_{gd} = G_o + \alpha C_{gd}$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = \frac{\text{current in } C_{gd} \text{ (left to right)}}{\text{voltage on } C_{gd} \text{ (+ on right, - on left)}} = -\alpha C_{gd}$$

[as no current in R_S , R_{11} or C_{gs} with 0 volts on them]

$$\therefore Y_{\text{nodal}}(s) = \begin{bmatrix} G_{in} + \alpha(C_{gs} + C_{gd}) & -\alpha C_{gd} \\ g_m - \alpha C_{gd} & G_o + \alpha C_{gd} \end{bmatrix} \quad \begin{array}{l} \text{where} \\ G_{in} = G_S + G_{11} \\ G_o = g_o + G_L \end{array}$$

and

$$\det Y = y_{11} y_{22} - y_{12} y_{21} = [G_{in} + \alpha(C_{gs} + C_{gd})][G_o + \alpha C_{gd}] - (-\alpha C_{gd})(g_m - \alpha C_{gd})$$

$$= G_{in} G_o + \alpha [G_{in} C_{gs} + G_o (C_{gs} + C_{gd}) + g_m C_{gd}] + \alpha^2 C_{gs} C_{gd}$$

$$\therefore \frac{v_o}{v_i} = \frac{1}{R_S} \frac{v_o}{i_i'} = \frac{1}{R_S} \cdot \frac{-y_{21}}{\det Y} = T(s)$$

$$= \frac{-g_m + s C_{gd}}{R_S (C_{gs} C_{gd} s^2 + [G_{in} C_{gs} + G_o (C_{gs} + C_{gd}) + g_m C_{gd}] s + G_{in} G_o)}$$

as a check, at DC where $s=0$

$$T(0) = \frac{-g_m}{R_S \cdot G_{in} G_o}$$

and if $g_o \ll G_L$, $G_{in} \ll G_S$

$$= \frac{-g_m}{R_S \cdot \frac{1}{R_S} \cdot \frac{1}{R_L}} = -g_m R_L$$