

EE 303
02/17/06

$$T(s) = \frac{-g_m + sC_{gd}}{R_S (C_{gs}C_{gd} s^2 + [G_{in}C_{gs} + G_o(C_{gs} + C_{gd}) + g_mC_{gd}] s + G_{in}G_o)}$$


$$= \frac{C_{gd}}{R_S C_{gs} C_{gd}} \left[\frac{s - g_m/C_{gd}}{s^2 + \left[G_{in} \frac{1}{C_{gd}} + G_o \left(\frac{1}{C_{gd}} + \frac{1}{C_{gs}} \right) + \frac{g_m}{C_{gs}} \right] s + \frac{G_{in} G_o}{C_{gd} C_{gs}}} \right]$$

$$= \frac{K (s - \sigma_0)}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$\omega_0 = \sqrt{\frac{G_{in} G_o}{C_{gd} C_{gs}}} = \text{undamped natural radian frequency}$$

$$= 2\pi f_0$$

$Q =$ quality factor

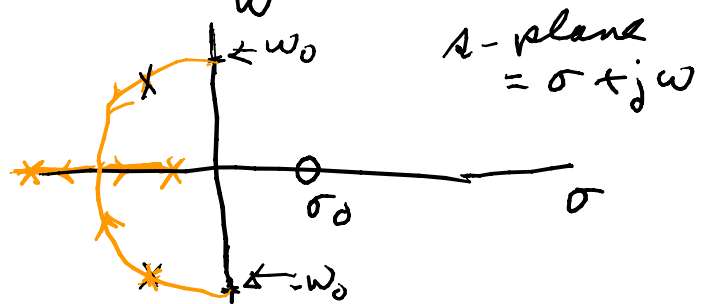

let $C_{gs} = 2 \text{ pF}$, $C_{gd} = 1 \text{ nF}$

$R_S = 50 \Omega$, $R_1 = R_2 = 10 \text{ Meg} \Omega \Rightarrow R_{||} = \frac{1}{2} 10 \text{ Meg} \Omega = 5 \text{ meg}$

$G_{in} = \frac{R_S + R_{||}}{R_S R_{||}} \approx \frac{R_{||}}{R_S R_{||}} = \frac{1}{R_S}$; $g_m = 10^{-3} \text{ S}$

$g_o = \frac{1}{1 \text{ Meg} \Omega}$; $R_L = 10 \text{ K} \Omega$

$G_o = \frac{1 \text{ Meg} + 10 \text{ K} \Omega}{1 \text{ Meg} \cdot 10 \text{ K} \Omega} \approx \frac{1}{10 \text{ K} \Omega} = \frac{1}{100} = 10^{-2}$

$$K = \frac{1}{R_s C_{gs}} = \frac{1}{50 \times 2 \times 10^{-12}} = \frac{10^2 \times 10^{10}}{100} = 10^{10}$$

$$\frac{g_m}{C_{gd}} = \frac{10^{-3}}{1 \times 10^{-12}} = 10^9$$

$$\begin{aligned} \frac{G_{in}}{G_{gd}} \cdot \frac{G_0}{C_{gs}} &= \frac{1}{50 \times 1 \times 10^{-12}} \times \frac{10^{-2}}{2 \times 10^{-12}} = \frac{1}{5} \times 10^{-3} \times (10^{12})^2 \\ &= 2 \times (10^{-2})^2 (10^{12})^2 = 2 \times 10^{20} \end{aligned}$$

$$\omega_0 = \sqrt{2 \times 10^{20}} = \sqrt{2} \times 10^{10}$$

$$\begin{aligned} \frac{G_{in}}{C_{gd}} + G_0 \left(\frac{1}{C_{gd}} + \frac{1}{C_{gs}} \right) + \frac{g_m}{C_{gs}} &= \frac{10^{12}}{50} + 10^{-2} \left(\frac{10^{12}}{1} + \frac{10^{12}}{2} \right) + \frac{10^{-3} \times 10^{12}}{2} \\ &= 2 \times 10^{10} + \frac{3}{2} \times 10^{10} + \frac{10^9}{2} = 10^{10} \times \frac{10^{-1}}{2} = 10^{10} \times \frac{10}{2} \times 10^{-2} = 0.05 \times 10^{10} \\ &\approx \frac{1}{2} \times 10^{10} = \frac{\omega_0}{Q} \Rightarrow Q = \frac{\sqrt{2} \times 10^{10}}{\frac{1}{2} \times 10^{10}} = \frac{2\sqrt{2}}{1} \approx \frac{1}{2} \end{aligned}$$

added after class

$$T(s) = 10^{10} \frac{s - 10^9}{s^2 + 3.55 \times 10^{10} s + 2 \times 10^{20}}$$


factor denominator, $s_{1,2} = \frac{-3.55 \times 10^{10} \pm \frac{1}{2} \sqrt{(3.55 \times 10^{10})^2 - 4 \times 2 \times 10^{20}}}{2}$

$$= \frac{10^{10}}{2} (-3.55 \pm \sqrt{(3.55)^2 - 8}) = \frac{10^{10}}{2} (-3.55 \pm 1.898)$$

$$\text{or } T(s) = 10^{10} \frac{s - 10^9}{(s + 2.724 \times 10^{10})(s + 0.826 \times 10^{10})}$$

$$T(s) = T'(s') = \frac{s' - 0.1}{(s' + 2.724)(s' + 0.826)} \quad \text{if we let } s' = s/10^{10} \quad \text{as a normalized form}$$

Design of a current mirror or source

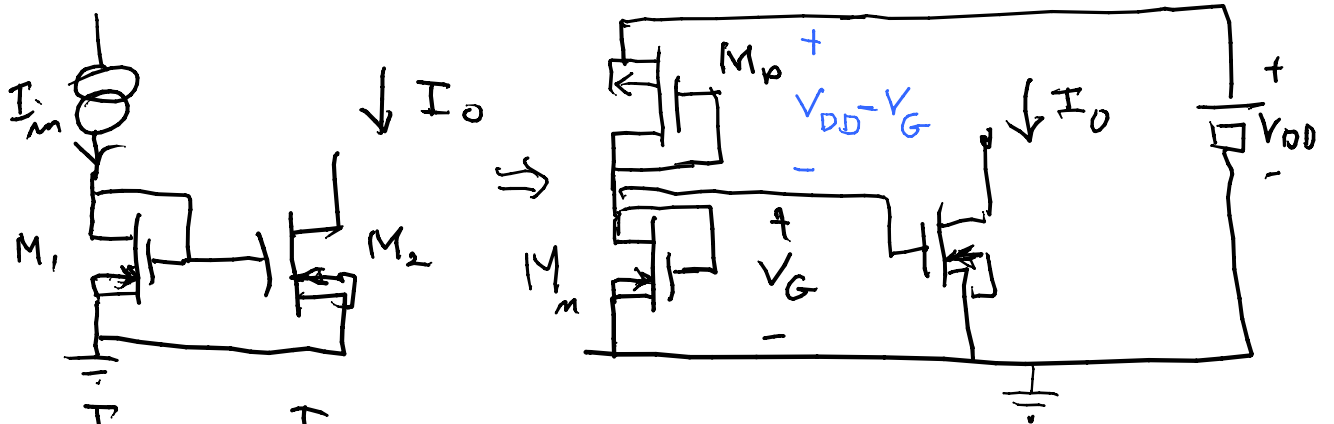

$$I_{S_p} = I_{D_m} = -I_{D_p}$$

$$= \frac{K P_p}{2} \frac{W_p}{L_p} ((V_{DD} - V_G) - |V_{T0_p}|)^2 = \frac{K P_m}{2} \frac{W_m}{L_m} (V_G - V_{T0_m})^2$$

can solve for V_G , can achieve almost any V_G by $\frac{W}{L}$ choices