
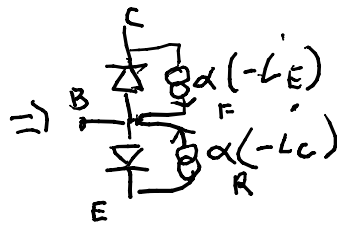
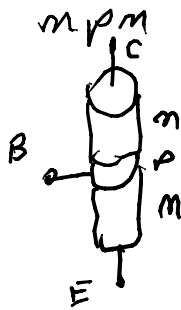
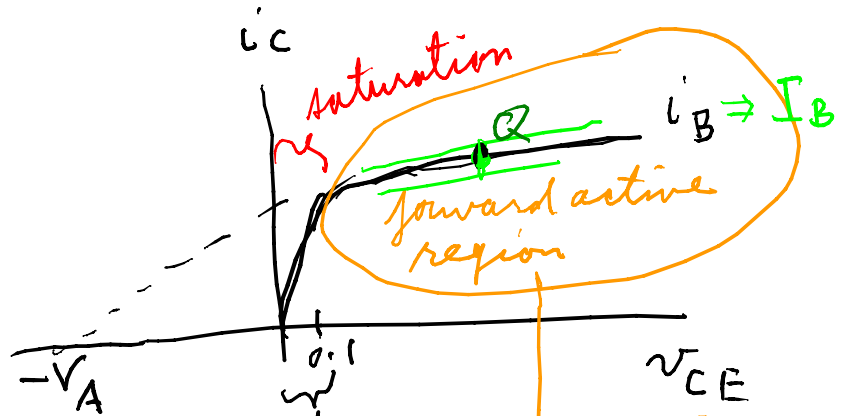


Hybrid- π model

N. 448

BJT

EE303
02/22/06

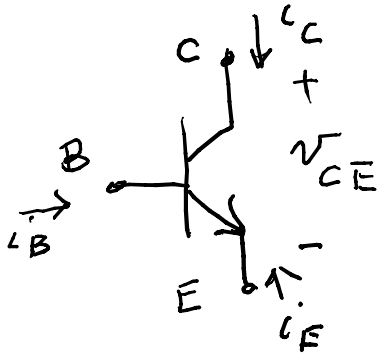

both
diodes
forward
bias

base bias
CB
forward bias
BE

Ebers-Moll
equivalent (large signal)


Small signal

$$i_c = f(i_B, v_{CE}) = I_C + \frac{\partial i_c}{\partial i_B} (i_B - I_B) + \frac{\partial i_c}{\partial v_{CE}} (v_{CE} - V_{CE})$$

$$i_c - I_C = \frac{\partial i_c}{\partial i_B} \Big|_Q i_b + \frac{\partial i_c}{\partial v_{CE}} \Big|_Q v_{ce}$$


+ ...
ignore
for small
signal
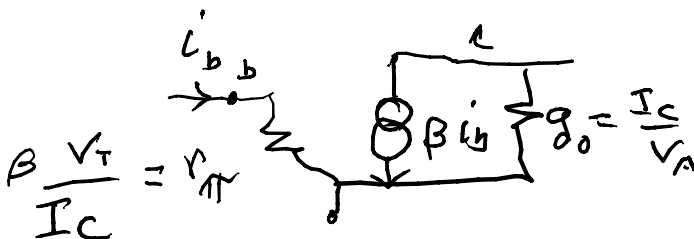
$$= \beta i_b + g_o v_{ce} \quad \text{here } g_o \approx \frac{I_C}{V_A}$$



$$i = yv$$


look

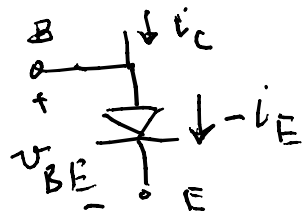

$$-i_E = I_{SE} e^{v_{BE}/V_T}, \quad V_T = \frac{kT}{q}$$

$$\left. \frac{d(-i_E)}{dv_{BE}} \right|_Q = \frac{I_{SE} e^{v_{BE}/V_T}}{V_T}$$
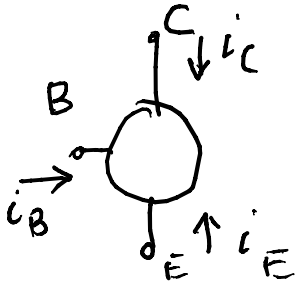
$$= \frac{-I_E}{V_T} \Rightarrow i_e = -\frac{I_E}{V_T} v_{be}$$



$$\text{KCL: } i_B + i_C + i_E = 0 \equiv i_b + i_c + i_e = 0$$

$$\text{if } i_c = \beta i_b \Rightarrow i_b + \beta i_b = -i_e \Rightarrow i_e = -(1+\beta)i_b$$

$$i_c = \beta i_b$$

$$= -\frac{\beta}{1+\beta} i_e$$

$$= -\alpha i_e$$

$$\alpha = \frac{\beta}{1+\beta}; \Rightarrow (1+\beta)\alpha = \beta$$

$$\beta - \beta\alpha = \alpha$$

$$\beta = \frac{\alpha}{1-\alpha}$$

numerical:

$$\beta = 50 \Rightarrow \alpha = \frac{50}{51} \approx 0.98$$

$$-i_e = \frac{|I_E| \cdot v_{be}}{V_T}$$


$$(1+\beta)i_b = \frac{|I_E| \cdot v_{be}}{V_T}$$

$$i_b = \frac{|I_E|}{(1+\beta)V_T} \cdot v_{be}$$

$$g_{\pi} = \frac{|I_E|}{(1+\beta)V_T} = \frac{1}{\alpha} \cdot \frac{I_C}{(1+\beta)V_T}$$

$$= \frac{I_C}{\beta V_T} = g_{\pi}$$
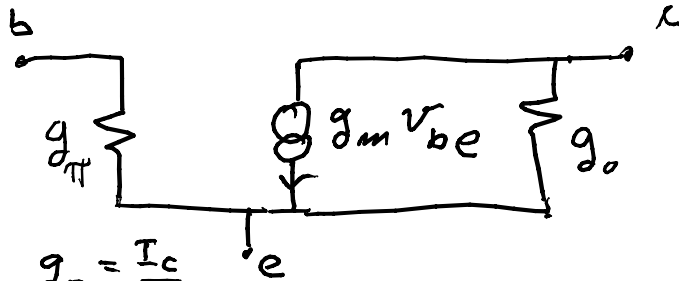
$$\beta \cdot i_b = \beta (g_{\pi} v_{be}) = \frac{\beta I_C}{\beta V_T} \cdot v_{be} = \frac{I_C}{V_T} \cdot v_{be} = g_m v_{be}$$



$$g_{\pi} = \frac{I_C}{\beta V_T}$$

$$g_m = \frac{I_C}{V_T}$$

$$g_o = \frac{I_C}{V_A} = \frac{V_T}{V_A} \cdot \frac{I_C}{V_T}$$

$$= \frac{1}{\beta} g_m$$

$$= \eta_A \cdot g_m$$