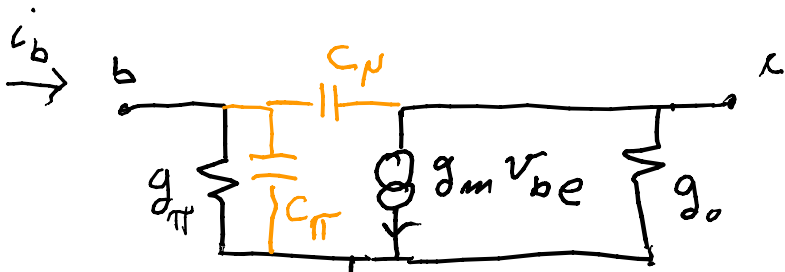


BJT

EE303
02/24/06



$$g_\pi = \frac{I_c}{\beta V_T} = \frac{1}{\beta} g_m$$

$$g_m = \frac{I_c}{V_T}$$

$$g_o = \frac{I_c}{(V_A + V_{CE})} = \frac{V_T}{(V_A + V_{CE})} \cdot \frac{I_c}{V_T} = \frac{1}{A} g_m$$

$V_T =$ thermal voltage


Ex: $\beta = 50$, $I_c = 2 \text{ mA}$, $V_A = 100 \text{ V}$; $V_T = 0.026$

$$g_m = \frac{I_c}{V_T} = \frac{2 \times 10^{-3}}{26 \times 10^{-3}} = 0.077 = 77 \text{ mS}$$

$$g_\pi = \frac{g_m}{\beta} = 0.0015 = 1.5 \text{ mS}; r_\pi = 0.67 \text{ k}\Omega$$

$$g_o = \frac{I_c}{V_A} = \frac{2 \times 10^{-3}}{1 \times 10^2} = 0.2 \times 10^{-6}; r_o = \frac{1}{g_o} = 5 \text{ meg}\Omega$$

Problem is to bias

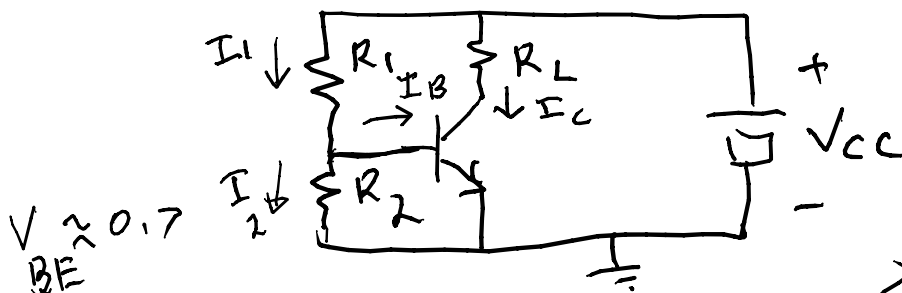

given I_c & β
$$I_B = \frac{I_c}{\beta}$$

$$I_1 = I_2 + I_B$$

choose R_2 , large, $\Rightarrow I_2 \Rightarrow I_1$

$V_{BE} \approx 0.7$


$$\sim e^{(V/kT/q)}$$

very dependent on temperature

actual bias uses


$$V_{BE}/R_2$$

$$R_1 = \frac{V_{CC} - V_{BE}}{I_1}$$

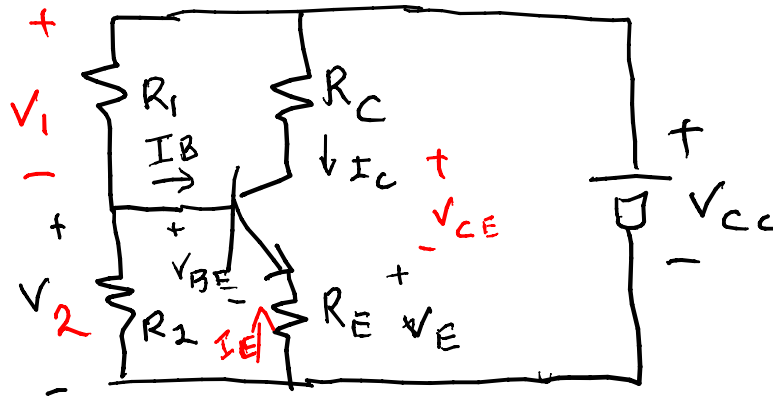

if $I_C \uparrow \rightarrow V_E \uparrow$
 if $V_2 = \text{const} \rightarrow V_{BE} = V_2 - V_E \downarrow$
 $\rightarrow I_E \downarrow \rightarrow I_C \downarrow$
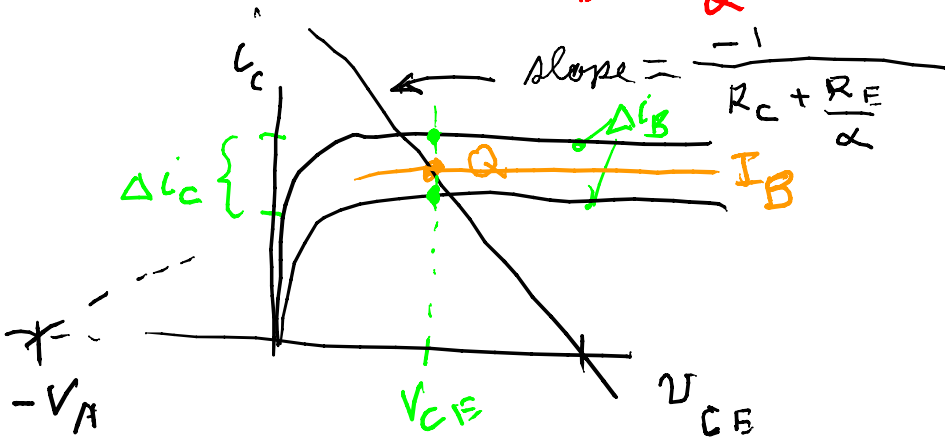
$$I_B = -\frac{I_C}{\alpha}; V_E = R_E \left(\frac{I_C}{\alpha} \right) = \left(\frac{R_E}{\alpha} \right) I_C$$



$$\beta = \frac{\partial I_C}{\partial I_B} \Big|_Q$$

$$\alpha = \frac{\beta}{\beta + 1}$$

if choose R_E (say $1k\Omega$) the load line fixes R_C
 after we get $\beta \rightarrow \alpha = \frac{\beta}{\beta + 1}$ & Q_{point} fixes I_C

Choose R_2 large (say $1\text{meg}\Omega$); V_E fixed by α, I_C, R_E

$$V_2 = I_2 \cdot R_2 \Rightarrow I_2 = \frac{V_2}{R_2} = \frac{V_{BE} + V_E}{R_2} \approx \frac{0.07 + (\frac{I_C}{\alpha})R_E}{R_2}$$

know I_B (= Q at base current)

& I_2


$$I_1 = I_2 + I_B \Rightarrow R_1 = \frac{V_{CC} - V_2}{I_1}$$

R_C normally fixed by gain; $\frac{V_o}{V_i} = -g_m R_C$

assume we desire $\frac{V_o}{V_i} = \text{open circuit} = 10$
voltage gain

and $I_C = 2\text{mA}$; $\Rightarrow R_C = 10/g_m = 10 \times 13 = 130$

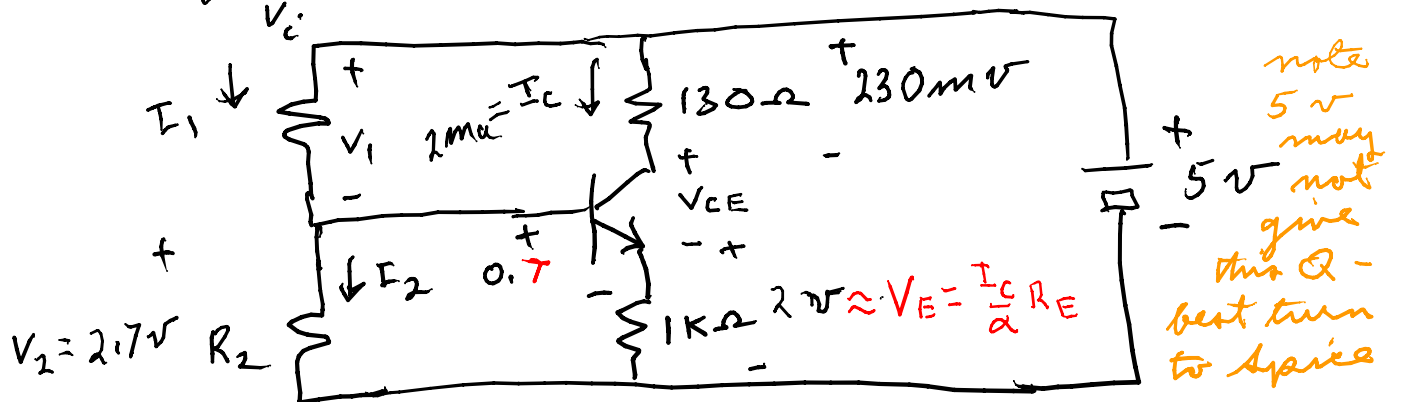note if $\frac{V_o}{V_i} = -100$, $R_C = 1.3\text{K}\Omega$



choose $R_2 = 1\text{M}\Omega = 10^6 \Omega$; $I_2 = \frac{2.7\text{V}}{10^6} = 2.7\mu\text{amp}$

$I_B = \frac{I_C}{\beta} = \frac{2 \times 10^{-3}}{100} = 20\mu\text{A} > I_2$; $I_1 = 22.7\mu\text{amp}$
 $V_1 = 5 - 2.7\text{V} = 2.3\text{V}$

$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.9901$

$R_1 = \frac{V_1}{I_1} \approx \frac{2.3}{23} \times 10^6 = 0.1 \times 10^6 \Omega$