

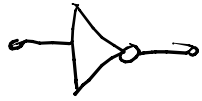


EE303
03/06/06

Inverters - CMOS


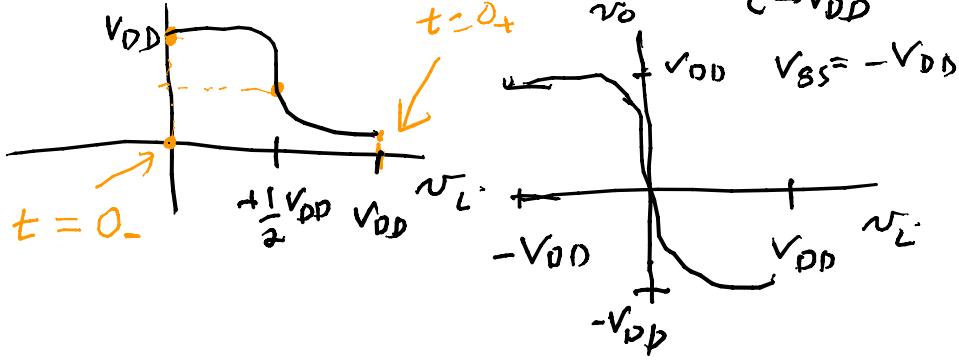


Symbols

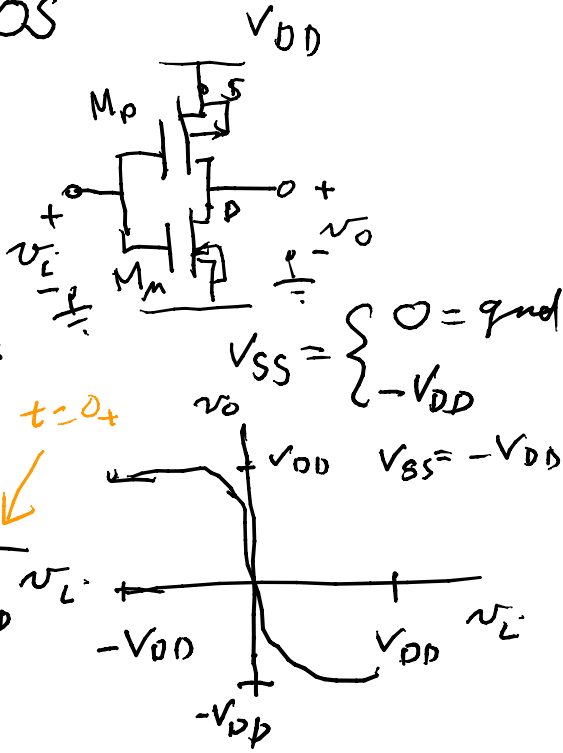

use this below

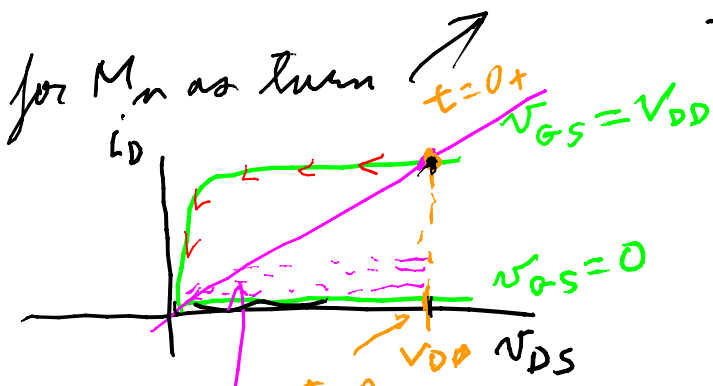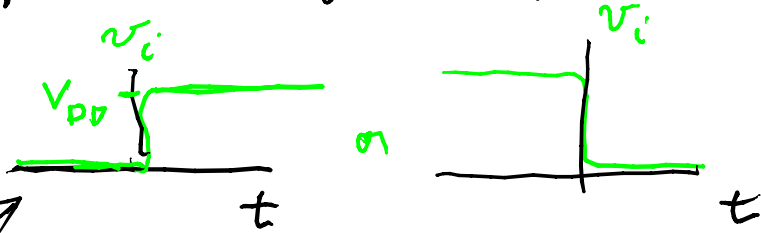normally for computers v_i jumps from one level to another





for getting delay need the RC time constant


average "conductance" curve = $I_{out} = 1/R_{out}$
(as v_{DS} goes from V_{DD} to 0 through ohmic region)

This gives the resistance to charge or discharge a load capacitor (could be C_{in} of another inverter)

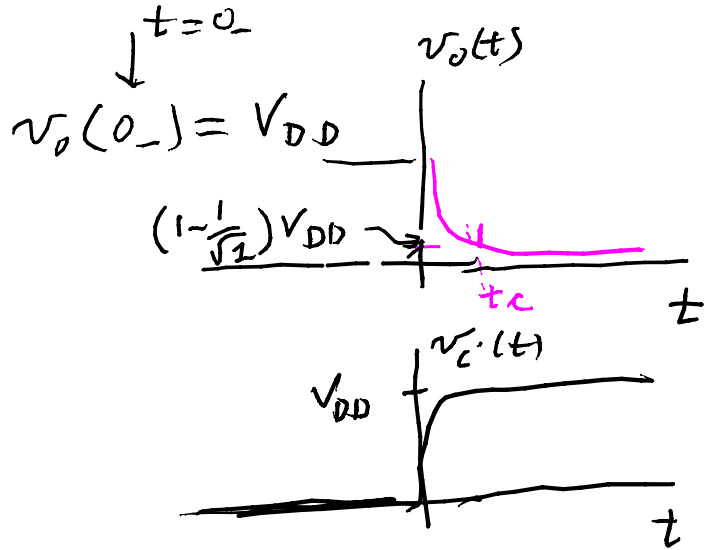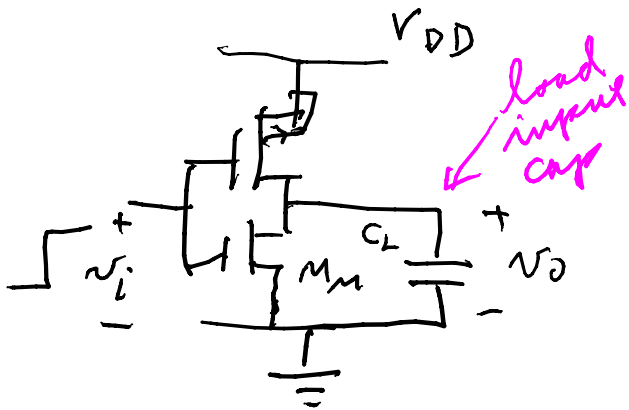time constants of RC circuits are $R \cdot C$




$$RC = r_{out} \cdot C_L = t_c$$

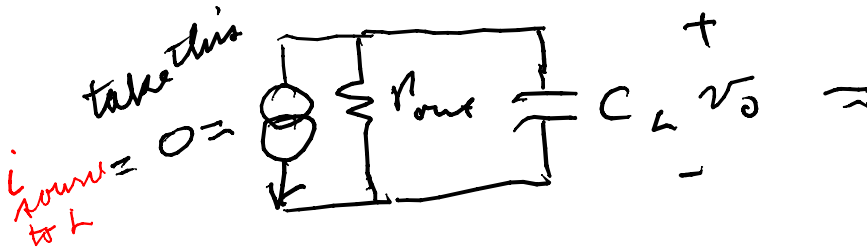

$$r_{out} = \frac{1}{\text{slope}} = \frac{1}{\frac{\frac{K_P W}{2 L} (V_{DD} - V_{TO})^2}{V_{DD}}} = \frac{V_{DD}}{\frac{K_P W}{2 L} (V_{DD} - V_{TO})^2}$$


Ex: load = 2nd inverter

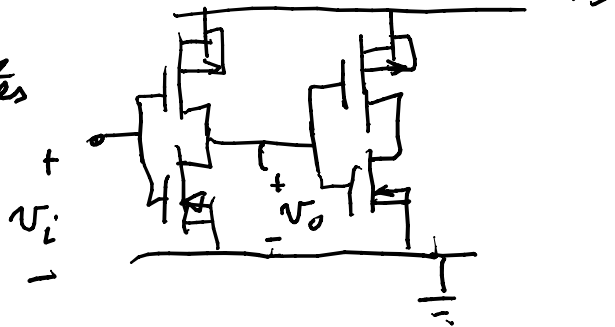

to get delay to go through 1st stage

$$C_L = C_{gs} + C_{gd}$$

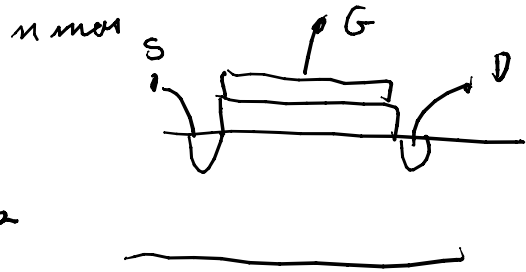assume $C_{gs} \approx \frac{1}{2} \frac{(W \cdot L) \epsilon_{SiO_2}}{t_{ox}}$
 $\approx C_{gd}$



say

$$C_{gs} = 5 \text{ pF} \Rightarrow C_L = 10 \text{ pF}$$

desire $t_{\text{constant}} \Rightarrow V_{out} \cdot C_L$; let $V_{DD} = 5 \text{ v}$

$$V_{TO} = 1 \text{ v}$$

$$W = L \Rightarrow \mu$$

$$K_P = 20 \times 10^{-4} \text{ amp}^2/\text{V}^2$$

$$V_{out} = \frac{V_{DD}}{\frac{K_P \mu}{2} \frac{W}{L} (V_{DD} - V_{TO})^2}$$

$$= \frac{5}{10 \times 10^{-4} \times 1 \times (5-1)^2} = \frac{5}{10^{-3} \times 16} = \frac{5 \times 10^3}{16} = \frac{50}{10} \times 10^2$$

$$= 3.1 \times 10^2$$

$$t_c = 3.1 \times 10^2 \times 10 \times 10^{-12} = 31 \times 10^{-10} = 3.1 \times 10^{-9}$$

$$= 3.1 \text{ nano sec}$$

delay time better calculated as time to fall to $V_{DD}/2$ (probably about 2 nano)

