

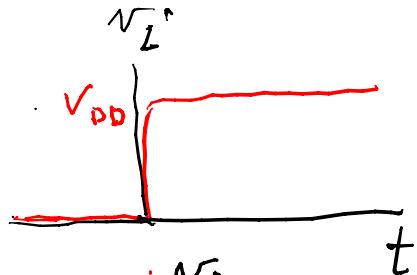


EE 303  
03/10/06

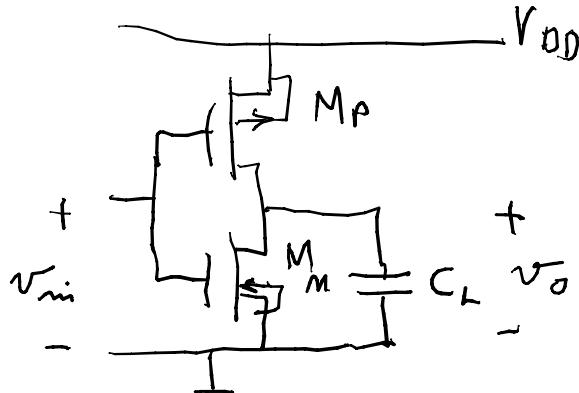

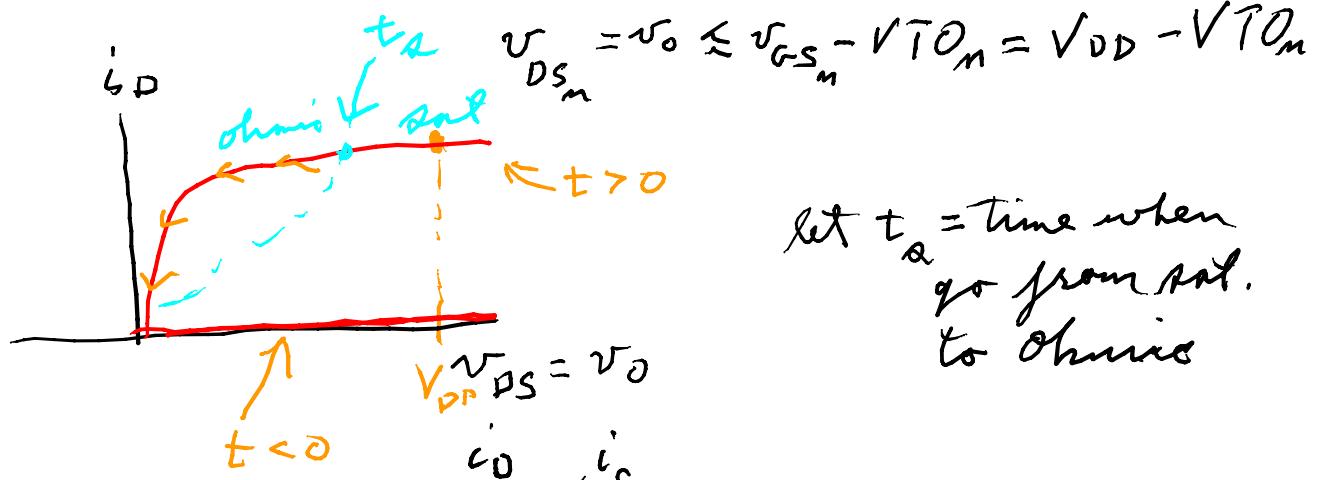
$$i_{Dm} = \frac{KP_m}{2} \left( \frac{W_m}{L_m} \right) \begin{cases} (V_{GS_m} - VT_{O_m})^2 & v_o \geq v_i - VT_{O_m} \\ 2(V_{GS_m} - VT_{O_m})v_o - v_o^2 & \end{cases}$$



Let  $t_\alpha$  = time when go from sat. to ohmic

Eq.

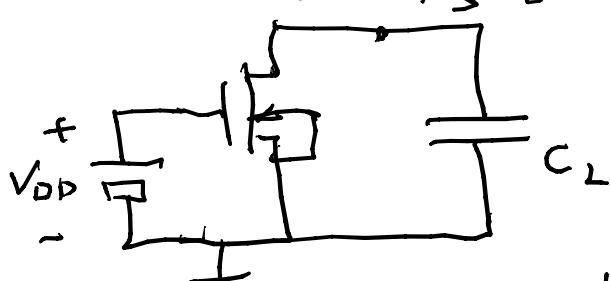

$$t \quad v_o \quad -$$

$$v_o(0) = V_{DD}$$

$$\beta_m = \frac{KP_m}{2} \left( \frac{W_m}{L_m} \right)$$

$$KCL: -i_D - i_{C_L} = 0$$

$$t < t_\alpha \quad i_{Dm} = \beta_m \cdot (V_{DD} - VT_{O_m})^2 = -i_{C_L} = -C_L \frac{dV_o}{dt}$$

$$\dot{v}_o = -\frac{\beta_m}{C_L} (V_{DD} - VT_{O_n})^2 = \text{constant} \Rightarrow \int_0^t \dot{v}_o dt = \int_0^t \text{constant}$$

$$v_o(t) = -\frac{\beta_m}{C_L} (V_{DD} - VT_{O_n})^2 \cdot t \Big|_0^t, \quad 0 \leq t \leq t_s$$

$$t_s \text{ is when } v_o = v_i - VT_{O_n} = V_{DD} - VT_{O_n}$$

$$v_o(t) = -\left(\frac{\beta_m}{C_L}\right)(V_{DD} - VT_{O_n})^2 t + V_{DD} = v_o(0+) \quad 0 < t < t_s$$

$$t_s: V_{DD} - VT_{O_n} = -\left(\frac{\beta_m}{C_L}\right)(V_{DD} - VT_{O_n})^2 t_s + V_{DD}$$

$$t_s = \frac{VT_{O_n}}{\left(\frac{\beta_m}{C_L}\right)(V_{DD} - VT_{O_n})^2}$$

for  $t > t_s$

$$-C_L \frac{dV_o}{dt} = \beta_m (2(V_{DD} - VT_{O_n})v_o - v_o^2)$$

$$\dot{v}_o = -\frac{\beta_m}{C_L} [2(V_{DD} - VT_{O_n})v_o - v_o^2] \quad \text{a Riccati}$$

$$\frac{dV_o}{-\left(\frac{\beta_m}{C_L}\right)[2(V_{DD} - VT_{O_n})v_o - v_o^2]} = dt \quad \text{let } \alpha = \frac{\beta_m}{C_L}, \quad \gamma = V_{DD} - VT_{O_n}$$

$$\int_{t_s}^t d\gamma = \int_{v_o(t_s)}^{v_o(t)} \frac{dv_o}{\alpha v_o(v_o - 2\gamma)} = \frac{1}{\alpha} \int_{v_{o,t}}^{v_{o,t}} \left[ \frac{k_1}{v_o} + \frac{k_2}{v_o - 2\gamma} \right] dv_o$$

$$k_1(v_o - 2\gamma) + k_2 v_o = 1 \Rightarrow k_1 + k_2 = 0 \Rightarrow k_2 = -k_1$$

$$-2\gamma k_1 = 1 \Rightarrow k_1 = -1/2\gamma, k_2 = 1/2\gamma$$

$$t - t_s = \frac{1}{2\alpha} \left[ k_1 \ln v_o - k_1 \ln (v_o - 2\gamma) \right] \Big|_{v_o(t_s)}^{v_o(t)}$$

$$= \frac{-1}{2\alpha\gamma} \left[ \ln \left( \frac{v_o}{v_o - 2\gamma} \right) \right]_{v_o(t_s)}^{v_o(t)} ; \quad v_o(t_s) = V_{DD} - VT_0 \approx \gamma$$

$$= -\frac{1}{2\alpha\gamma} \left[ \ln \left( \frac{\frac{v_o(t)}{v_o(t) - 2\gamma}}{\frac{\gamma}{\gamma - 2\gamma}} \right) \right]$$

$$= -\frac{1}{2\alpha\gamma} \ln \left( \frac{v_o/\gamma}{\frac{2\gamma - v_o}{\gamma}} \right) = -\frac{1}{2\alpha\gamma} \ln \left( \frac{v_o/\gamma}{2 - \frac{v_o}{\gamma}} \right)$$

$$\therefore e^{-2\alpha\gamma(t-t_s)} = \left( \frac{v_o/\gamma}{2 - \frac{v_o}{\gamma}} \right) \Rightarrow e^{\rho} = \frac{x}{2-x} \Rightarrow 2e^{\rho} - e^{\rho}x = x$$


$$x(1+e^{\rho}) = 2e^{\rho}$$

$$\frac{v_o(t)}{\gamma} = \frac{2e^{-2\alpha\gamma(t-t_s)}}{1 + e^{-2\alpha\gamma(t-t_s)}}$$

$$t > t_s$$

$$@ t = t_s, e^{\rho} = 1$$
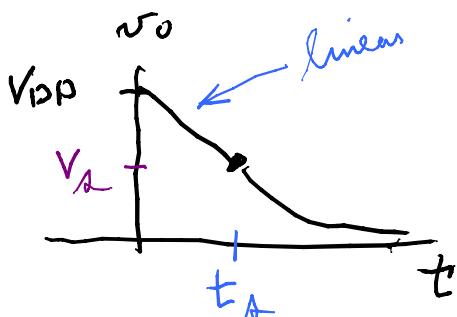
$$\text{gives } v_o(t) = \frac{2}{2} \gamma = \gamma = V_{DD} - VT_0$$



$$\text{call } \gamma = V_A$$

$$v_o(t) = \frac{2V_A}{1 + e^{\frac{2V_A \cdot \beta (t-t_s)}{C_L}}} \quad t > t_s$$


More added: delay time:  $\Rightarrow t$  for  $V_d = V_{DD}/2$   
from above

$$t = t_s - \left(\frac{C_L}{\beta}\right) \cdot \frac{1}{2V_A} \ln\left(\frac{V_0/V_A}{2 - V_0/V_A}\right) \quad \text{if } t_d > t_s$$

or

$$t_d = t_s - \left(\frac{C_L}{\beta}\right) \frac{1}{2V_A} \cdot \ln\left(\frac{V_{DD}/V_A}{4 - V_{DD}/V_A}\right) \quad \text{if } t_d > t_s$$

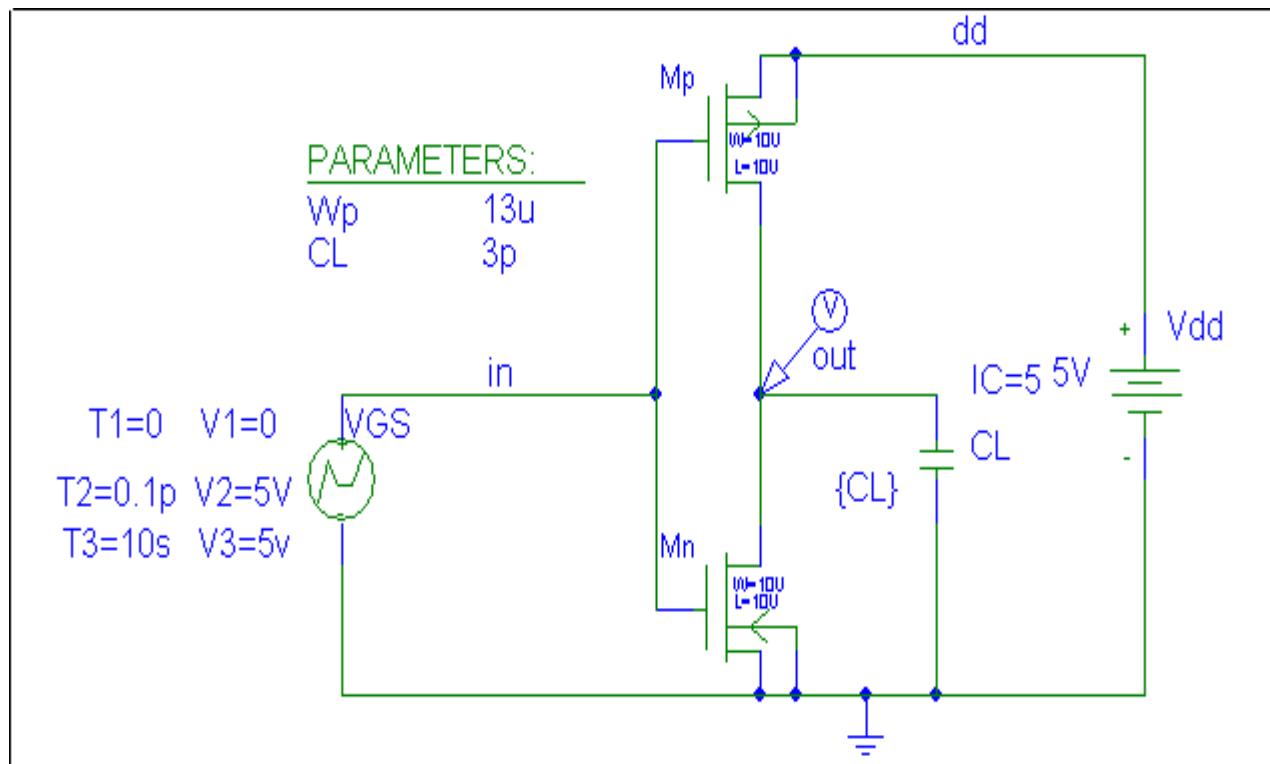[if  $t_d < t_s$  use  $t = \frac{V_{DD} - V_o(t)}{(\beta/C_L)V_A^2}$  or  $t_d = \left(\frac{C_L}{\beta}\right) \frac{V_{DD}}{2V_A^2}$



file: e:\courses\spring2006\434\inver\_Ct\_303.sch

transient analysis;  $0 \leq t \leq 110\text{ns}$   
mnmosis & mpmosis transistors used

