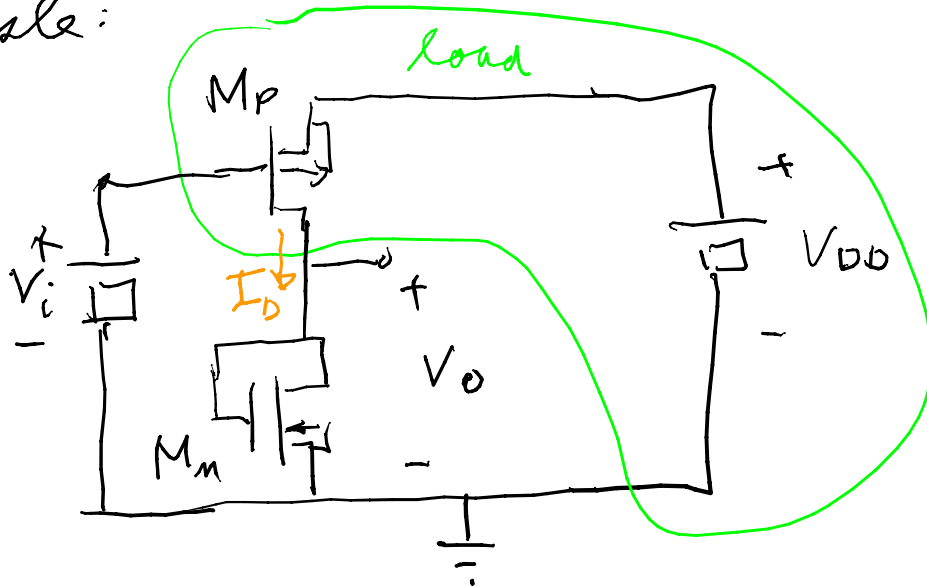




Example:



assume $V_{T0n} > 0$ M_n is in saturation
 as $V_{GSn} - V_{T0n} = V_{DSn} - V_{T0n}$



$$I_{Dn} = \frac{K P_n (W/L)_n}{2} (V_o - V_{T0n})^2 (1 + \lambda_n V_o) \text{ if } V_o \geq V_{T0n} < V_{DSn}$$

$$= 0 \text{ if } V_o \leq V_{T0n}$$

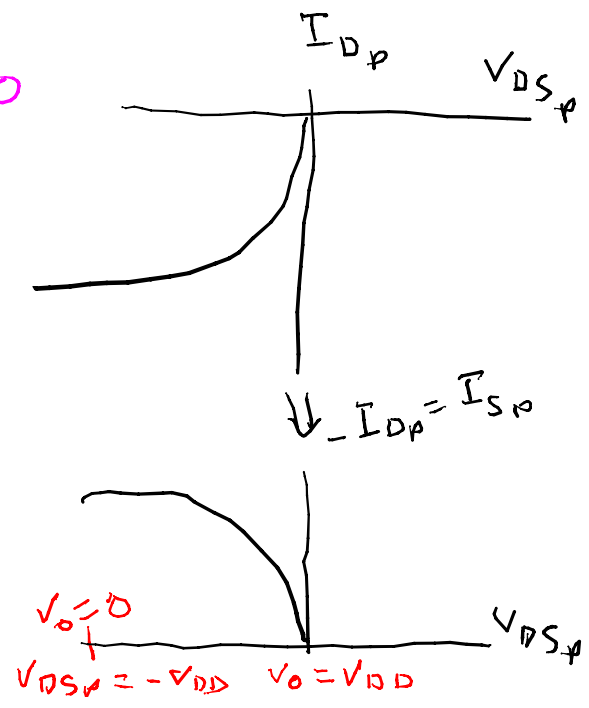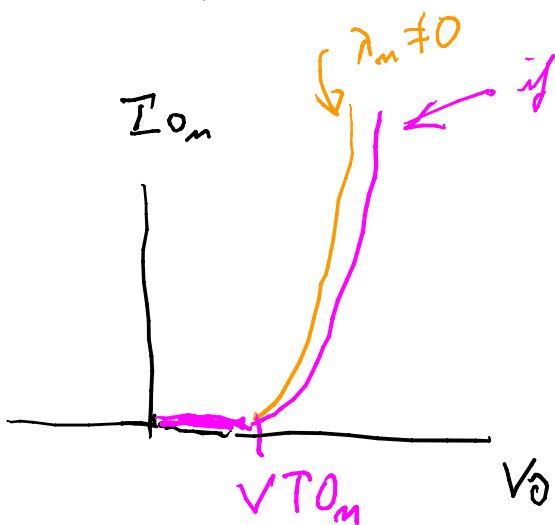

$$V_{DS_p} \Rightarrow V_o = V_{DS_p} + V_{DD}$$

$$V_{SG_p} = V_{DD} - V_i$$

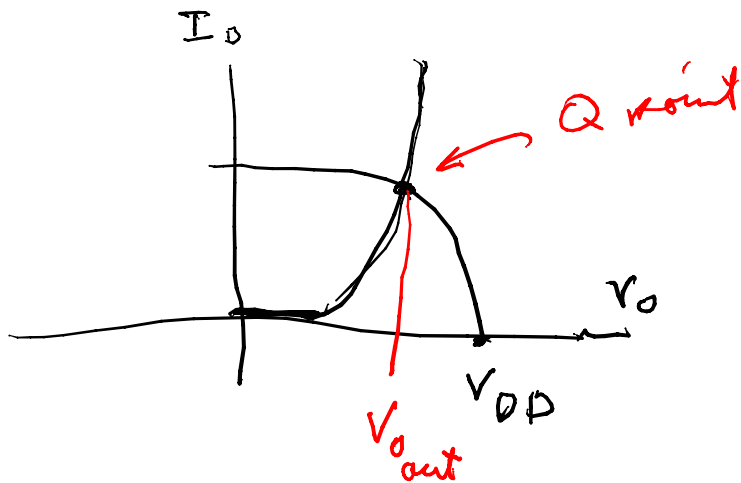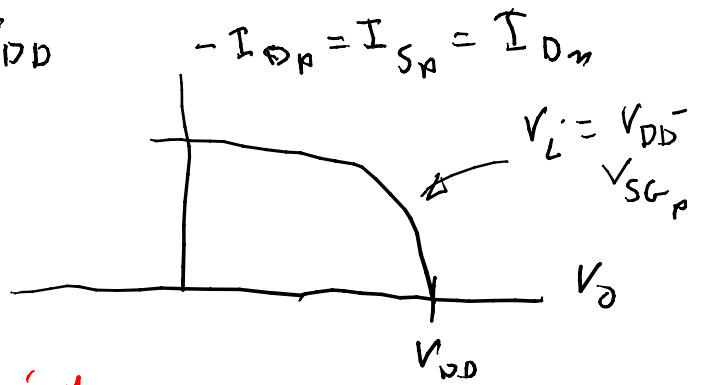

$$V_{SG_p} - |V_{TO_p}| \approx V_{SD_p} \Rightarrow V_o = V_{DS_p} + V_{DD} = -V_{SD_p} + V_{DD}$$

$$\parallel \Rightarrow V_{SD_p} = V_{DD} - V_o$$

if $V_{DD} - V_i - |V_{TO_p}| < V_{DD} - V_o$ in saturation (M_p)

$\Rightarrow V_o - |V_{TO_p}| < V_i$ saturation } assume $V_{SG_p} > |V_{TO_p}|$
 $V_o - |V_{TO_p}| > V_i$ ohmic } (small enough $|V_i|$)

assume $V_i > V_o - |V_{TO_p}|$; $V_{DD} - V_i > |V_{TO_p}|$

$$\lambda_n = \lambda_p = 0$$

turned on


$$I_{D_n} = \frac{K P_n W}{2} \frac{L}{L_n} (V_o - |V_{TO_n}|)^2 = +I_{S_p} = \frac{K P_p (W)}{2} \frac{L}{L_p} (V_{DD} - V_o - |V_{TO_p}|)^2$$

$$(V_0 - |V_{T0n}|) = + \underbrace{\left(\frac{K_{Pp}}{K_{Pn}} \right) \left(\frac{(W/L)_p}{(W/L)_n} \right)}_k (V_{DD} - V_0 - |V_{T0p}|)$$

$$V_0 + kV_0 = V_{T0n} - k(V_{DD} + |V_{T0p}|)$$

$$V_0 = \frac{1}{1+k} (V_{T0n} + k(V_{DD} + |V_{T0p}|))$$

BJT current source, p. 442

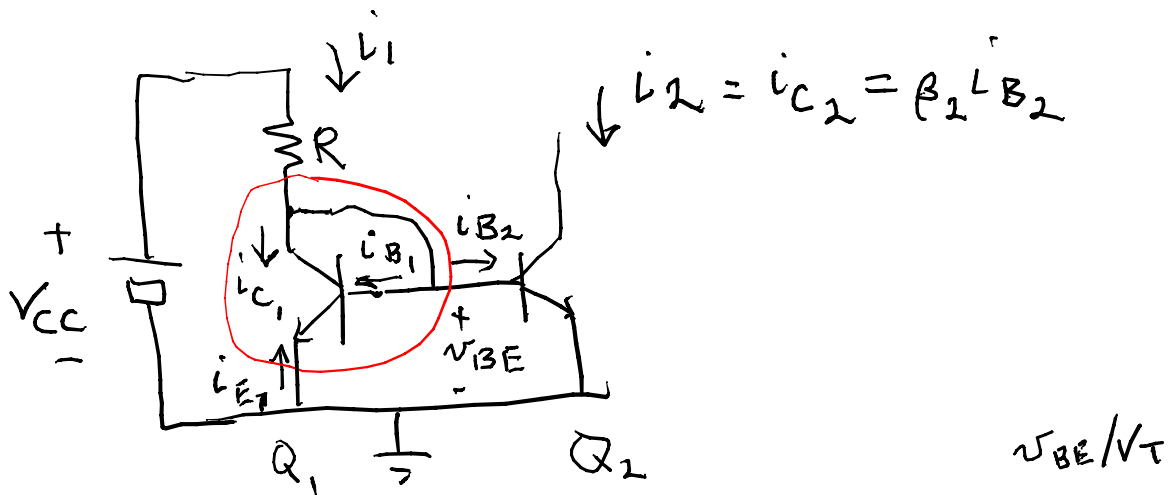

$$\text{KCL } i_1 - i_{B2} + i_{E1} = 0$$

$$-i_{E2} = A_2 J_S e^{V_{BE}/V_T}$$

$$-i_{E1} = A_1 J_S e^{V_{BE}/V_T}$$

$A_i = \text{emitter area}$

$$\frac{i_{E2}}{i_{E1}} = \frac{A_2}{A_1}$$

$$i_C = \beta i_B = -\alpha i_E \Rightarrow i_E = \frac{\beta}{\alpha} i_B$$

$$i_1 = i_{B2} - i_{E1}$$

$$\beta = \frac{\alpha}{\alpha - 1}$$

$$= \frac{1}{\alpha - 1} i_B$$

$i_2 = i_{C2} = \alpha i_{E2}$ use these to get i_2 vs i_1 as a function of A_2/A_1

$$i_B = (\alpha - 1) i_E$$

$$\begin{aligned} \therefore i_1 &= (\alpha_2 - 1) i_{E2} - \frac{A_1}{A_2} i_{E2} = \left[(\alpha_2 - 1) - \frac{A_1}{A_2} \right] \left(-\frac{i_{C2}}{\alpha_2} \right) \\ &= \left[\frac{(1 - \alpha_2)}{\alpha_2} + \frac{1}{\alpha_2} \frac{A_1}{A_2} \right] i_2 \end{aligned}$$

$$\text{or } i_2 = \frac{1}{\left[\frac{1}{\beta_2} + \frac{1}{\alpha_2} \frac{A_1}{A_2} \right]} i_1$$

To set up i_1 we usually approximate $v_{BE} \approx 0.7$ & use $V_{CC} = v_{BE} + R i_1$, or $i_1 = \frac{V_{CC} - v_{BE}}{R}$

More accurately though we can use the above for $i_1 = i_{B2} - i_{E1} = (\alpha_2 - 1) i_{E2} - i_{E1} = \left[(\alpha_2 - 1) \frac{A_2}{A_1} - 1 \right] i_{E1}$
 $= \left[(\alpha_2 - 1) \frac{A_2}{A_1} - 1 \right] \cdot I_{SE1} e^{v_{BE}/V_T}$

and solve the equation

$$i_1 = \frac{V_{CC} - v_{BE}}{R} = \left[(\alpha_2 - 1) \frac{A_2}{A_1} - 1 \right] I_{SE1} e^{v_{BE}/V_T}$$

