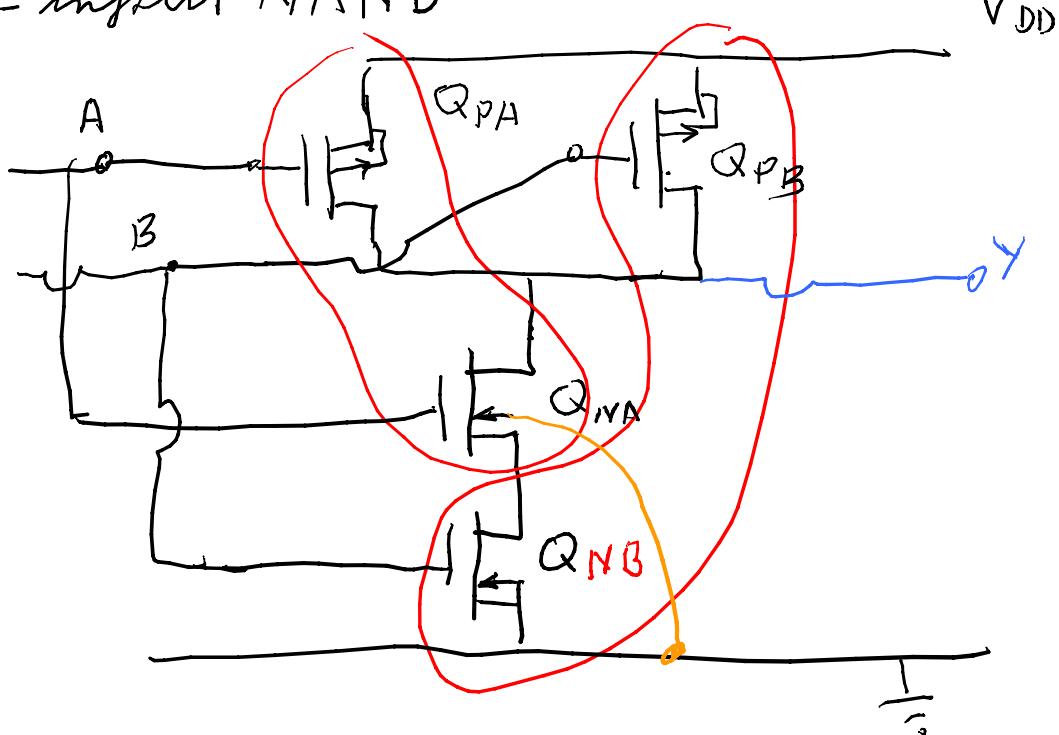


CMOS gates

P. 967

EE303
03/17/06

2-input NAND




if $A = 0, Y = 1$ (no matter B)


$B = 0, Y = 1$ (no matter A)

$A \otimes B = 0, Y = 1$

$A \otimes B = 1, Y = 0$

when
 $A \otimes B = 1$

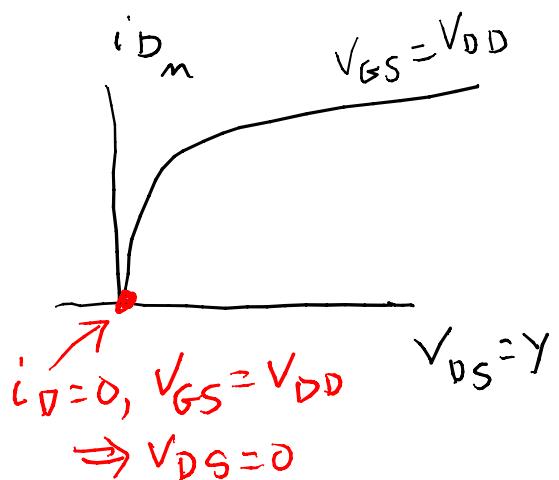

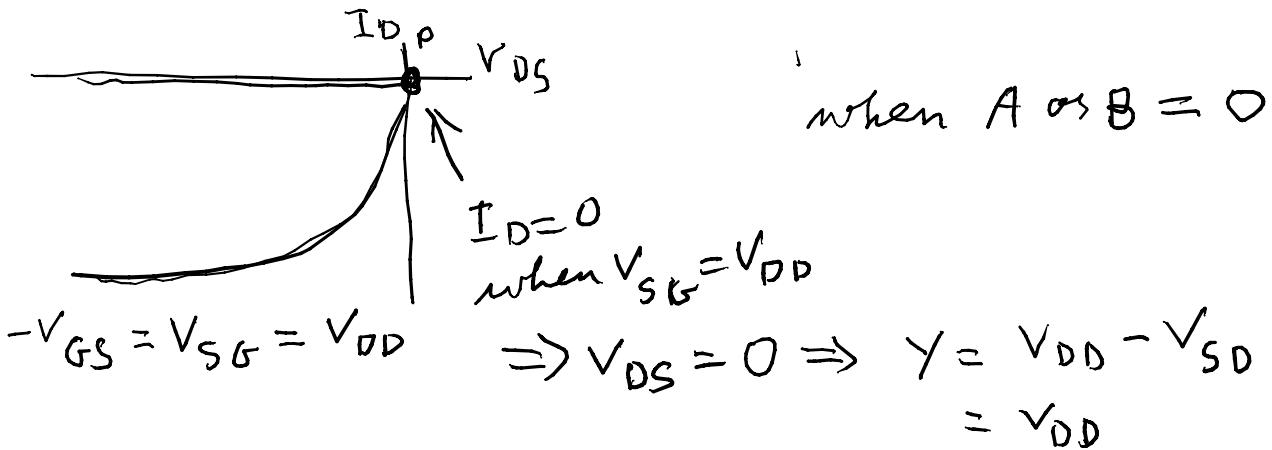

note substrate on Q_{NA} is not tied to the source unless put in a separate P-well if make on one chip. Means that $V_{th,NA} \neq V_{TO}$

$$V_{th} = V_{TO} + \text{GAMMA} \left(\sqrt{V_{SB} + 2\phi_f} - \sqrt{2\phi_f} \right)$$

\underline{L}_T , (4.33)

p. 258

