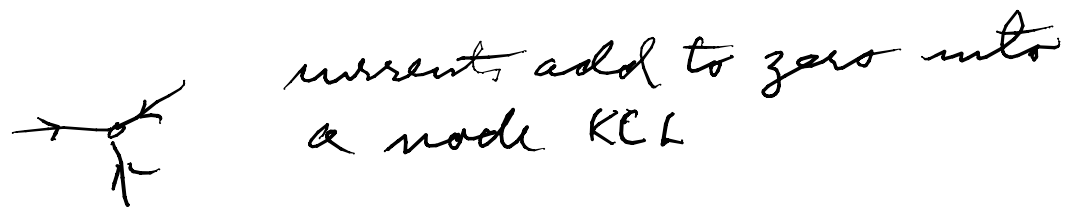





Homework 5 due M 04/17/06

current mode



currents add to zero into a node KCL

switched current circuits

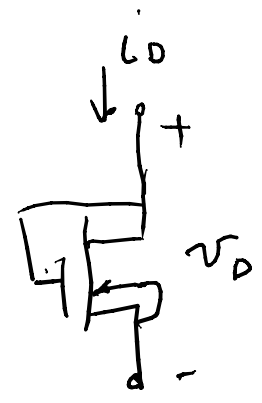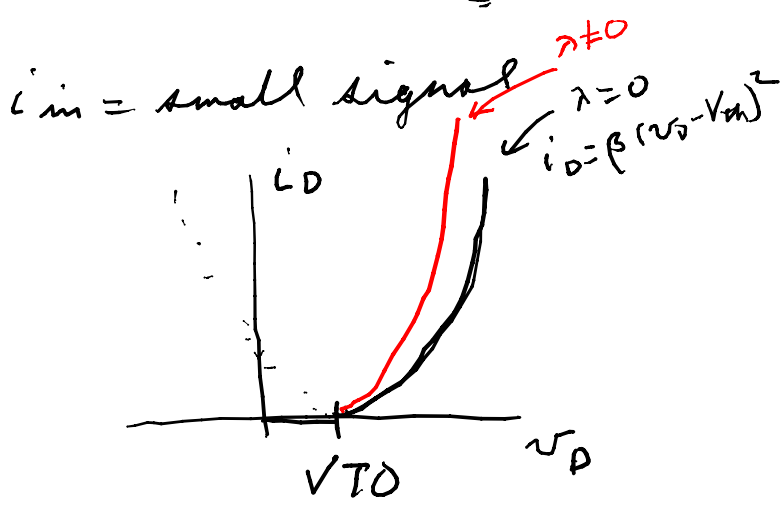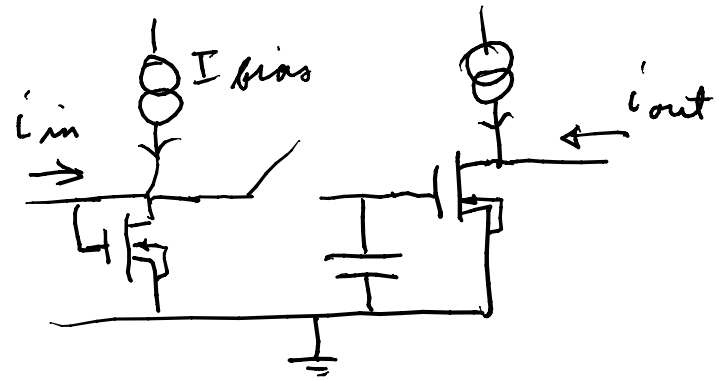


here $v_{DS} = v_D$
 $v_{GS} = v_D$

so $v_{DS} \geq v_{GS} - V_{T0}$

if assume $V_{T0} > 0$ (enhancement mode)

in saturation region if $v_D > V_{T0}$
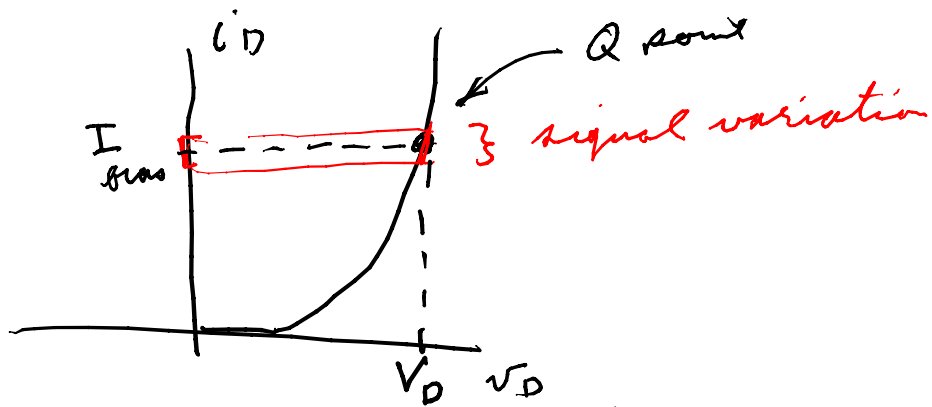
$$i_D = \frac{K_P W}{2 L} (v_D - V_{T0})^2 (1 + \lambda v_D)$$




small signal analysis

$$i_D = \beta (v_D - V_{th})^2 (1 + \lambda v_D)$$

$$\frac{\partial i_D}{\partial v_D} = \beta \{ 2(v_D - V_{th})(1 + \lambda v_D) + (v_D - V_{th})^2 (\lambda) \} = g_d$$


$$i_D = I_{bias} + g_d \cdot (v_D - V_D) + \dots$$

$$i_D = g_d \cdot v_D$$

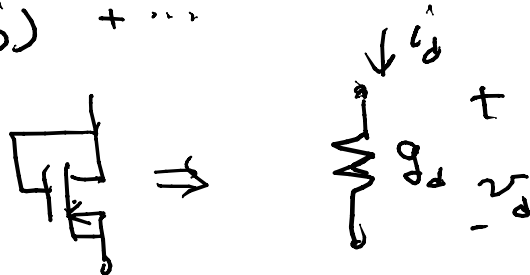

for g_d need V_D

small signal

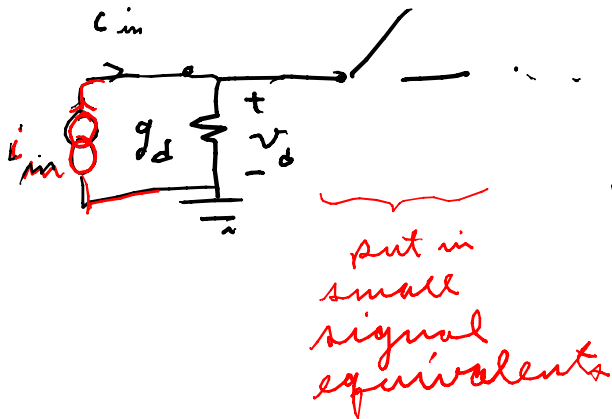

(if λ small)

$$V_D = V_{th} + \sqrt{\frac{I_{bias}}{\beta R}} \quad \frac{K_P W}{2 L}$$

