

File: E:/courses/spring2006/303/hmwrk1.doc RWN 01/30/06b-02/06/06


Homework Set 1 due ~~Monday February 6, 2006~~ Wednesday 02/08/06

If not yet done, download the bicos12 files to use in your Spice program. For grading purposes submit your circuit diagrams and typical probe plots.

1. [35 points] In Spice set up a circuit which will simultaneously generate a plot of the dc diode anode current versus the diode voltage for each of the following:

- Dbreak (in breakout library)
- d_body of the 4007 (=RCA36000) CMOS model (in Spice file ANL_MISC.lib)
- the BN2X4 npn BJT in the library bicos12 when the collector is connected to the base
- the BN2X4 npn BJT in the library bicos12 when the emitter is connected to the base

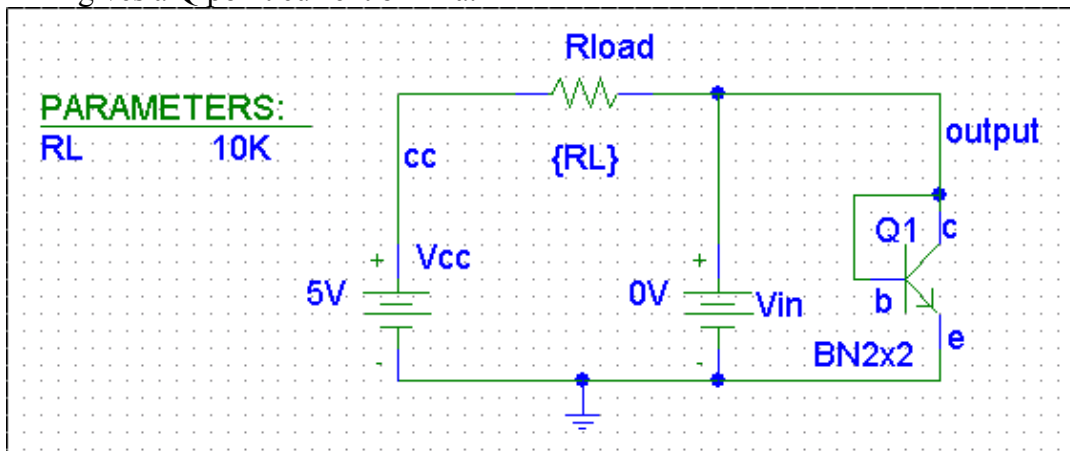2. [30 points] For the following circuit find by using Spice the value of Rload which gives a Q point current of 2ma.



3. [35 points] Set up the following circuit in Spice using mnmosis and mpmosis transistors (in the bicos12 library) and then do dc runs where Vin varies between Vss and Vdd.

- plot ID(M4) versus Vin
- for the same data as in a) plot ID(M4) versus ID(M3)
- plot Vout and Vmid vs Vin
- in the dc run add a parametric variation of W2 between 10u and 50u in 20u steps and repeat a)

