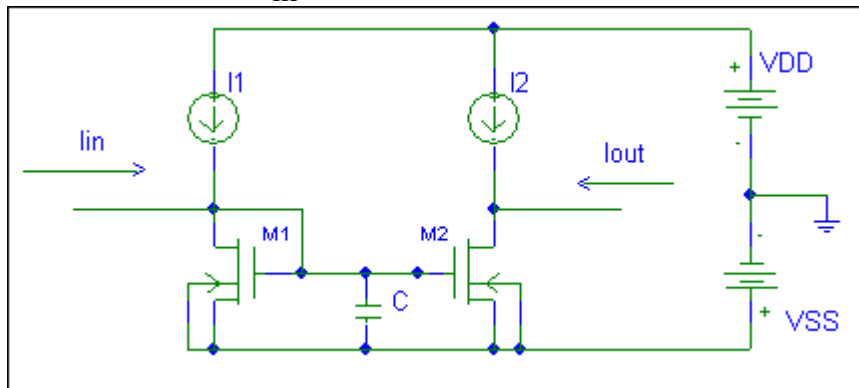


1. [50 points]
  - A) Design three ring oscillators, one each for 3, 5, 7 sections of inverters. Use the 1.2u level 3 AMI (MOSIS) transistors. For this set the minimum W and L to 7u and adjust the inverter sections so that zero input gives zero output [use  $V_{DD} = -V_{SS} = 5V$ ]. Compare their frequencies of oscillation and their waveforms. Compare your results with those given on page 1027 of the text and discuss differences (including frequency calculations vs simulated).
  - B) Repeat by inserting a 1NanoFarad load capacitor (to ground) for each inverter.

2. [50 points]
 

The following circuit is proposed in the literature [reference below, p, 411, Fig. 4] to be a current-mode low pass filter with transfer function

$$\frac{i_{out}(s)}{i_{in}(s)} = \frac{1}{\left(\frac{C}{g_m}\right) * s + 1}$$



- A) Show that this is the case by expanding about the bias point set by the two DC current sources. In so doing give  $g_m$  in terms of circuit parameters. What is the assumed M1 versus M2 ratios of W/L?
- B) Cascade two of these and give the resulting transfer function in the form

$$\frac{i_{out}(s)}{i_{in}(s)} = \frac{k}{s^2 + \left[\frac{\omega_0}{Q}\right]s + \omega_0^2}$$

Evaluate Q and  $\omega_0$  in terms of C1, C2, gm1, gm2 (the two stage parameters) and in so doing show that this cascade can not realize any degree two low-pass filter; give the possible Q which can be obtained.

- C) Introduce feedback into the cascade of B) and show how any low pass filter can be obtained to within a gain constant. How can  $k > 1$  and  $k < -1$  be obtained?

Reference: M. Siripruchyanum, "A Low-Voltage, Low-Power Current-mode Automatic Gain Control (AGC) for Battery-Powered Equipment," Proceedings of the Third IEEE International Workshop on Electronic Design, Test & Applications, Kuala Lumpur, January 2006, pp. 410 – 413.