

file: e:\courses\spring2006\303\inv\_charg.mcd RWN 03/10/06

values for mnmosis transistors

$$\begin{array}{lll} KPn := 5.048 \cdot 10^{-5} & VTOn := 0.858153 & KPP := 1.908 \cdot 10^{-5} \\ Wn := 7 \cdot 10^{-6} & Ln := 7 \cdot 10^{-6} & WP := 7 \cdot 10^{-6} \\ \lambda n := 1.843384 \cdot 10^{-2} & & LP := 7 \cdot 10^{-6} \\ VDD := 5 & CL := 3 \cdot 10^{-12} & \end{array}$$

$$VGSn := VDD \quad Vsn := VGSn - VTOn \quad Vsn = 4.142$$

$$\beta n := \left( \frac{KPn}{2} \right) \cdot \left( \frac{Wn}{Ln} \right) \quad \beta p := \left( \frac{KPP}{2} \right) \cdot \left( \frac{WP}{LP} \right)$$

time at which a transition from saturation to Ohmic occurs

$$ts := \left( \frac{CL}{\beta n} \right) \cdot \left( \frac{VTOn}{Vsn^2} \right) \quad ts = 5.946 \cdot 10^{-9}$$

capacitor voltage for  $t \leq ts$ , Using  $\Phi(\cdot)$  as the unit step function,

$$vc1(t) := \left[ VDD - \left( \frac{\beta n}{CL} \right) \cdot Vsn^2 \cdot t \right] \cdot \Phi(ts - t) \quad vc1(ts) = 4.142$$

capacitor voltage for  $t \geq ts$ :


$$vc2(t) := \left[ \frac{(2 \cdot (Vsn))}{\left[ 1 + \exp \left[ 2 \cdot Vsn \cdot \left( \frac{\beta n}{CL} \cdot (t - ts) \right) \right] \right]} \right] \cdot \Phi(t - ts) \quad vc2(ts) = 4.142$$


combining the voltage for the two regions of time:

$$vc(t) := vc1(t) + vc2(t)$$

$$tmin := 0 \quad tmax := 1 \cdot 10^{-7} \quad \Delta t := 0.01 \cdot 10^{-7}$$

$$t := tmin, tmin + \Delta t .. tmax$$

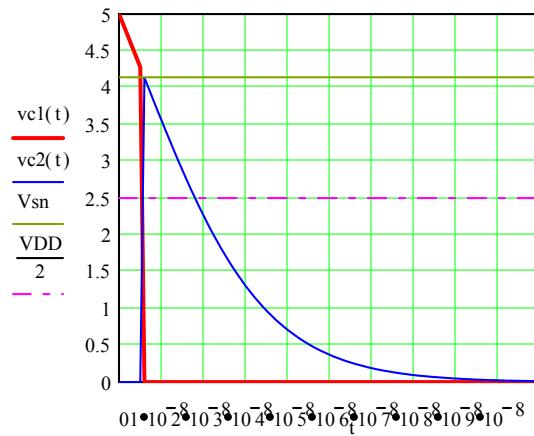

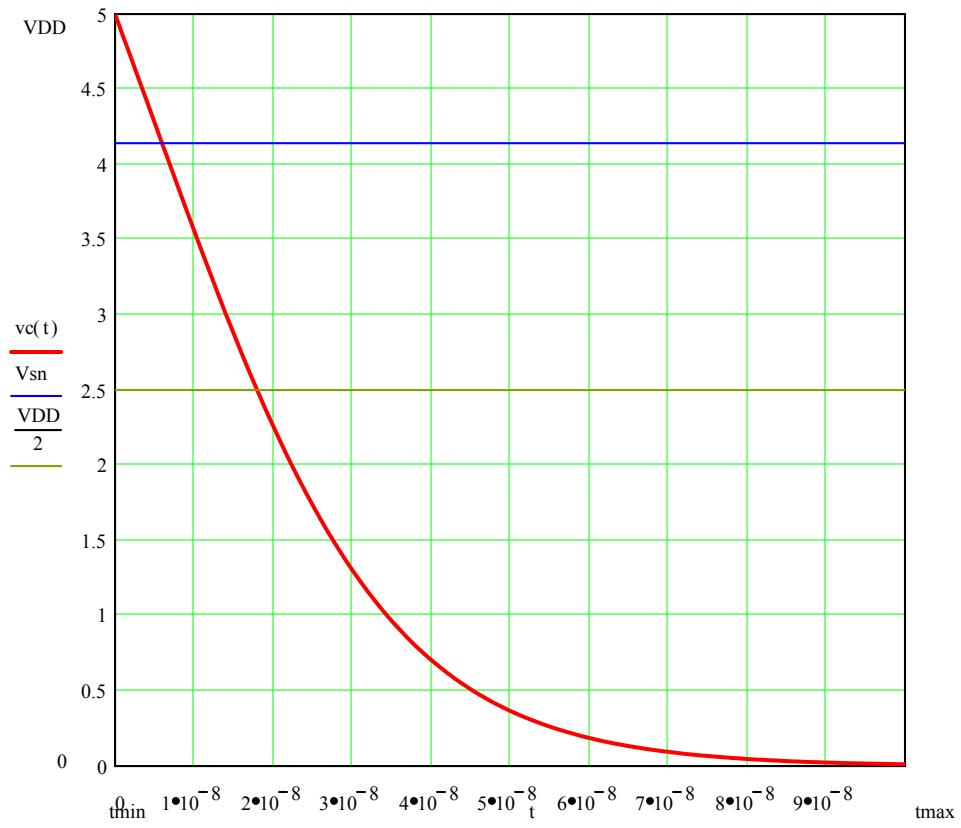

delay time,  $td$  = time to reach  $V_{\text{DD}}/2$ , which occurs in Ohmic region

$$td := ts - \left( \frac{CL}{\beta n} \right) \cdot \left( \frac{1}{2 \cdot V_{\text{sn}}} \right) \cdot \ln \left[ \frac{\left( \frac{V_{\text{DD}}}{V_{\text{sn}}} \right)}{\left[ 4 - \left( \frac{V_{\text{DD}}}{V_{\text{sn}}} \right) \right]} \right] \quad td = 1.798 \cdot 10^{-8}$$