

File: e:\courses\spring2006\434\hop\_ex1.doc RWN 03/02/06

The Hopfield neural network set up in class works well if the resistors are expressed as decimals rather than fractions - for some reason PSpice does not appear to accept rational fractions. So the decimal form is given below with the transient analysis results.

$$C \frac{dm}{dt} = +Wa - Gm + I_b ; m(0) \text{ given}$$

$$a = f(m)$$

$$W = \begin{bmatrix} 2.15568 & -0.035206 \\ -0.035213 & 2.1522 \end{bmatrix}, \quad v_1 := \begin{bmatrix} 0.5 \\ 0.25 \end{bmatrix}, \quad v_2 := \begin{bmatrix} -0.5 \\ 0.5 \end{bmatrix}$$

$$G := \begin{bmatrix} G1 & 0 \\ 0 & G2 \end{bmatrix}, \quad C := \begin{bmatrix} C1 & 0 \\ 0 & C2 \end{bmatrix}, \quad v_3 = \begin{bmatrix} 0.494563 \\ 0.3 \end{bmatrix}, \quad I = \begin{bmatrix} 0.012446 \\ -0.010841 \end{bmatrix}$$

$$y(v) := \begin{bmatrix} \tanh(v_1) \\ \tanh(v_2) \end{bmatrix}$$



