
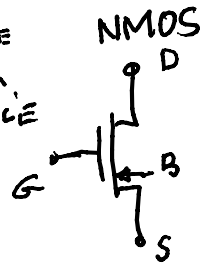


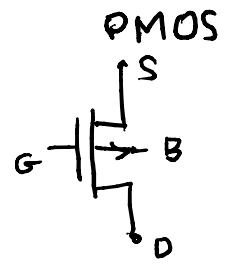BJT  
= bipolar  
junction  
transistor  
B = base  
E = emitter  
C = collector



EE303 *corrected*  
01/26/07




MOS  
= metal oxide  
silicon

G = gate  
S = source  
D = drain  
B = bulk

square law  
VCCS  
voltage controlled  
current source

polarity conventions

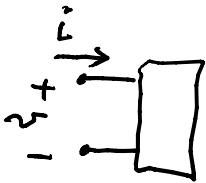

exponential  
laws


CCCS

"  
current controlled  
current source

diode: primitive level model




secondary model

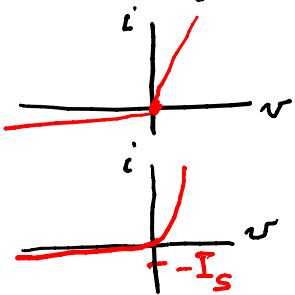

$$i = I_s (e^{v/V_T} - 1)$$

$$V_T = \frac{kT}{|q_{electron}|} = 0.026 \text{ V @ room temp}$$

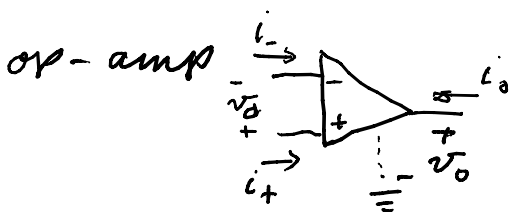

primary level  
 $v_d = 0, i_- = 0, i_+ = 0$

next level:  $v_o = K v_d, K > 0$   
 $i_- = i_+ = 0$

next level:  $i_- = i_+ = 0$ ;  $v_o = \frac{K}{1 + (s/\omega_0)} \cdot v_d$ ;  $s =$  Laplace transform variable


$=$  complex number or the derivative operator

if  $s = j\omega$  then means sinusoidal steady state




$$T(j\omega) = \frac{v_o}{v_d} = \frac{K}{1 + j(\omega/\omega_0)} = \text{transfer function of op-amp}$$

$$|T(j\omega)| = \left| \frac{v_o}{v_d}(j\omega) \right| = \frac{|K|}{|1 + j\frac{\omega}{\omega_0}|} = \frac{|K|}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$



if  $\omega = \omega_0$ ,  $\left| \frac{v_o}{v_d} \right| = \frac{K}{\sqrt{2}}$

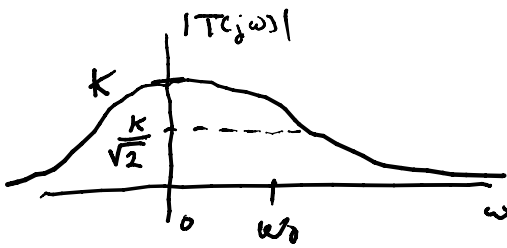


curves for BJT's

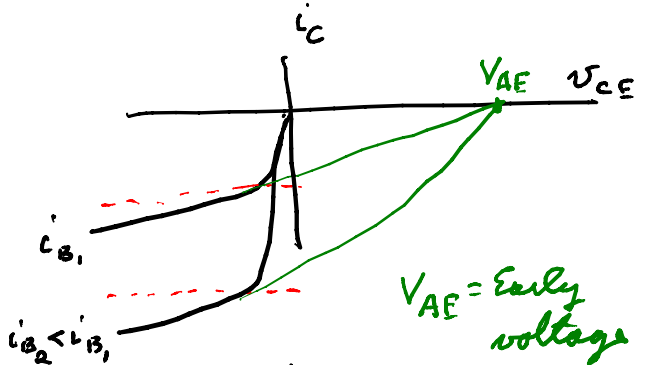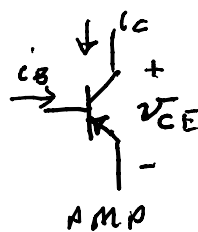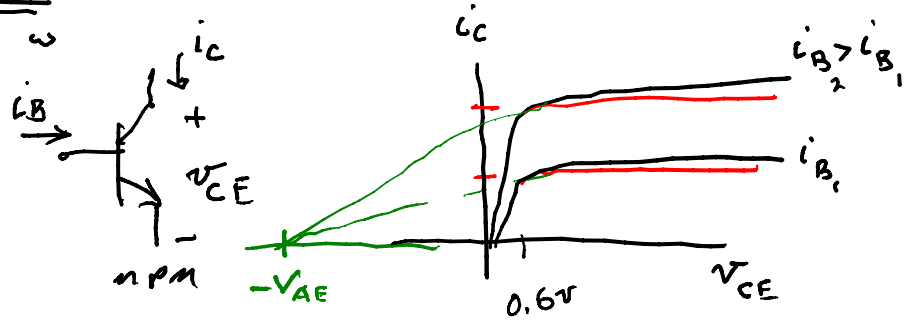

curves for MOS

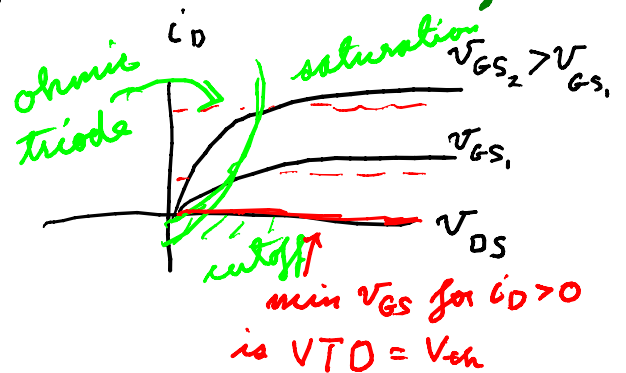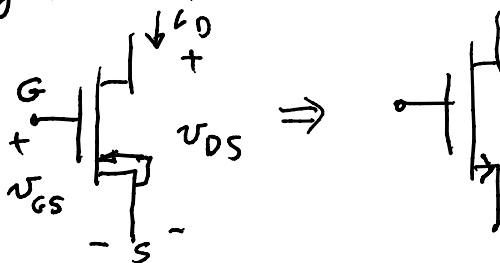

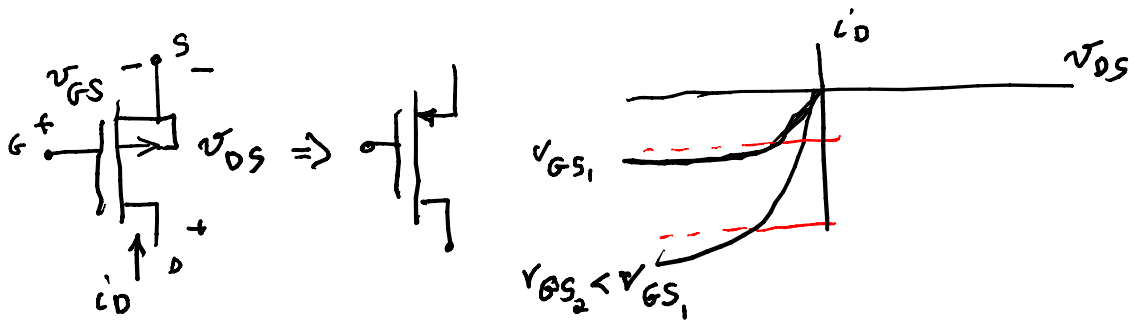

NMOS: (DC characteristics)

$$I_D = \frac{K_P}{2} \cdot \frac{W}{L} \begin{cases} 0 & V_{DS} \geq 0, \text{ but } V_{GS} < V_{TO} \\ (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS}) & V_{DS} \geq 0, \quad 0 \leq V_{GS} - V_{TO} \leq V_{DS} \\ (V_{GS} - V_{TO})V_{DS} - 2V_{DS}^2 & 0 \leq V_{DS} \leq V_{GS} - V_{TO} \end{cases}$$

correct the 2 to here

often ignore unless affect design