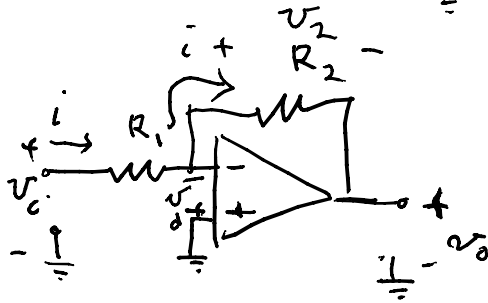


at case:  $v_d = 0 \Rightarrow v_i = R i$

$i_- = 0$


$v_c = -v_o = \frac{1}{sC} \cdot i = \frac{1}{sC} \cdot \frac{v_i}{R}$

$v_o = -\frac{1}{sRC} \cdot v_i$



$v_o = \frac{K}{1 + s/\omega_0} \cdot v_d$ ,  $K > 0$ ,  $\omega_0 > 0$

$i_- = 0, i_+ = 0$

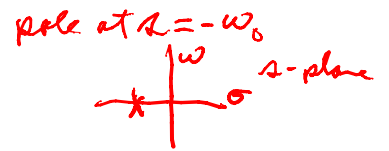



$v_i = R_1 i - v_d$  ;  $v_2 = R_2 i = -v_d - v_o$  }  $\frac{R_2}{R_1} v_i = -(1 + \frac{R_2}{R_1}) v_d - v_o$

$\Rightarrow v_d = \frac{(1 + s/\omega_0)}{K} v_o$

$\Rightarrow \frac{R_2}{R_1} v_i = -\left[ \frac{(R_2 + R_1)}{R_1} \left( \frac{1 + s/\omega_0}{K} \right) + 1 \right] v_o = -\frac{1}{K} \left[ \left( K + \frac{R_2 + R_1}{R_1} \right) + s \left( \frac{R_1 + R_2}{\omega_0 R_1} \right) \right] v_o$


$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \cdot \frac{K}{\left( K + \frac{R_2 + R_1}{R_1} \right) + \left( \frac{R_1 + R_2}{\omega_0 R_1} \right) s}$

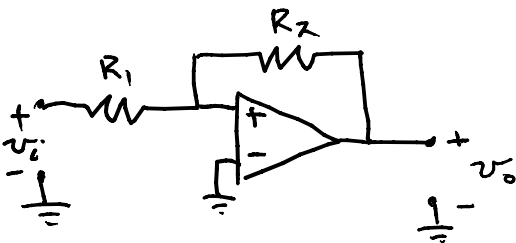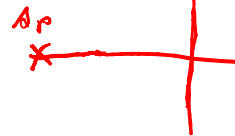pole:  $s_p = -\frac{(K + \frac{R_2 + R_1}{R_1})}{\left( \frac{R_1 + R_2}{\omega_0 R_1} \right)} < 0$



pole  $\Rightarrow s_p = -\left( \frac{-|K|}{\left( \frac{R_1 + R_2}{\omega_0} \right)} + \frac{1}{\omega_0} \right)$



as  $|K|$  is very large then  $s_p > 0$

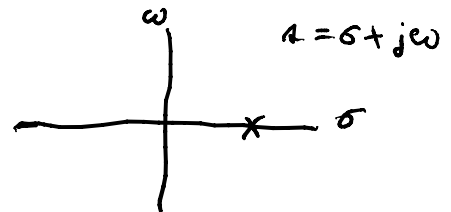

$\Rightarrow e^{+t}$

or this circuit unstable

$\Rightarrow$  saturates the op-amp.

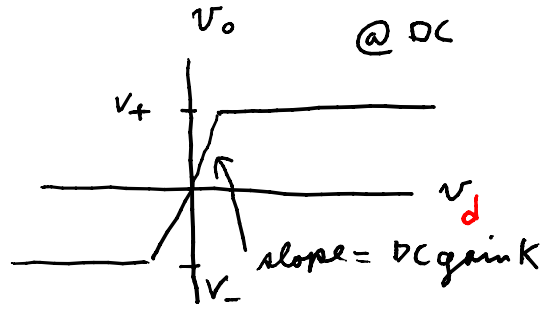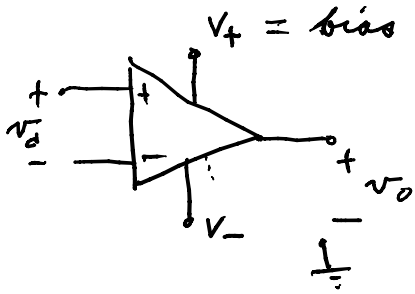

MOS fabrication  
 NMOS start with P-wafer

