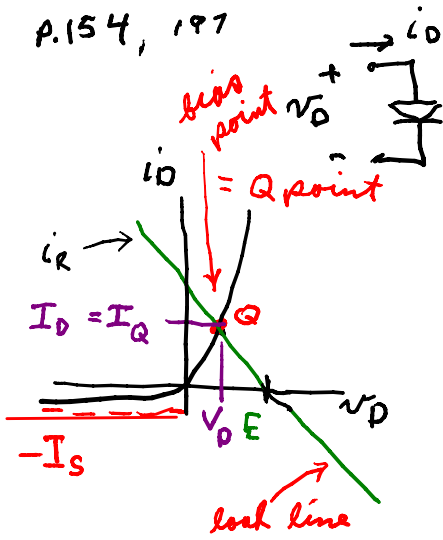



P.154, 197



$$i_D = I_S (e^{v_D / M V_T} - 1)$$

$$V_T = \frac{k_B T}{q} \approx 26 \text{ mV}$$


$$M \approx 1$$

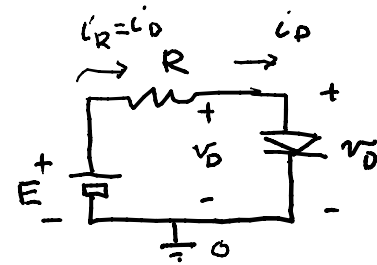


device: $i_D = I_S e^{v_D / V_T}$
 load: $v_D = -R i_D + E$
 or $i_D = -\frac{1}{R} (v_D - E)$
 $= -G (v_D - E) = i_R$

Q = quiescent

with signal v_a

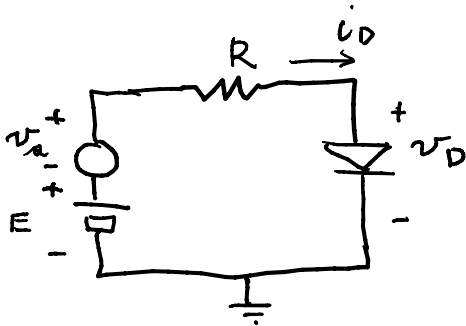

load: $i_D = i_R = -G (v_D - E - v_a)$

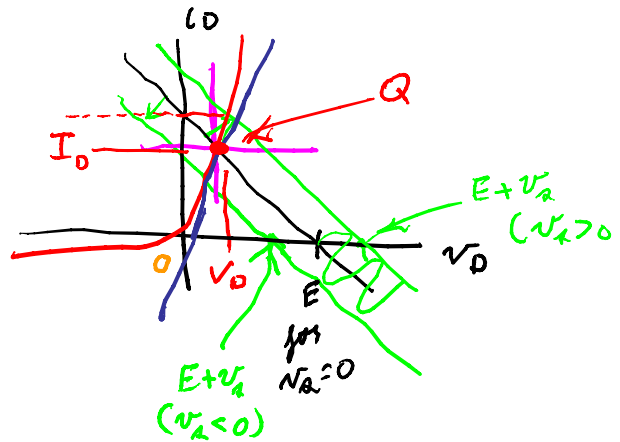

here

$$v_D = V_D + v_d \Rightarrow v_d = v_D - V_D$$

$$i_D = I_D + i_d \Rightarrow i_d = i_D - I_D$$

total bias signal

Next expand the device law equation

$$i_D = I_S (e^{v_D / V_T} - 1) = I_S \left[\underbrace{(e^{v_D / V_T} - 1)}_{I_D} + \underbrace{\frac{1}{V_T} e^{v_D / V_T}}_{i_d} (v_D - V_D) + \dots \right]$$

$$= I_D + i_d; i_d =$$


if ignore higher order terms
 $\Rightarrow (v_D - V_D) = v_d$

in the circuit

$$E + v_a = -R i_D + v_D = -R (I_D + i_d) + V_D + v_d$$

$$\text{but } E = -R I_D + V_D \Rightarrow v_a = -R i_d + v_d$$


has $|v_d| \ll E$

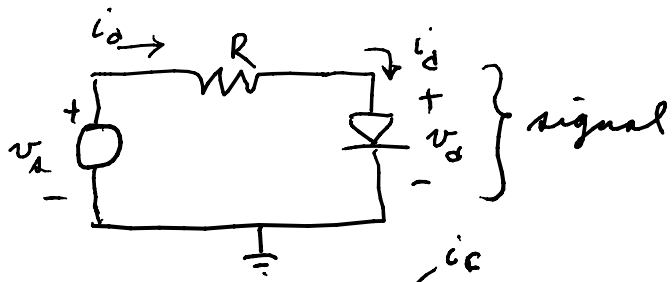

$$i_d = \frac{I_s}{V_T} e^{\frac{v_d}{V_T}} \cdot (v_d)$$

diode conductance

Transistor

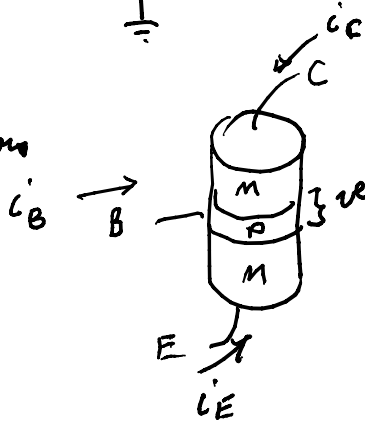

very thin so $i_C \approx -i_E$ use $i_C = -\alpha i_E$
 $\alpha \approx 1$

by KCL: $i_B + i_E + i_C = 0$

$$\Rightarrow i_B + \left(-\frac{1}{\alpha} i_C\right) + i_C = 0$$

$$\Rightarrow i_C = \frac{1}{\left(-1 + \frac{1}{\alpha}\right)} i_B = \frac{\alpha}{1 - \alpha} i_B = \beta i_B$$