

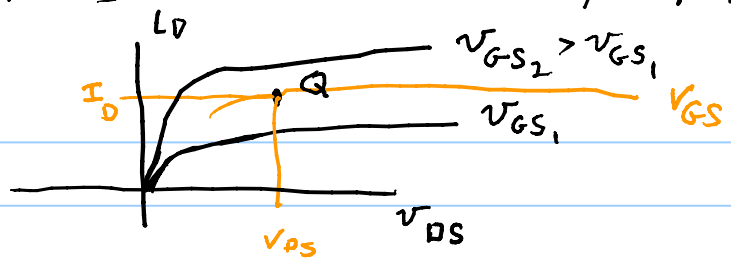


small signal for NMOS

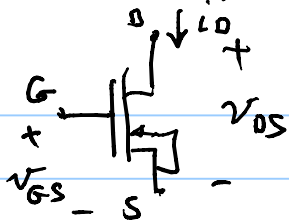


$$i_D = f(v_{GS}, v_{DS}) = f(V_{GS}, V_{DS}) + \left. \frac{\partial f}{\partial v_{GS}} \right|_Q (v_{GS} - V_{GS}) + \left. \frac{\partial f}{\partial v_{DS}} \right|_Q (v_{DS} - V_{DS}) + \dots$$
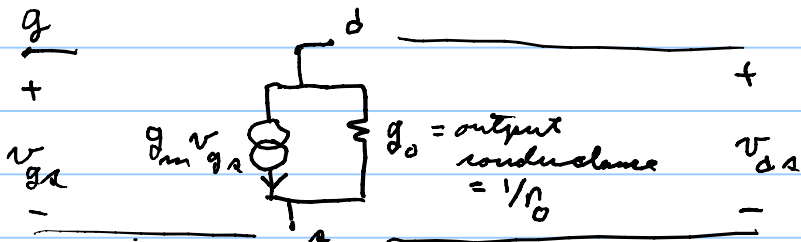
$$i_D - I_D = i_D' = g_m \cdot v_{gs} + g_o \cdot v_{ds} \quad (+ \dots \text{ which ignore if small enough } v_{gs}, v_{ds})$$



$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q$$

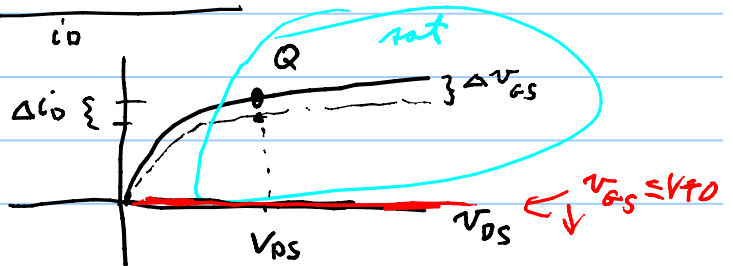


If in saturation: $i_D = \frac{K_P W}{2 L} (v_{GS} - V_{TO})^2 (1 + \lambda v_{DS})$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = 2 \left(\frac{K_P W}{2 L} \right) (v_{GS} - V_{TO}) (1 + \lambda v_{DS}) \Big|_Q$$

$$= 2 \left[\frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS}) \right] \Big|_Q$$


$$= 2 \frac{I_D}{(V_{GS} - V_{TO})}$$

$$g_o = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q = \text{slope of curve @ } Q$$

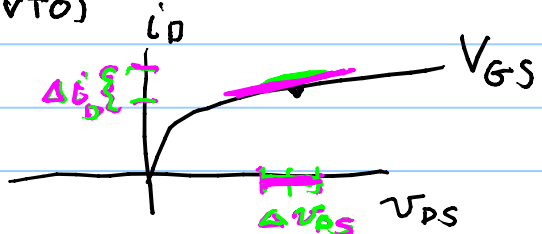

$$\frac{\partial i_D}{\partial v_{DS}} \Big|_Q = \frac{k_p W}{2L} (v_{GS} - V_{TO})^2 \cdot \lambda \Big|_Q = \frac{\lambda I_D}{(1 + \lambda v_{DS})} \Big|_Q = g_o = \frac{\lambda I_D}{1 + \frac{V_{DS}}{V_A}}$$

for small λ

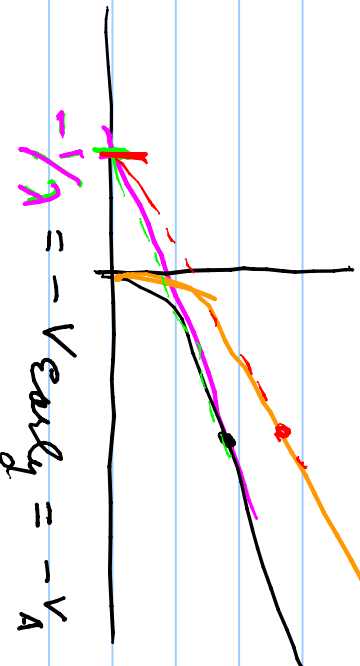

$$i_D = \frac{k_p W}{2L} (v_{GS} - V_{TO})^2 (1 + \lambda v_{DS})$$

