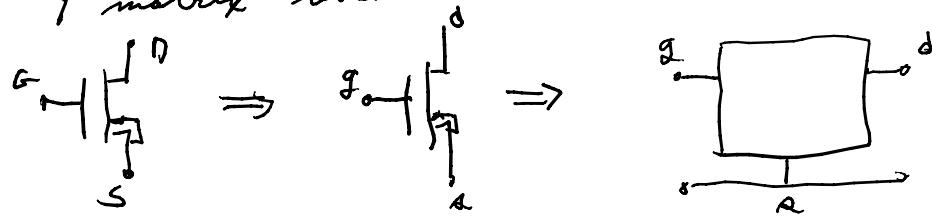



EE303  
02/09/07

small signal equivalent circuits

$\gamma$  matrix used:



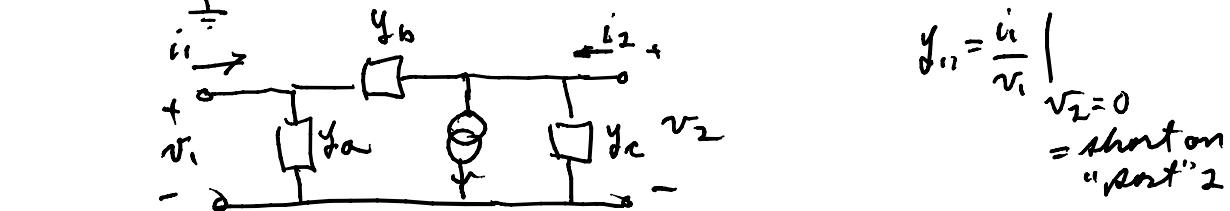
$$\begin{array}{c} i_1 \\ \downarrow \\ \text{v}_1 \\ \text{v}_2 \\ \uparrow \\ \text{lines} \\ \downarrow \\ i_1 \\ i_2 \\ \downarrow \\ \text{v}_2 \end{array} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} \text{v}_1 \\ \text{v}_2 \end{bmatrix} \Rightarrow i = \gamma v$$




$$g_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$

= shunt on "port" 2

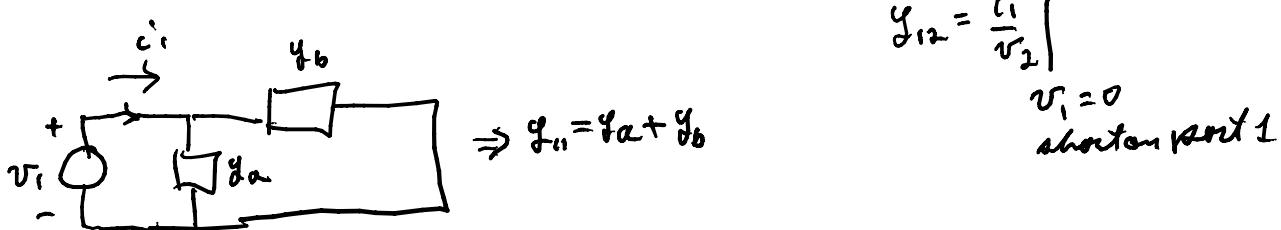

$$g_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}$$

shorten port 1

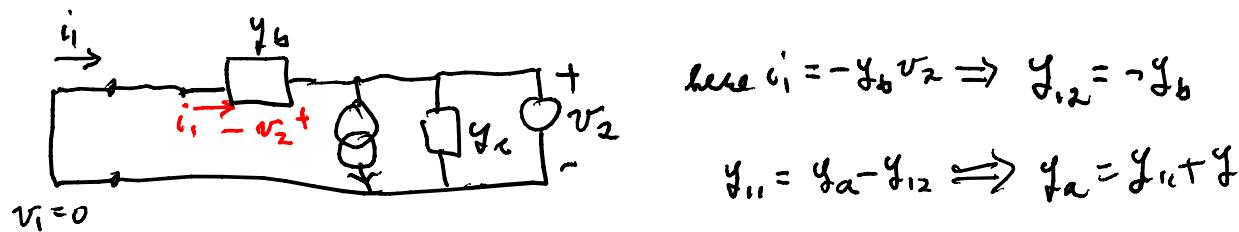


$$\text{here } i_1 = -g_b v_2 \Rightarrow g_{21} = -g_b$$

$$g_{21} = g_a - g_{12} \Rightarrow g_a = g_{11} + g_{12}$$

$$g_{21} = \frac{i_2}{v_1} \Big|_{v_2=0}$$


$$g_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

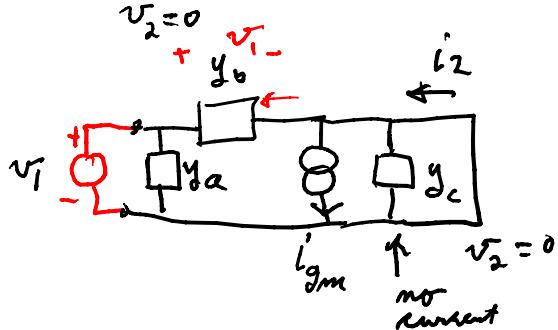



$$\text{here } i_2 = i_{g_m} + (-g_b v_1) \Rightarrow g_{22} = \frac{i_2}{v_2} \Big|_{v_2=0} = \frac{i_{g_m}}{v_1} - g_b$$

$$= \frac{i_{g_m}}{v_1} + g_{12}$$
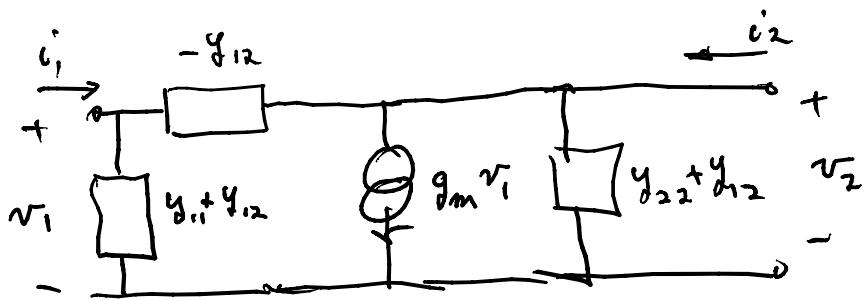
$$\Rightarrow \frac{i_{g_m}}{v_1} = g_{22} - g_{12} \triangleq g_m \quad (= \text{def. of } g_m)$$



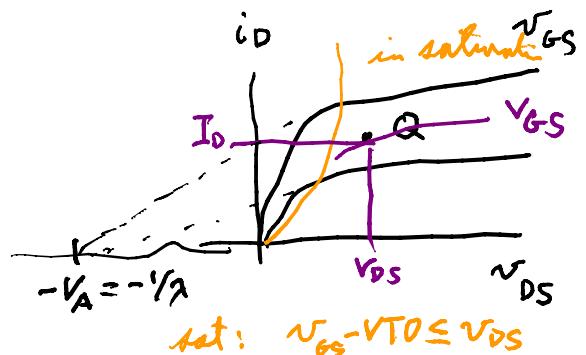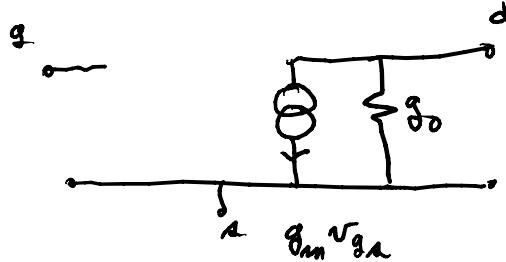this is the  $T$  equivalent circuit for a linear 2-port



$$g_m = \frac{2 I_D}{(V_{GS} - V_{TO})}$$

$$g_o = \frac{I_D}{V_A} \times \frac{1}{1 + V_{DS}/V_A}$$

$$Y = \begin{bmatrix} 0 & 0 \\ g_m & g_o \end{bmatrix}$$

$$i_D = \frac{K_P}{2} \frac{W}{L} (V_{GS} - V_{TO})^2 (1 + \gamma V_{DS})$$

$\text{Ex: } \left\{ \begin{array}{l} K_P = 2 \times 10^{-4} \frac{\text{amps}}{\text{volt}^2} ; W = 10\mu \text{m} \\ L = 10\mu \text{m} \end{array} \right. \quad V_{TO} = 1.1 \text{ volt} \\ V_A = 200 \text{ volt}$

B-S transistor properties

circuit choice:  $Q \quad V_{GS} = 3.1 \text{ V}, \quad V_{DS} = 3 \text{ V}$

check on transistor status:  $V_{GS} - V_{TO} = 2 \text{ V} < V_{DS} = 3 \text{ V}$

$$I_D = \frac{2 \times 10^{-4}}{2} \cdot \frac{10 \times 10^{-6}}{10 \times 10^{-6}} (2)^2 \left(1 + \frac{3}{200}\right) \approx 4 \times 10^{-4} \text{ amps} = 0.4 \text{ mA}$$


thus at  $Q$ :  $g_m = \frac{2 I_D}{(V_{GS} - V_{TO})} = \frac{2 \times 4 \times 10^{-4}}{2} = 0.4 \text{ m}-\text{S}$

$$r_0 = \frac{1}{g_o} = \frac{V_A}{I_D} = \frac{200}{4 \times 10^{-4}} = 50 \times 10^4 = 500 \text{ k}\Omega$$

For higher frequencies we need to add the capacitances  
total gate resistance is  $W \times L \times \frac{C_{ox}}{t_{ox}}$ ;  $\gamma = 2.43$   $C_{ox} = 3.45 \times 10^{-11} \frac{\text{F}}{\text{m}^2}$

"Useful" capacitance: in saturation:  $C_{gs} = \frac{2}{3} \cdot W \times L \times C_{ox}$   
 F. 321  
 $C_{gd} = 0$

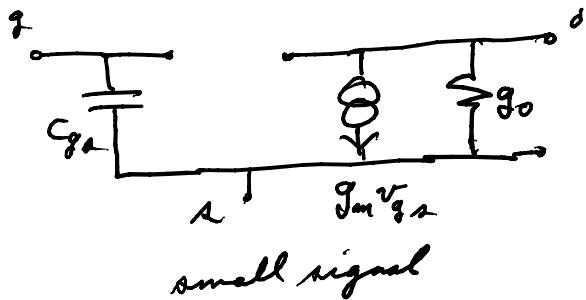in Ohmic:  $C_{gs} = C_{gd} = \frac{1}{2} W \times L \times C_{ox}$



$$Y(A) = \begin{bmatrix} C_{gs} \cdot R & 0 \\ g_m & g_d \end{bmatrix}$$