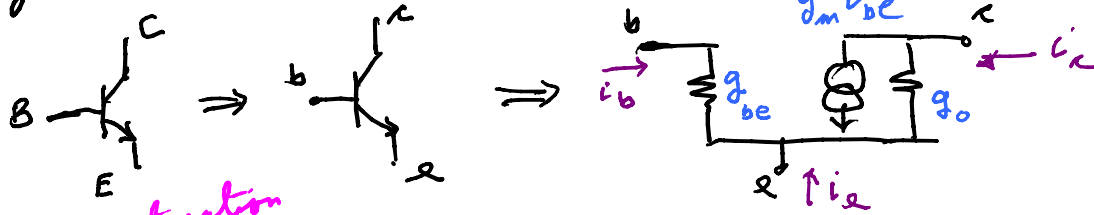



pp. 443-449

EE303
02/17/07

π equivalent for BJT grounded emitter, n-p-n





(small signal)

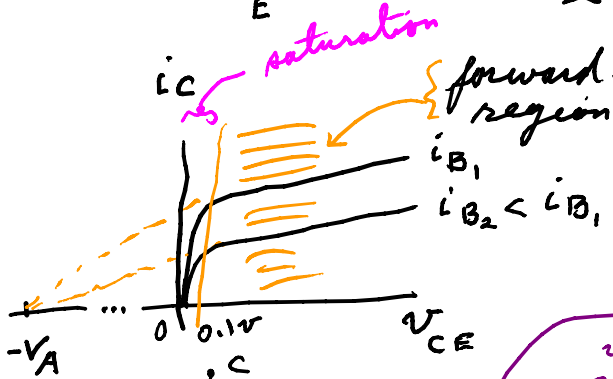

forward-active = forward bias B-E
back bias C-B

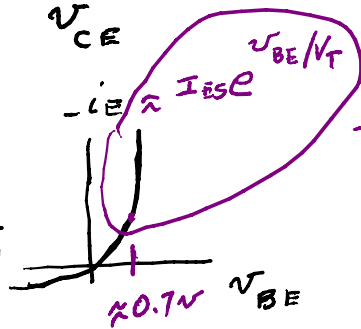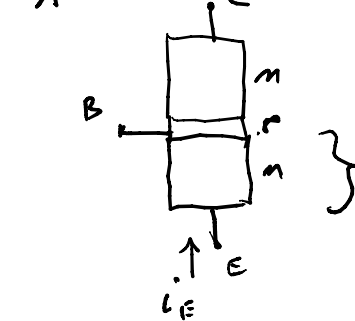for forward bias use $V_{BE} \approx 0.7V$



$$- \frac{d i_E}{d v_{BE}} = \frac{-I_E}{V_T}$$

$$i_C + i_B + i_E = 0$$

$$i_C + i_B + i_E = 0$$

$$i_C = \beta \cdot i_B = \alpha (-i_E)$$

$$\Rightarrow - \frac{d i_E}{d v_{BE}} = \frac{-I_E}{V_T} = \frac{1}{\alpha V_T} \cdot I_C$$


but derive for the π -eq.


$$\frac{d i_B}{d v_{BE}} = \frac{d(\frac{1}{\beta} i_C)}{d v_{BE}} = \frac{1}{\beta} \frac{d i_C}{d v_{BE}} = \frac{1}{\beta} \frac{d(-\alpha i_E)}{d v_{BE}} = \frac{\alpha}{\beta} \cdot \frac{d(-i_E)}{d v_{BE}} = \frac{\alpha}{\beta} \cdot \frac{I_C}{\alpha V_T}$$

$$g_{be} \cdot v_{be} = i_b \Rightarrow \frac{i_b}{v_{be}} = g_{be} = g_{\pi} = \frac{I_C}{\beta V_T}$$

$$g_o = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_Q = \frac{I_{CQ}}{V_A + V_{CE}} \approx \frac{I_{CQ}}{V_A}$$

$$= \frac{i_c}{v_{ce}}$$

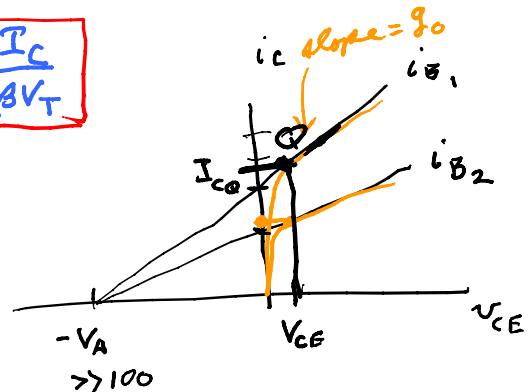

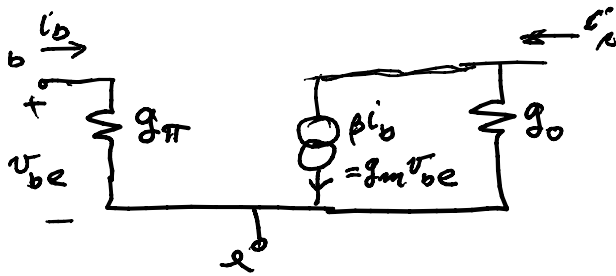

$$i_c = \beta i_b$$

$$\text{but } i_b = g_\pi v_{be}$$

$$\Rightarrow \beta i_b = \beta g_\pi v_{be} = i_c \quad | \quad \Delta v_{ce} = 0$$

$$\Rightarrow i_c = g_m v_{be} \Rightarrow$$

$$g_m = \beta g_\pi = \beta \frac{I_c}{\beta V_T}$$

$$= \frac{I_c}{V_T}$$

$$g_\pi = \frac{I_c}{\beta V_T} = \frac{1}{\beta} g_m$$

$$g_m = \frac{I_c}{V_T}; \quad g_o = \frac{I_c}{V_A}$$

$\therefore I_c$ fixes the π eq. once know the transistor parameters

$$\beta, V_A; \quad V_T = kT/q$$

Hybrid π equivalent circuit: add in series "lead" resistors

