

For $Y = \begin{bmatrix} \Delta C_{in} & 0 \\ g_m & g_o \end{bmatrix}$ then $\frac{v_o}{v_i} = \frac{-R_L g_m}{1 + R_L g_o}$


if $R_L g_o \ll 1$ $\frac{v_o}{v_i} = -R_L g_m$

If at low frequencies (\approx DC) $\Delta C_{in} \rightarrow 0$

$$\frac{v_o}{v_i} = \frac{-R_L g_m}{1 + R_S \times 0 + R_L g_o + R_L R_S \times 0}$$

" $\Delta = 0$ if $\Delta C_{in} \rightarrow 0$ "

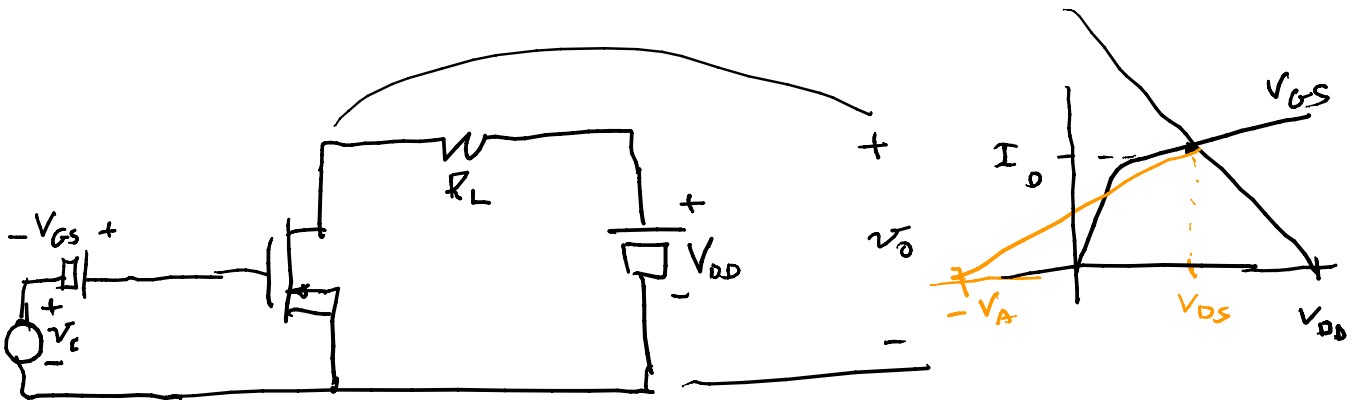an ^N MOS bias: $I_D = \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS})$



Ex: $\frac{K_P}{2} = 2 \times 10^{-4}$, $V_{TO} = 0.99$, $W = L = 10 \mu = 10^{-5} \text{ m}$

$\lambda = \frac{1}{V_A} = \frac{1}{100}$; $V_{DD} = 5$, $t_{ox} = 400 \text{ \AA} = 400 \times 10^{-10} \text{ m}$


$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11} \text{ Fd/m}}{4 \times 10^{-8} \text{ m}}$; $C_{gate} = W \times L \times C_{ox} = 10^{-5} \times 10^{-5} \times \frac{3.45}{4} \times 10^{-3} \text{ Fd}$

to check or saturation; use $V_{GS} = 2 \times V_{TO}$, $I_D = 0.2 \text{ ma} = 1.98 \text{ v}$ (check) \uparrow

use $I_D = \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS})$ to get V_{DS}

$$V_{DS} = \frac{-1 + \frac{I_D}{\frac{K_P W}{2 L} (V_{GS} - V_{TO})^2}}{\lambda} = \left(-1 + \frac{0.2 \times 10^{-3}}{2 \times 10^{-4} (0.99)^2} \right) \times V_A = 2.03 \text{ v}$$

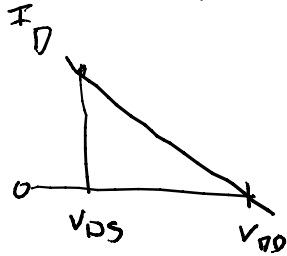for sat: $V_{DS} > V_{GS} - V_{TO} = V_{TO} = 0.99 \Rightarrow$ in saturation
 2.03



$$\text{slope} = G_L = \frac{I_D}{V_{DD} - V_{DS}} = \frac{0.2 \times 10^{-3}}{5 - 2.03} = 0.673 \times 10^{-3}$$

$$R_L = \frac{1}{G_L} = 1.485 \text{ K}\Omega = 1,485 \Omega$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TO}} = \frac{2 \times 0.2 \times 10^{-3}}{0.99} = 4.04 \times 10^{-4} \text{ S}$$

$$g_o = \frac{I_D}{V_A} = \frac{0.2 \times 10^{-3}}{100} = 2 \times 10^{-6}, \quad V_o = \frac{1}{2 \times 10^{-6}} = 500 \text{ K}\Omega$$

$$C_{gs} = C_{in} = \frac{2}{3} C_{gate} = \frac{2}{3} \times \frac{3.45}{4} \times 10^{-13} = 0.0575 \times 10^{-12} \text{ F}_d \\ = 0.06 \text{ pF}_d$$

$$Y = \begin{bmatrix} \Delta C_{in} & 0 \\ g_m & g_o \end{bmatrix}, \quad -R_L g_m = -1.485 \times 10^3 \times 4.04 \times 10^{-4} \\ = -6 \times 10^{-1} = -0.6$$

\therefore near DC get a "loss"

to eliminate the 1st battery